Example 11.3 *continued*

$A\beta \equiv -V_r/V_t$ involves repeated application of the voltage divider rule, resulting in

$$A\beta = \mu \frac{\{R_L \parallel [R_2 + R_1 \parallel (R_{id} + R_s)]\}}{\{R_L \parallel [R_2 + R_1 \parallel (R_{id} + R_s)]\} + r_o} \times \frac{[R_1 \parallel (R_{id} + R_s)]}{[R_1 \parallel (R_{id} + R_s)] + R_2} \times \frac{R_{id}}{R_{id} + R_s}$$

EXERCISE

11.6 For the feedback voltage amplifier of Fig. 11.8(c):

(a) Find an expression for β.

(b) Neglecting the MOSFET r_o, find an expression for the loop gain $A\beta$. (*Hint*: Break the loop at the gate of Q.)

(c) Find an expression for the open-loop gain A.

(d) For $g_m = 4$ mA/V, $R_D = 10$ kΩ, $R_1 = 20$ kΩ, and $R_2 = 80$ kΩ, find the values of β, $A\beta$, A, and the closed-loop gain A_f. What would A_f be if $A\beta$ were much greater than unity?

Ans. (a) $\frac{R_1}{R_1 + R_2}$; (b) $g_m \frac{R_D R_1}{R_D + R_1 + R_2}$; (c) $g_m \frac{R_D(R_1 + R_2)}{R_D + R_1 + R_2}$; (d) 0.2, 7.27, 36.36 V/V, 4.4 V/V, 5 V/V.

11.3.4 A Final Remark

The loop-gain analysis method, though simple, is not complete: It does not enable us to find the input and output resistances of the feedback amplifier. This shortcoming is remedied in the next section, where we present a systematic approach to the analysis of feedback voltage amplifiers.

11.4 Systematic Analysis of Feedback Voltage Amplifiers

In this section we provide a systematic procedure for the analysis of feedback voltage amplifiers. The procedure essentially disassembles a given feedback voltage-amplifier circuit so as to obtain the "A circuit," from which we can determine the open-loop gain A and other parameters of the open-loop amplifier, such as the input and output resistances, and the "β circuit" from which the value of the feedback factor β can be found. We can then use the

feedback formulas to determine the characteristic parameters of the feedback amplifier, such as the closed-loop gain A_f and the input and output resistances with feedback.

Our approach will be to first consider the *ideal* case in which the feedback network does *not* load the basic amplifier. Then, we consider the practical case in which not only does the feedback network load the basic amplifier, but also there is a finite source resistance R_s and a finite load resistance R_L.

11.4.1 The Ideal Case

As mentioned before, series–shunt is the appropriate feedback topology for a voltage amplifier.The ideal structure of the series–shunt feedback amplifier is shown in Fig. 11.12(a). It consists of a *unilateral* open-loop amplifier (the A circuit) and an ideal voltage-sampling, voltage-mixing feedback network (the β circuit). The A circuit has an input resistance R_i, an open-circuit voltage gain A, and an output resistance R_o. It is assumed that the source is ideal with a zero resistance and that there is no load resistance. Furthermore, note that the β circuit

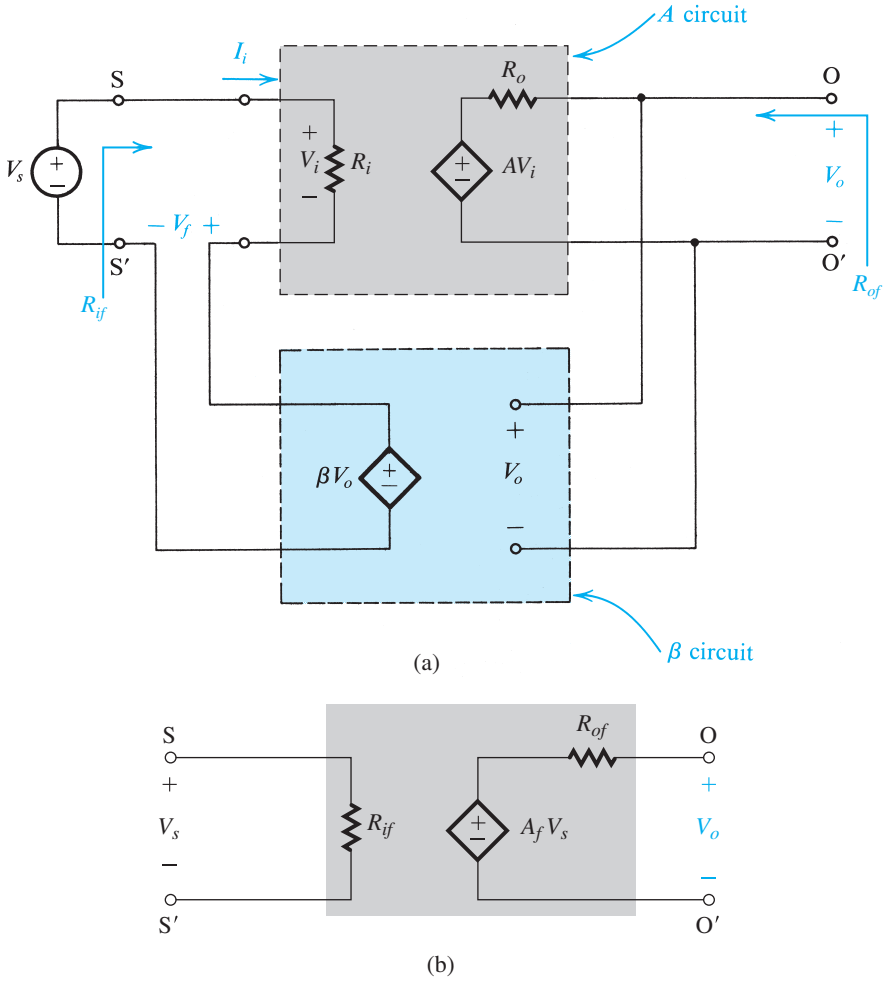


Figure 11.12 The series–shunt feedback amplifier: **(a)** ideal structure; **(b)** equivalent circuit.

does *not* load the A circuit; that is, connecting the β circuit does not change the value of A (defined as $A \equiv V_o/V_i$).

The circuit of Fig. 11.12(a) exactly follows the ideal feedback model of Fig. 11.1. Therefore the closed-loop voltage gain A_f is given by

$$A_f \equiv \frac{V_o}{V_s} = \frac{A}{1+A\beta} \tag{11.18}$$

The equivalent-circuit model of the series–shunt feedback amplifier is shown in Fig. 11.12(b). Observe that A_f is the open-circuit voltage gain of the feedback amplifier, R_{if} is its input resistance, and R_{of} is its output resistance. Expressions for R_{if} and R_{of} can be derived as follows.

For R_{if}, refer to the input loop of the circuit in Fig. 11.12(a). The series mixing subtracts V_f from V_s and thus reduces V_i by a factor equal to the amount of feedback (Eq. 11.7),

$$V_i = \frac{V_s}{1+A\beta}$$

Thus the input current I_i becomes

$$I_i = \frac{V_i}{R_i} = \frac{V_s}{(1+A\beta)R_i} \tag{11.19}$$

Since I_i is the current drawn from V_s, the input resistance R_{if} can be expressed as

$$R_{if} \equiv \frac{V_s}{I_i}$$

and using Eq. (11.19) is found to be

$$R_{if} = (1+A\beta)R_i \tag{11.20}$$

Thus, as expected, the series-mixing feedback results in an increase in the amplifier input resistance by a factor equal to the amount of feedback, $(1+A\beta)$, a highly desirable property for a voltage amplifier.

To determine the output resistance R_{of} of the feedback amplifier in Fig. 11.12(a), we set $V_s = 0$ and apply a test voltage V_x between the output terminals, as shown in Fig. 11.13. If the current drawn from V_x is I_x, the output resistance R_{of} is

$$R_{of} \equiv \frac{V_x}{I_x} \tag{11.21}$$

An equation for the output loop yields

$$I_x = \frac{V_x - AV_i}{R_o} \tag{11.22}$$

From the input loop we see that

$$V_i = -V_f$$

Now $V_f = \beta V_o = \beta V_x$; thus,

$$V_i = -\beta V_x$$

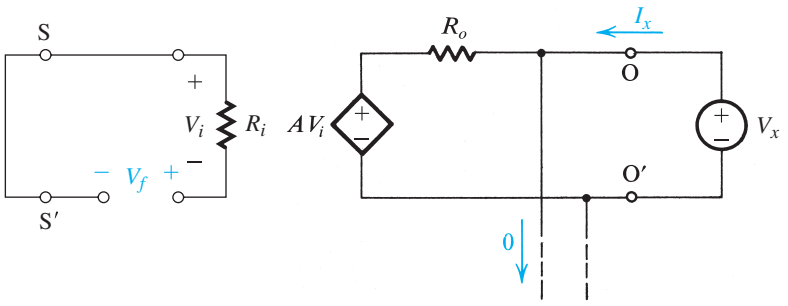


Figure 11.13 Determining the output resistance of the feedback amplifier of Fig. 11.12(a): $R_{of} = V_x/I_x$.

which when substituted in Eq. (11.22) yields

$$I_x = \frac{V_x(1+A\beta)}{R_o}$$

Substituting this value of I_x into Eq. (11.21) provides the following expression for R_{of},

$$R_{of} = \frac{R_o}{1+A\beta} \tag{11.23}$$

Thus, as expected, the shunt sampling (or voltage sampling) at the output results in a decrease in the amplifier output resistance by a factor equal to the amount of negative feedback, $(1+A\beta)$, another highly desirable property for a voltage amplifier.


Although perhaps not entirely obvious, the reduction of the output resistance is a result only of the method of sampling the output and does not depend on the method of mixing. Thus, the transistance amplifier, which is the other amplifier type in which shunt (or voltage) sampling is employed, will also exhibit a reduced output resistance.

11.4.2 The Practical Case


In a practical series–shunt feedback amplifier, the feedback network will not be an ideal voltage-controlled voltage source. Rather, as in the circuits of Fig. 11.8, the feedback network is usually resistive and hence will load the basic amplifier and thus affect the values of A, R_i, and R_o. In addition, there will be finite source and load resistances, which in turn will affect these three parameters. Thus the problem we have is as follows: Given a series–shunt feedback amplifier represented by the block diagram of Fig. 11.14(a), find the A circuit and the β circuit.

The problem in essence is to represent the general feedback voltage amplifier of Fig. 11.14(a) with the ideal structure of Fig. 11.12(a). The solution is presented, without derivation, in Fig. 11.14(b). We make the following observations.

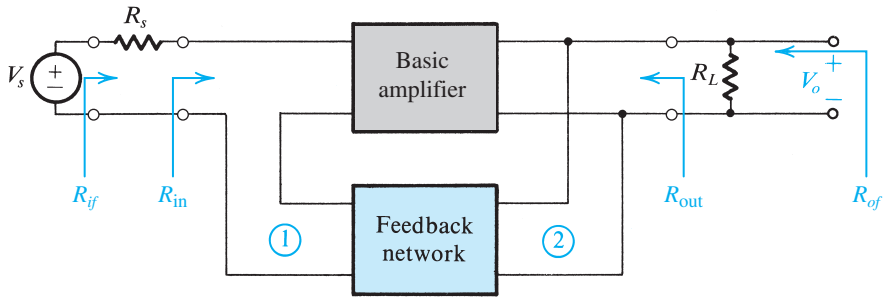
1. The A circuit is obtained by augmenting the basic amplifier at the input with the source resistance R_s and a resistance R_{11}, and at the output with the load resistance R_L and a resistance R_{22}. Resistances R_{11} and R_{22} represent the loading effect of the feedback network on the basic amplifier at the input and the output, respectively.
2. Resistance R_{11} is the resistance looking into port 1 of the feedback network while port 2 is short-circuited. Resistance R_{22} is the resistance looking into port 2 of the




(a)

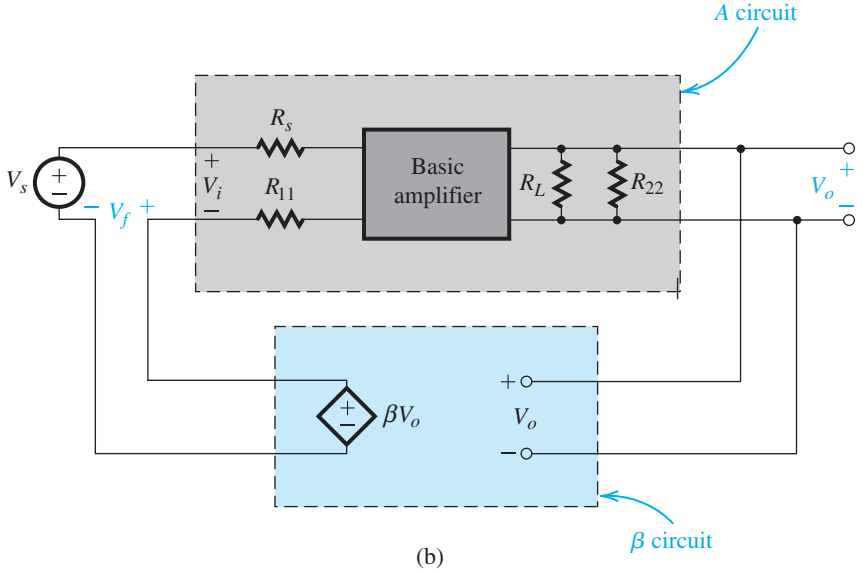

(b)

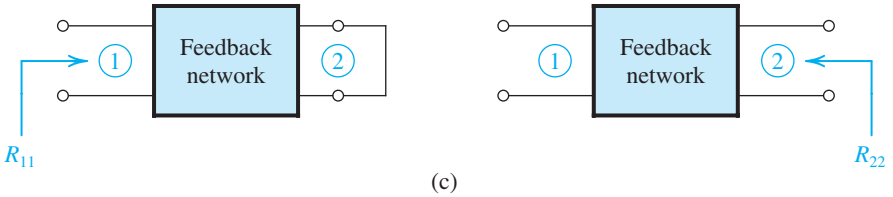


(c)

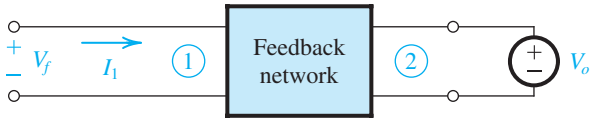

$$\beta \equiv \frac{V_f}{V_o}\bigg|_{I_1 = 0}$$

(d)

Figure 11.14 **(a)** Block diagram of a practical series–shunt feedback amplifier. **(b)** The circuit in **(a)** represented by the ideal structure of Fig. 11.12(a). **(c)** Definition of R_{11} and R_{22}. **(d)** Determination of the feedback factor β. **(e)** The A circuit, showing the open-loop resistances R_i and R_o.

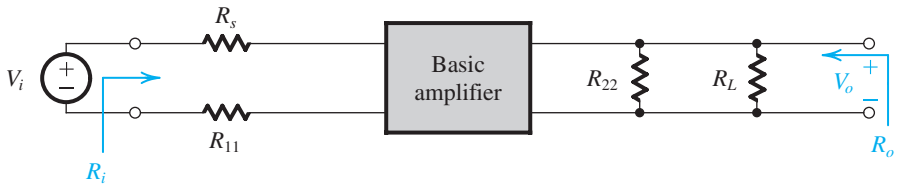

(e)

Figure 11.14 *continued*

feedback network while port 1 is open-circuited. These definitions are illustrated in Fig. 11.14(c). Since the feedback network is connected in shunt with the output, shorting its port 2 destroys the feedback. Similarly, because the feedback network is connected in series with the input, opening its port 1 destroys the feedback. It follows that the loading effect of the feedback network is obtained by looking into its appropriate port while the other port is open-circuited or short-circuited so as to destroy the feedback.[4]

3. The feedback factor β is the transmission from port 2 to port 1 of the feedback network, with port 1 open-circuited (which destroys the feedback). Reference to Fig. 11.14(c) shows that

$$\beta \equiv \left.\frac{V_f}{V_o}\right|_{I_1=0} \tag{11.24}$$

4. The open-loop gain A can be obtained from the A circuit in Fig. 11.14(e) as $A = \dfrac{V_o}{V_i}$

5. The values of A and β can be used to determine the closed-loop gain A_f,

$$A_f \equiv \frac{V_o}{V_s} = \frac{A}{1+A\beta}$$

6. The open-loop input resistance R_i and output resistance R_o can be determined from the A circuit [see Fig. 11.14(e)]. These values can be used to determine the input and output resistances with feedback,

$$R_{if} = R_i(1+A\beta)$$
$$R_{of} = R_o/(1+A\beta)$$

From Fig. 11.14(a) we see that R_{if} is the resistance seen by the ideal signal source V_s. The actual input resistance of the feedback amplifier R_{in} excludes R_s and is found from R_{if},

$$R_{\text{in}} = R_{if} - R_s \tag{11.25}$$

[4] A simple rule to remember: If the connection is *sh*unt, *sh*ort it; if *se*ries, *se*ver it.

Similarly, R_{of} is the output resistance of the feedback amplifier including R_L. The actual output resistance excludes R_L (see Fig. 11.14(a)) and is found from R_{of},

$$R_{\text{out}} = 1 \Big/ \left(\frac{1}{R_{of}} - \frac{1}{R_L} \right) \tag{11.26}$$

A final and important note: The representation in Fig. 11.14(b) is only *approximately* equivalent to the original circuit in Fig. 11.14(a). The approximation is a result of neglecting the small forward transmission in the feedback network relative to the much larger forward transmission in the basic amplifier. Also, recall that we continue to assume that the basic amplifier is unilateral—that is, it does not have internal feedback; all the feedback occurs in the feedback network and is represented by the feedback factor β.

Example 11.4

Figure 11.15(a) shows an op amp connected in the noninverting configuration. The op amp has an open-circuit voltage gain μ, a differential input resistance R_{id}, and an output resistance r_o. Recall that in our analysis of op-amp circuits in Chapter 2, we neglected the effects of R_{id} (assumed it to be infinite) and of r_o (assumed it to be zero). Here we wish to use the feedback method to analyze the circuit taking both R_{id} and r_o into account. Find expressions for A, β, the closed-loop gain V_o/V_s, the input resistance R_{in} [see Fig. 11.15(a)], and the output resistance R_{out}. Also find numerical values, given $\mu = 10^4$, $R_{id} = 100\,\text{k}\Omega$, $r_o = 1\,\text{k}\Omega$, $R_L = 2\,\text{k}\Omega$, $R_1 = 1\,\text{k}\Omega$, $R_2 = 1\,\text{M}\Omega$, and $R_s = 10\,\text{k}\Omega$. Note that this circuit was analyzed in Example 11.3 using the loop-gain method and, where appropriate, compare results.

Solution

We observe that the feedback network consists of R_2 and R_1. This network samples the output voltage V_o and provides a voltage signal (across R_1) that is mixed in series with the input source V_s.

The A circuit can be easily obtained following the rules of Fig. 11.14, and is shown in Fig. 11.15(b). Observe that the loading effect of the feedback network at the input side is obtained by short-circuiting port 2 of the feedback network (because it is connected in shunt) and looking into port 1, with the result that $R_{11} = R_1 \parallel R_2$. The loading effect of the feedback network at the output side is found by open-circuiting port 1 (because it is connected in series) and looking into port 2, with the result that $R_{22} = R_2 + R_1$. For the resulting A circuit in Fig. 11.15(b), we can write by inspection:

$$A \equiv \frac{V_o}{V_i} = \mu \frac{R_L \parallel (R_1 + R_2)}{\left[R_L \parallel (R_1 + R_2)\right] + r_o} \frac{R_{id}}{R_{id} + R_s + (R_1 \parallel R_2)}$$

For the values given, we find that $A \simeq 6000$ V/V.

The circuit for determining β is shown in Fig. 11.15(c), from which we obtain

$$\beta \equiv \frac{V_f}{V_o} = \frac{R_1}{R_1 + R_2} \simeq 10^{-3}\ \text{V/V}$$

Thus,

$$A\beta = 6000 \times 10^{-3} = 6$$

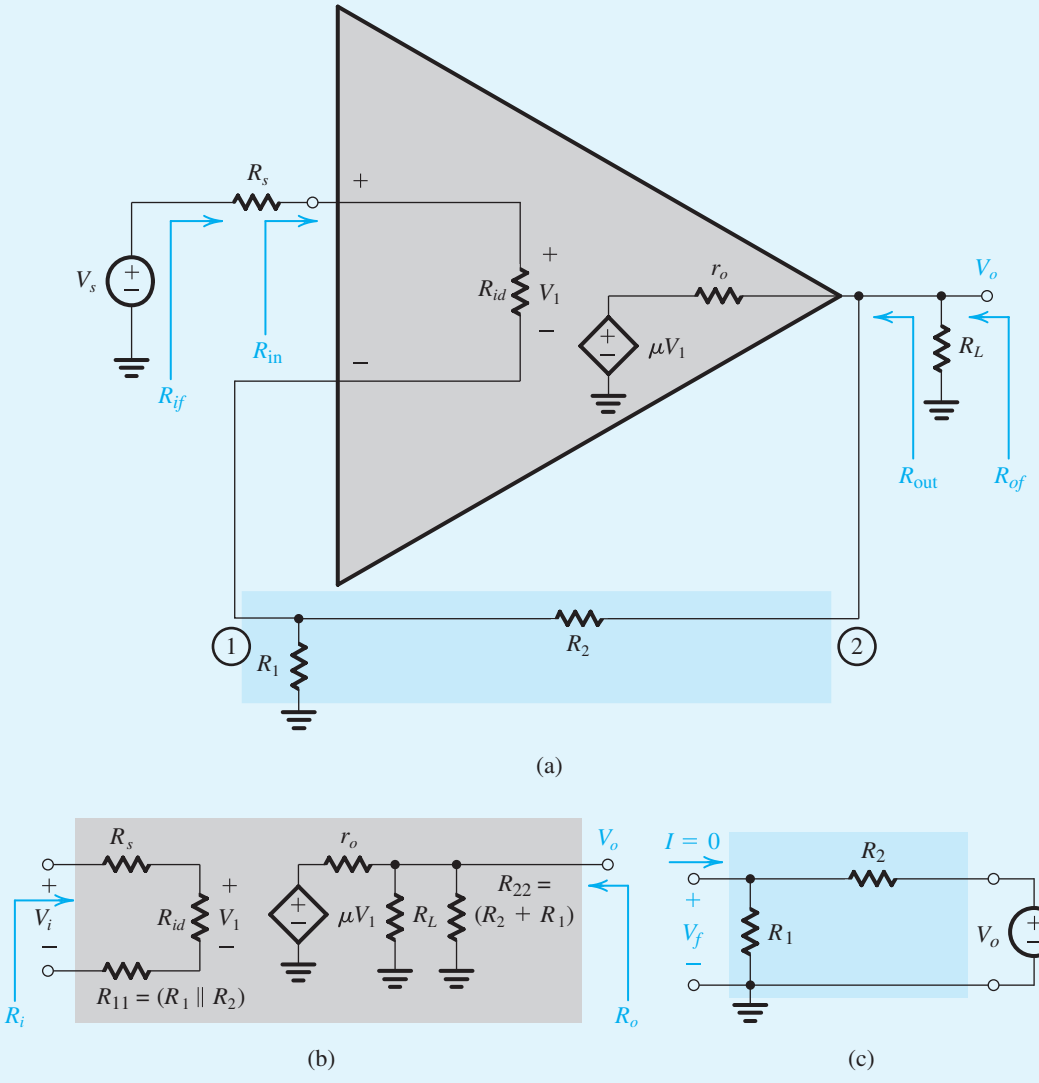


Figure 11.15 Circuits for Example 11.4.

and

$$1 + A\beta = 7$$

Identical results are obtained by substituting the given numerical values into the expression for $A\beta$ derived in Example 11.3.

The voltage gain with feedback can now be obtained as

$$A_f \equiv \frac{V_o}{V_s} = \frac{A}{1 + A\beta} = \frac{6000}{7} = 857 \text{ V/V}$$

Example 11.4 *continued*

The input resistance R_{if} determined by the feedback equations is the resistance seen by the external source (see Fig. 11.15a), and is given by

$$R_{if} = R_i(1 + A\beta)$$

where R_i is the input resistance of the A circuit in Fig. 11.15(b):

$$R_i = R_s + R_{id} + (R_1 \parallel R_2)$$

For the values given, $R_i \simeq 111$ kΩ, resulting in

$$R_{if} = 111 \times 7 = 777 \text{ k}\Omega$$

This, however, is not the resistance asked for. What is required is R_{in}, indicated in Fig. 11.15(a). To obtain R_{in} we subtract R_s from R_{if}:

$$R_{\text{in}} = R_{if} - R_s = 767 \text{ k}\Omega$$

The resistance R_{of} given by the feedback equations is the output resistance of the feedback amplifier, including the load resistance R_L, as indicated in Fig. 11.15(a). R_{of} is given by

$$R_{of} = \frac{R_o}{1 + A\beta}$$

where R_o is the output resistance of the A circuit. R_o can be obtained by inspection of Fig.11.15(b) with V_i set to zero, as

$$R_o = r_o \parallel R_L \parallel (R_2 + R_1)$$

For the values given, $R_o \simeq 666\,\Omega$, and

$$R_{of} = \frac{666}{7} = 95.2\ \Omega$$

The resistance asked for, R_{out}, is the output resistance of the feedback amplifier excluding R_L. From Fig. 11.15(a) we see that


$$R_{of} = R_{\text{out}} \parallel R_L$$

Thus


$$R_{\text{out}} \simeq 100\ \Omega$$

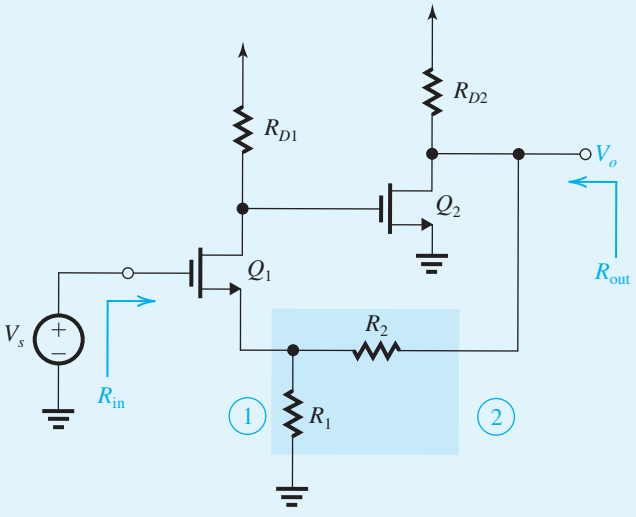Example 11.5


As another example of a series–shunt feedback amplifier, consider the circuit shown in Fig. 11.8(b), which we analyzed in Example 11.2 by determining the loop gain $A\beta$. In this example we wish to first analyze the circuit using our systematic procedure and then compare the results to those obtained in Example 11.2. For convenience, the circuit is repeated in Fig. 11.16(a). It is required to obtain the voltage gain V_o/V_s, input resistance R_{in}, and output resistance R_{out}. Find numerical values for the case $g_{m1} = g_{m2} = 4$ mA/V, $R_{D1} = R_{D2} = 10$ kΩ, $R_1 = 1$ kΩ, and $R_2 = 9$ kΩ. For simplicity, neglect r_o of each of Q_1 and Q_2.



(a)

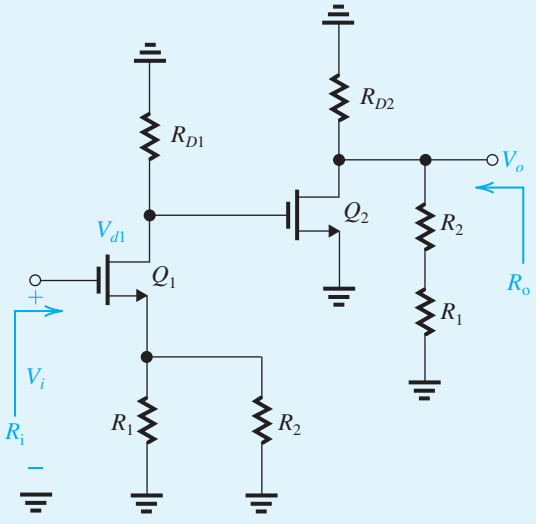

(b)

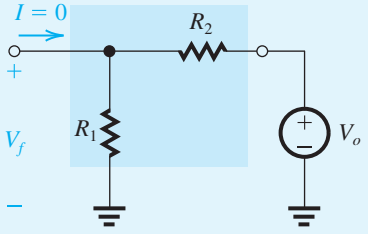

(c)

Figure 11.16 **(a)** Series–shunt feedback amplifier for Example 11.5; **(b)** the A circuit; **(c)** the β circuit.

Example 11.5 *continued*

Solution

We identify the feedback network as the voltage divider (R_1, R_2). Its loading effect at the input is obtained by short-circuiting its port 2 (because it is connected in shunt with the output). Then, looking into its port 1, we see $R_1 \| R_2$. The loading effect at the output is obtained by open-circuiting port 1 of the feedback network (because it is connected in series with the input). Then, looking into port 2, we see R_2 in series with R_1. The A circuit will therefore be as shown in Fig. 11.16(b). The gain A is determined as the product of the gain of Q_1 and the gain of Q_2 as follows:

$$A_1 = \frac{V_{d1}}{V_i} = -\frac{R_{D1}}{1/g_{m1} + (R_1 \| R_2)} = -\frac{g_{m1}R_{D1}}{1 + g_{m1}(R_1 \| R_2)}$$

$$A_2 = \frac{V_o}{V_{d1}} = -g_{m2}\left[R_{D2} \| (R_1 + R_2)\right]$$

$$A = \frac{V_o}{V_i} = A_1 A_2 = \frac{g_{m1}R_{D1}g_{m2}\left[R_{D2} \| (R_1 + R_2)\right]}{1 + g_{m1}(R_1 \| R_2)}$$

For the numerical values given,

$$A = \frac{4 \times 10 \times 4[10 \| (1+9)]}{1 + 4(1 \| 9)} = 173.9 \text{ V/V}$$

which is reasonably close to the value of 166.7 V/V obtained in Example 11.2.

The value of β is determined from the β circuit in Fig. 11.16(c),

$$\beta \equiv \frac{V_f}{V_o} = \frac{R_1}{R_1 + R_2}$$

For the numerical values given,

$$\beta = \frac{1}{1+9} = 0.1$$

The closed-loop gain V_o/V_s can now be found as

$$\frac{V_o}{V_s} = A_f = \frac{A}{1 + A\beta} = \frac{173.9}{1 + 173.9 \times 0.1} = 9.46 \text{ V/V}$$

which is very close to the value of 9.43 V/V obtained in Example 11.2.

The input resistance is obviously infinite because of the infinite input resistance of the MOSFET. The output resistance R_{out} is obtained as follows,

$$R_{\text{out}} = R_{of} = \frac{R_o}{1 + A\beta}$$

where R_o is the output resistance of the A circuit. From Fig. 11.16(b),

$$R_o = R_{D2} \| (R_1 + R_2)$$
$$= 10 \| 10 = 5\,\text{k}\Omega$$

The amount of feedback is

$$1 + A\beta = 1 + (173.9 \times 0.1) = 18.39$$

Thus,

$$R_{\text{out}} = \frac{5000}{18.39} = 272\ \Omega$$

which is relatively low given that the open-loop amplifier has $R_o = 5000\ \Omega$. We finally note that the loop-gain method utilized in Example 11.2 cannot provide the input and output resistances because the A circuit is not determined.

EXERCISES

11.7 If the op amp of Example 11.4 has a uniform –6-dB/octave high-frequency rolloff with $f_{3\text{dB}} = 1$ kHz, find the 3-dB frequency of the closed-loop gain V_o/V_s.
Ans. 7 kHz

11.8 The circuit shown in Fig. E11.18 consists of a differential stage followed by an emitter follower, with series–shunt feedback supplied by the resistors R_1 and R_2. Assuming that the dc component of V_s is zero, and that β of the BJTs is very high, find the dc operating current of each of the three transistors and show that the dc voltage at the output is approximately zero. Then find the values of A, β, $A_f \equiv V_o/V_s$, R_{in}, and R_{out}. Assume that the transistors have $\beta = 100$.
Ans. 0.5 mA, 0.5 mA, 5 mA; 85.7 V/V; 0.1 V/V; 8.96 V/V; 191 kΩ; 19.1 Ω.

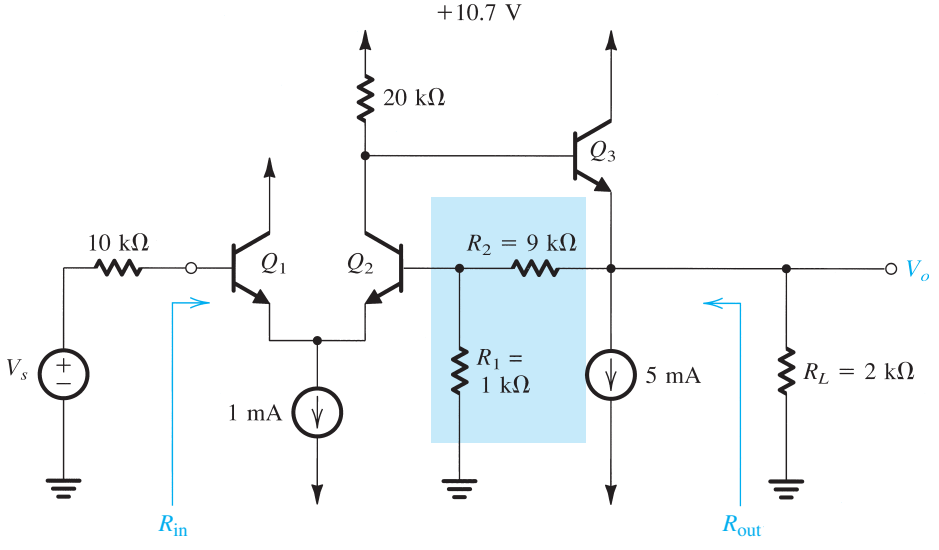


Figure E11.8

11.9 For the series–shunt amplifier in Fig. 11.8(c), which was considered in Exercise 11.6, find A, β, A_f, R_{in}, and R_{out}. Neglect r_o of Q. Compare results to those obtained in Exercise 11.6.

Ans. $A = g_m[R_D \parallel (R_1 + R_2)]$; $\beta = R_1/(R_1 + R_2)$;
$A_f = A/(1 + A\beta)$; $R_{in} = (1/g_m)(1 + A\beta)$;
$R_{out} = [R_D \parallel (R_1 + R_2)]/(1 + A\beta)$

Comparison: A and β are identical to the corresponding expressions found in Exercise 11.6. However, R_{in} and R_{out} cannot be determined using the method of Exercise 11.6.

11.5 Other Feedback-Amplifier Types

Having studied in detail the most common feedback-amplifier type, the feedback voltage amplifier, we now consider the three other types of feedback amplifier: the feedback transconductance amplifier, the feedback current amplifier, and the feedback transresistance amplifier. The presentation builds on that of the feedback voltage amplifier, and the results will be given without derivation. The analysis method will be illustrated with a large number of worked-out examples dealing with practical and widely utilized circuits.

11.5.1 Basic Principles

1. *Sensing:* The feedback network must sample the output signal of interest. Thus if V_o is the output signal of interest, as in the case of voltage and transresistance amplifiers, the feedback network is connected in parallel (or *shunt*) with the amplifier output node, just as a voltmeter is connected to measure a voltage. On the other hand, if I_o is the output signal of interest, as in the case of transconductance and current amplifiers, the feedback network is connected in *series* with the output loop, just as a current meter is connected to measure a current.
2. *Mixing:* If the input signal to be amplified is a voltage, as in the case of voltage and transconductance amplifiers, the signal source is represented by its Thévenin equivalent and the feedback voltage signal V_f is connected in *series* with the input signal source V_s. On the other hand, if the signal to be amplified is a current, as in the case of current and transresistance amplifiers, the Norton form is used to represent the signal source, and the feedback current signal I_f is connected in parallel (*shunt*) with the input signal source I_s.
3. *Feedback topology:* From the above, it follows that for each of the four amplifier types there is a uniquely appropriate feedback topology:

Amplifier Type	Appropriate Feedback Topology
Voltage	Series–Shunt
Transconductance	Series–Series
Current	Shunt–Series
Transresistance	Shunt–Shunt

The appropriate feedback topology not only stabilizes the gain of interest (e.g., the transconductance $A_f \equiv I_o/V_s$ in a transconductance amplifier), but also makes the input and output resistances more ideal (e.g., the shunt–series topology decreases the input resistance and increases the output resistance of a current amplifier).

4. *Input and output resistance:* The increase or decrease of the input or output resistance depends *solely* on the type of connection: Series connection always increases the resistance; parallel (shunt) connection always decreases the resistance. Furthermore, the increase or decrease is always by the amount of feedback, $(1 + A\beta)$. Thus, as an example, for the feedback current amplifier, the shunt connection at the input decreases the input resistance; $R_{if} = R_i/(1 + A\beta)$, and the series connection at the output increases the output resistance; $R_{of} = (1 + A\beta)R_o$, where R_i and R_o are the input and output resistances of the open-loop amplifier (A circuit).
5. *Dimensions of $A, \beta, A\beta$, and A_f:* Depending on the amplifier type, A, β, and A_f have the dimensions of V/V, A/A, V/A, or A/V. However, $A\beta$ is always dimensionless. For a feedback transconductance amplifier, for example, $A \equiv I_o/V_i$ (A/V), $\beta \equiv V_f/I_o$ (V/A), $A_f \equiv I_o/V_s$ (A/V), and $A\beta$ is in V/V or essentially dimensionless.
6. *Analysis using the loop gain:* For any feedback-amplifier type, the loop gain $A\beta$ can be determined using the method described in Section 11.3.3. The loop gain can then be used together with the feedback factor β to determine the open-loop gain A and hence the closed-loop gain A_f. This approach, however, does not enable the determination of the input and output resistances of the feedback amplifier. For these, we need to obtain the A circuit using the systematic analysis approach described below.

Example 11.6

Figure 11.17(a) shows a feedback transconductance amplifier utilizing an op amp together with an NMOS transistor. The feedback network consists of a resistor R_F that senses the output current I_o (recall that the drain and source currents of the MOSFET are equal) and provides a feedback voltage that is subtracted from V_s by means of the differencing action of the op-amp input. Observe that the feedback topology is series–series, which is uniquely appropriate for transconductance amplifiers.

(a) Find β and hence the closed-loop gain $A_f \equiv I_o/V_s$ obtained when $A\beta \gg 1$.
(b) Replace the op amp with its equivalent-circuit model characterized by an open-circuit voltage gain μ, an input differential resistance R_{id}, and an output resistance r_{o1}. Also, replace the MOSFET with its hybrid-π model characterized by a transconductance g_m and an output resistance r_{o2}. With the complete equivalent circuit in hand, set $V_s = 0$ and break the loop to determine $A\beta$.
(c) Use $A\beta$ together with β to find A.
(d) For $\mu = 1000$, $R_{id} = 100\ \text{k}\Omega$, $g_m = 2\ \text{mA/V}$, $r_{o2} = 20\ \text{k}\Omega$, and $R_F = 1\ \text{k}\Omega$, find the values of β, $A\beta$, A, and A_f. Compare A_f to the ideal value obtained when $A\beta \gg 1$.

Example 11.6 *continued*

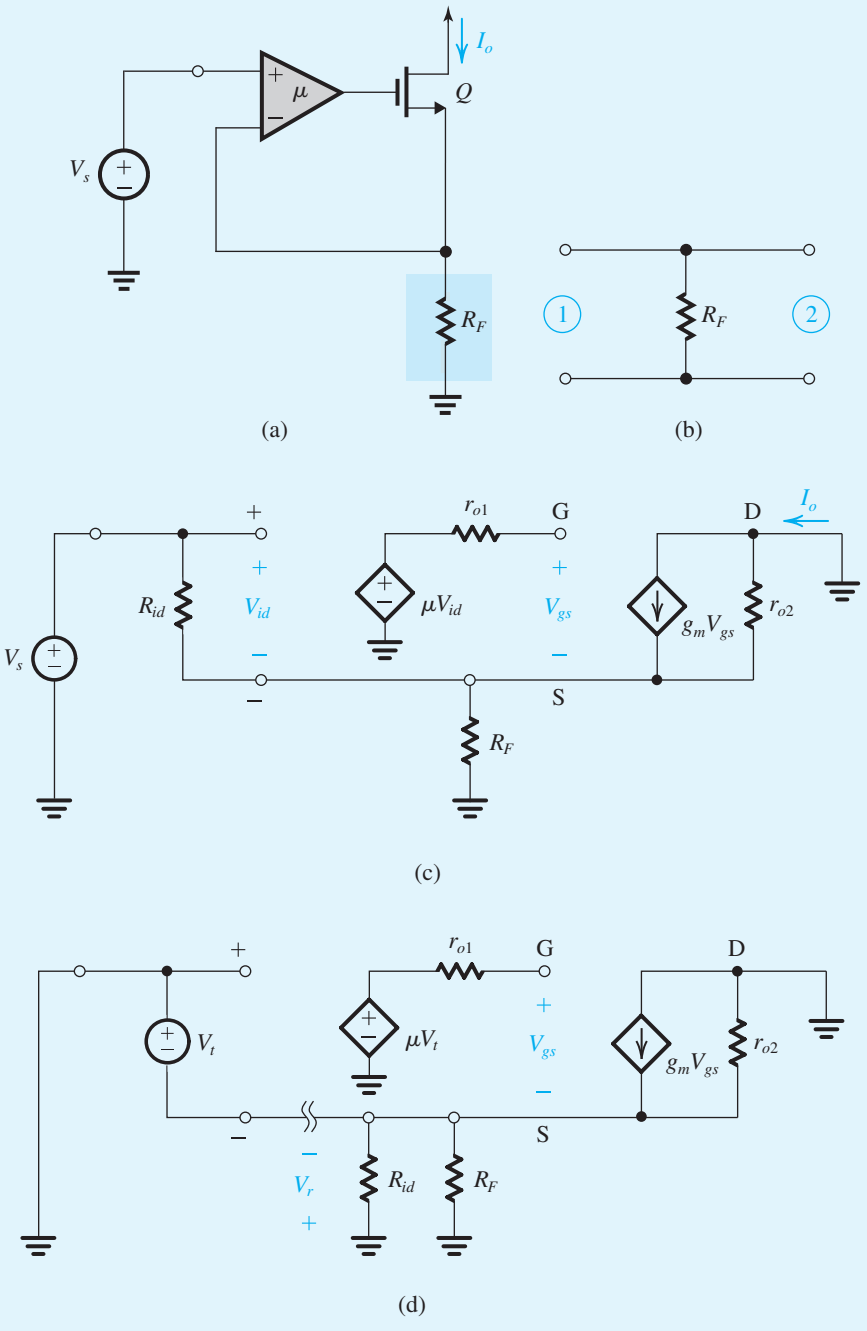


Figure 11.17 Example 11.6.

Solution

(a) The two-port feedback network is shown in Fig. 11.17(b). When port 2 is fed with a current I_o the voltage V_f appearing across port 1 is $I_o R_F$, thus

$$\beta = R_F$$

When $A\beta \gg 1$,

$$A_f \equiv \frac{I_o}{V_s} \simeq \frac{1}{\beta} = \frac{1}{R_F}$$

(b) Figure 11.7(c) shows the equivalent-circuit model of the feedback transconductance amplifier. To determine $A\beta$, we set $V_s = 0$ and break the loop at the input terminals of the op amp as shown in Fig. 11.17(d). Note that we have applied an input voltage V_t and terminated the loop at the break in the resistance R_{id} to prevent any change in the loop conditions. This circuit can be easily analyzed to determine $A\beta \equiv -V_r/V_t$ as follows:

$$V_{gs} = \mu V_t - (-V_r) = \mu V_t + V_r$$
$$-V_r = g_m V_{gs}(R_F \parallel R_{id} \parallel r_{o2})$$

Combining these two equations yields

$$A\beta \equiv -\frac{V_r}{V_t} = \mu \frac{g_m(R_F \parallel R_{id} \parallel r_{o2})}{1 + g_m(R_F \parallel R_{id} \parallel r_{o2})}$$

(c) Substituting $\beta = R_F$ provides

$$A = \frac{\mu}{R_F} \frac{g_m(R_F \parallel R_{id} \parallel r_{o2})}{1 + g_m(R_F \parallel R_{id} \parallel r_{o2})}$$

(d) For the given numerical values,

$$\beta = 1\ \text{k}\Omega$$
$$A\beta = 1000 \times \frac{2(1 \parallel 100 \parallel 20)}{1 + 2(1 \parallel 100 \parallel 20)}$$
$$= 653.6$$
$$A = 653.6\ \text{mA/V}$$
$$A_f \equiv \frac{I_o}{V_s} = \frac{653.6}{1 + 653.6} = 0.9985\ \text{mA/V}$$

Since the ideal value of A_f is 1 mA/V, the actual A_f is only 0.15% lower than ideal.

EXERCISES

11.10 For the circuit in Example 11.6, let the op-amp gain decrease by 10%. What is the corresponding percentage change in $A_f \equiv I_o/V_s$?
Ans. -0.02%

D11.11 Redesign the circuit in Example 11.6 to obtain a nominal closed-loop transconductance of 2 mA/V. What is the required value of R_F, and what is the actual transconductance A_f realized?
Ans. $R_F = 500\ \Omega$; $A_f = 1.996$ mA/V


11.5.2 The Feedback Transconductance Amplifier (Series–Series)

Figure 11.18(a) shows the ideal structure of the feedback transconductance amplifier. The open-loop amplifier (A circuit) is unilateral, has an input resistance R_i, a short-circuit transconductance gain A in A/V, and an output resistance R_o. The short-circuit output current $I_o = AV_i$ is sensed by the feedback network. Note that since the resistance looking into port 2 of the feedback network is zero, the feedback network does not load the amplifier output. The feedback network provides at port 1 a voltage signal $V_f = \beta I_o$, where the feedback factor β has the dimensions of V/A. The feedback signal is connected in series with the input signal source V_s, and the feedback network does not load the amplifier input. Finally, note the definitions of the input resistance with feedback, R_{if}, and the output resistance with feedback, R_{of}. The latter is the resistance found by looking into the output loop between any two nodes such as O and O'.


The equivalent circuit of the feedback transconductance amplifier is shown in Fig. 11.18(b). Note that the closed-loop gain A_f is the ratio of the short-circuit output current I_o and the input voltage V_s, thus it is the short-circuit transconductance of the feedback amplifier. Also, R_{of} is the resistance seen between any two nodes in the output loop, such as O and O', while V_s is set to zero. Finally, Fig. 11.18(c) provides the formulas for determining A_f, R_{if}, and R_{of}.

With the ideal case in hand, we now consider the general or practical case of a feedback transconductance amplifier, shown in Fig. 11.19(a). To be able to apply feedback analysis to this circuit, we have to find the A circuit and β. These are shown in Fig. 11.19(b). The A circuit is obtained by augmenting the basic amplifier with R_s and R_L and the two resistances R_{11} and R_{22}, which represent the loading effect of the feedback network on the basic amplifier at the input and output, respectively. Figure 11.19(b) shows how R_{11} and R_{22} are determined. Here, the series connection at both the input and the output means that the other port of the feedback network must be left open-circuited. This is also the case when β is determined.

(a) Ideal Structure

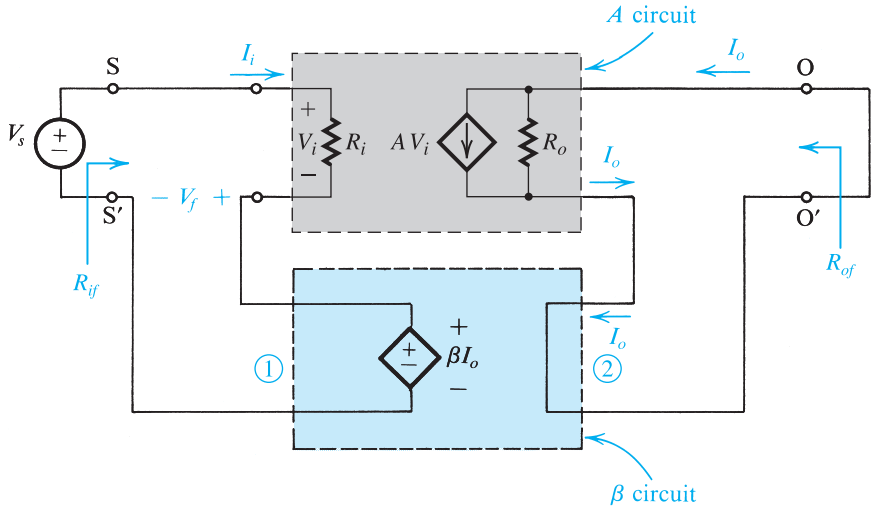

(b) Equivalent Circuit

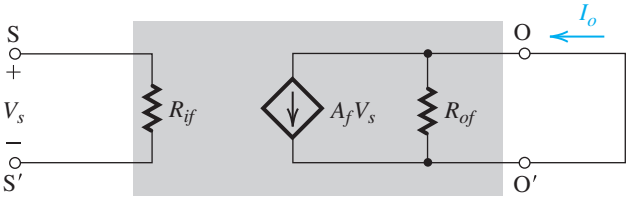

(c) Formulas

$$A_f = \frac{I_o}{V_s} = \frac{A}{1+A\beta}$$


$$R_{if} = (1+A\beta)R_i$$

$$R_{of} = (1+A\beta)R_o$$

Figure 11.18 The feedback transconductance amplifier (series–series).


Finally Fig. 11.19(c) gives the formulas for determining the actual values of the input and output resistances, R_{in} and R_{out}, of the feedback amplifier from R_{if} and R_{of}. To see how these formulas come about, note from Fig. 11.19(a) that unlike R_{if}, R_{in} does not include R_s, and unlike R_{of}, R_{out} does not include R_L.

(a) General Structure

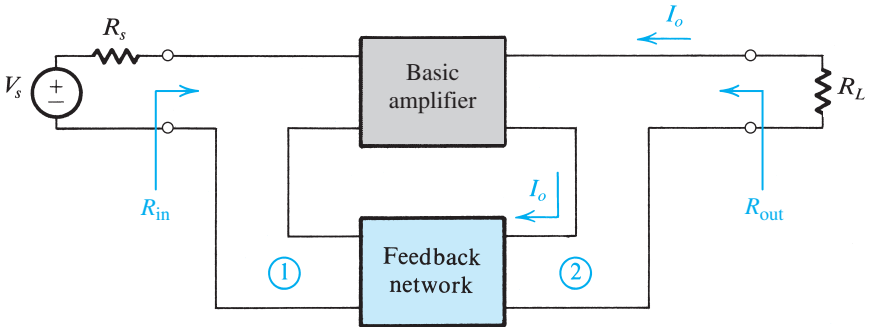


(b) Finding the A Circuit and β


(i) The A circuit is

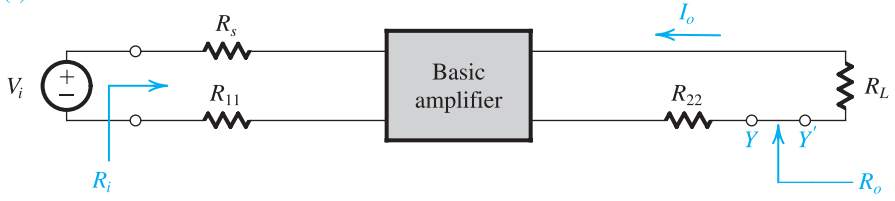

where R_{11} is obtained from

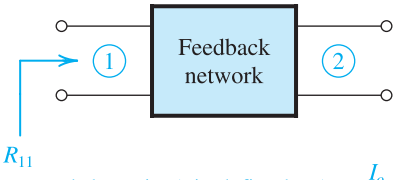


and R_{22} is obtained from

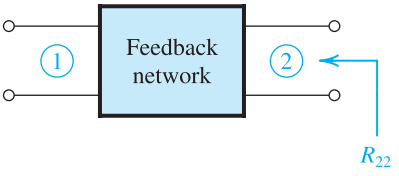

and the gain A is defined $A \equiv \dfrac{I_o}{V_i}$

(ii) β is obtained from

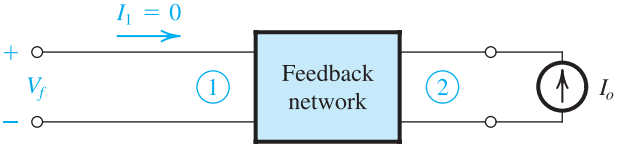

$$\beta \equiv \left.\frac{V_f}{I_o}\right|_{I_1 = 0}$$

(c) Gain, Input, and Output Resistance

- Use the formulas in Fig. 11.18 to find A_f, R_{if}, and R_{of}.
- R_{in} and R_{out} can then be found from

$$R_{\text{in}} = R_{if} - R_s$$
$$R_{\text{out}} = R_{of} - R_L$$

Figure 11.19 The feedback transconductance amplifier (series–series).

Example 11.7

Figure 11.20(a) shows a feedback transconductance amplifier composed of a differential amplifier A_1 with an input differential resistance R_{id}, an open-circuit voltage gain A_1, and an output resistance R_{o1}, connected in cascade with a common source MOSFET Q_2 having a transconductance g_{m2} and an output resistance r_{o2}. Use the feedback-analysis method to determine the closed-loop transconductance $A_f \equiv I_o/V_s$, the input resistance R_{in}, and the output resistance R_{out}. The latter is the resistance seen between the terminals of R_L, looking back into the output loop.

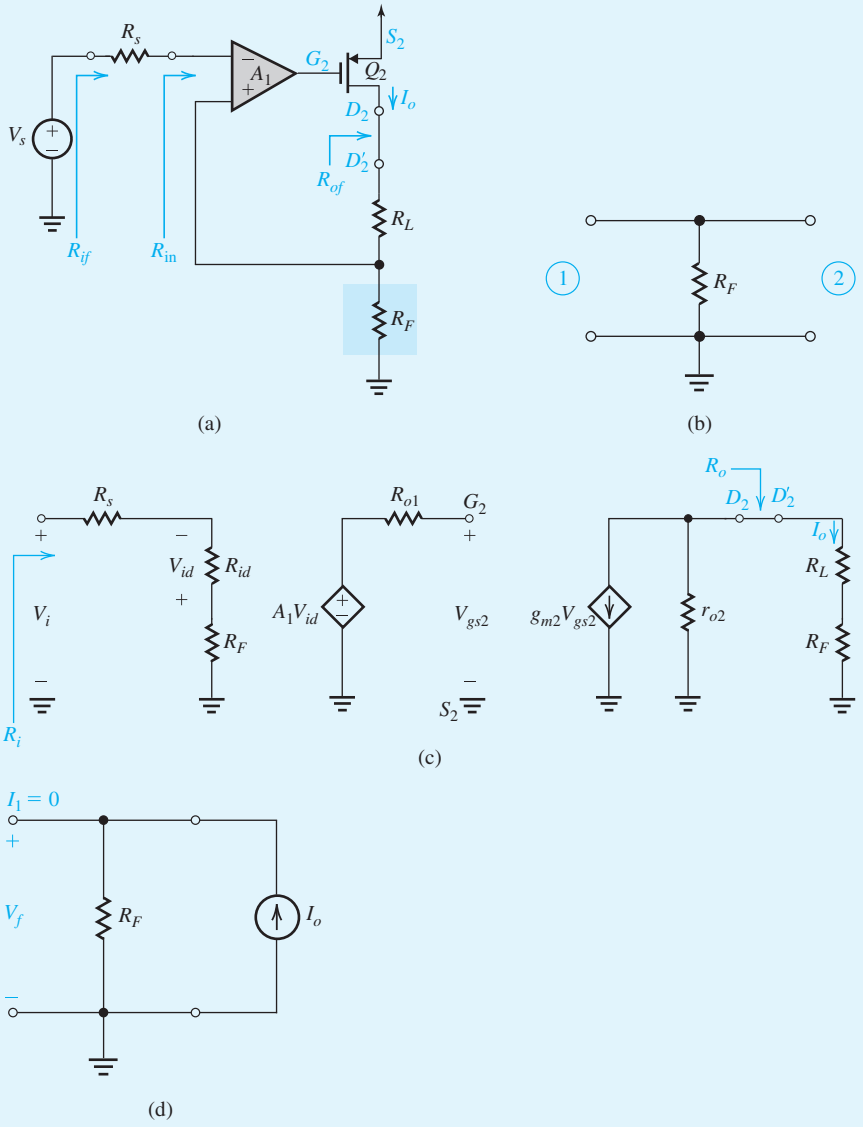


Figure 11.20 Circuits for Example 11.7.

Example 11.7 *continued*

Solution

First we identify the basic amplifier and the feedback circuit. The basic amplifier consists of the differential amplifier A_1 cascaded with the CS PMOS transistor Q_2. The output current I_o is sensed by the series resistance R_F. The latter is the feedback network (Fig. 11.20b). It develops a voltage V_f that is mixed in series with the input loop.

The second step is to ascertain that the feedback is negative. This can be done by assuming an increase in V_s and following the resulting change around the loop. An increase in V_s will cause the voltage at the inverting input terminal of A_1 to increase. This in turn causes a decrease in the output voltage of A_1, which is the voltage at the gate of Q_2. Thus, transistor Q_2 will have a larger V_{SG}, which will cause I_o to increase. This in turn causes an increase in the voltage across R_F, which is the same polarity as the change in V_s. Thus, the feedback is indeed negative.

Next, we determine an approximate value for $A_f \equiv I_o/V_s$ under the assumption that the loop gain $A\beta$ is much greater than unity. This value, found before any analysis is undertaken, will help us determine at the end whether our analysis is correct: If the loop gain is found to be much greater than unity, then the final A_f should be close to the value initially determined. From the circuit of Fig. 11.20(d),

$$\beta = R_F$$

and thus for large $A\beta$,

$$A_f \simeq \frac{1}{\beta} = \frac{1}{R_F}$$

Next, we determine the A circuit. Since the feedback network (Fig. 11.20b) is connected in series with both the input and output loops, we include a resistance R_F in each of these loops (which is equivalent to saying we include, at the input, the input resistance of the feedback circuit with port 2 open and, at the output, the input resistance of the feedback circuit with port 1 open). Doing this, including R_s and R_L in the A circuit, and replacing A_1 and Q_2 with their small-signal models, results in the A circuit shown in Fig. 11.20(c). Analysis of this circuit is straightforward:

$$V_{id} = -V_i \frac{R_{id}}{R_{id} + R_s + R_F} \tag{11.27}$$

$$V_{gs2} = A_1 V_{id} \tag{11.28}$$

$$I_o = -g_{m2} V_{gs2} \frac{r_{o2}}{r_{o2} + R_L + R_F} \tag{11.29}$$

Combining these three equations results in

$$A \equiv \frac{I_o}{V_i} = (A_1 g_{m2}) \left(\frac{R_{id}}{R_{id} + R_s + R_F} \right) \left(\frac{r_{o2}}{r_{o2} + R_L + R_F} \right) \tag{11.30}$$

Usually $R_{id} \gg (R_s + R_F)$, $r_{o2} \gg (R_L + R_F)$, resulting in the approximate expression for A:

$$A \simeq A_1 g_{m2} \tag{11.31}$$

The input resistance R_i can be found by inspection as

$$R_i = R_s + R_{id} + R_F \tag{11.32}$$

The output resistance R_o is found by setting $V_i = 0$, and breaking the output loop at any location, say between D_2 and D_2'. Thus,

$$R_o = r_{o2} + R_L + R_F \tag{11.33}$$

The loop gain $A\beta$ is thus

$$A\beta = (A_1 g_{m2} R_F)\left(\frac{R_{id}}{R_{id} + R_s + R_F}\right)\left(\frac{r_{o2}}{r_{o2} + R_L + R_F}\right) \tag{11.34}$$

$$\simeq A_1 g_{m2} R_F \tag{11.35}$$

With numerical values, one can now obtain the value of $A\beta$ and determine whether it is indeed much greater than unity. We next determine the closed-loop gain

$$A_f = \frac{A}{1 + A\beta}$$

Substituting for A from Eq. (11.31) and for $A\beta$ from Eq. (11.35), we have

$$A_f \simeq \frac{A_1 g_{m2}}{1 + A_1 g_{m2} R_F} \tag{11.36}$$

For $A_1 g_{m2} R_F \gg 1$,

$$A_f \simeq \frac{1}{R_F}$$

which is the value we found at the outset.

The series mixing raises the input resistance with feedback,

$$R_{if} = R_i(1 + A\beta)$$

and R_{in} can be obtained by subtracting R_s from R_{if}.

To obtain R_{of}, we note that the series connection at the output raises the output resistance, thus,

$$R_{of} = R_o(1 + A\beta)$$

and R_{out}, which is the resistance seen by R_L, can be obtained by subtracting R_L from R_{of}.

EXERCISES

D11.12 For the circuit analyzed in Example 11.7, select a value for R_F that will result in $A_f \simeq 5$ mA/V. Now, for $A_1 = 200$ V/V, $g_{m2} = 2$ mA/V, $R_{id} = 100$ kΩ, $r_{o2} = 20$ kΩ, and assuming that $R_s \ll R_{id}$ and $R_L \ll r_{o2}$, find the value of A_f realized and the input and output resistances of the feedback transconductance amplifier. If for some reason g_{m2} drops in value by 50%, what is the corresponding percentage change in A_f?

Ans. 200 Ω; 4.94 mA/V; 8.1 MΩ; 1.64 MΩ; −1.25%

11.13 Determine the loop gain of the feedback amplifier of Fig. 11.20(a) by setting $V_s = 0$, breaking the feedback loop at G_2, applying a voltage V_{g2}, and determining the voltage V_{o1} that appears at the output of A_1; $A\beta \equiv -V_{o1}/V_{g2}$. Assume $R_F \ll (R_{id} + R_s)$ and $r_{o2} \gg R_L + R_F$.

Ans. $A\beta \simeq A_1 g_{m2} R_F$

11.14 Utilizing the full expression for $A\beta$ in Eq. (11.34) but assuming that $r_{o2} \gg R_L + R_F$ and $R_F \ll R_{id}$, show that

$$R_{\text{in}} \simeq R_{id}(1 + A_1 g_{m2} R_F)$$

11.15 Utilizing the full expression for $A\beta$ in Eq. (11.34) but assuming that $R_{id} \gg R_s + R_F$ and $R_F \ll r_{o2}$ show that


$$R_{\text{out}} \simeq r_{o2}(1 + A_1 g_{m2} R_F)$$

Example 11.8


Because negative feedback extends the amplifier bandwidth, it is commonly used in the design of broadband amplifiers. One such amplifier is the MC1553. Part of the circuit of the MC1553 is shown in Fig. 11.21(a). The circuit shown (called a **feedback triple**) is composed of three gain stages with series–series feedback provided by the network composed of R_{E1}, R_F, and R_{E2}.

Observe that the feedback network samples the emitter current I_o of Q_3, and thus I_o is the output quantity of the feedback amplifier. However, practically speaking, I_o is rather difficult to utilize. Thus it is usual to take as the output I_c, the collector current of Q_3. This current is of course almost equal to I_o; $I_c = \alpha I_o$. Thus, as a transconductance amplifier with I_c as the output current, the output resistance of interest is that labeled R_{out} in Fig. 11.21(a). In some applications, I_c is passed through a load resistance, such as R_{C3}, and the voltage V_o is taken as the output. Assume that the bias circuit, which is not shown, establishes $I_{C1} = 0.6$ mA, $I_{C2} = 1$ mA, and $I_{C3} = 4$ mA. Also assume that for all three transistors,[5] $h_{fe} = 100$ and $r_o = \infty$.

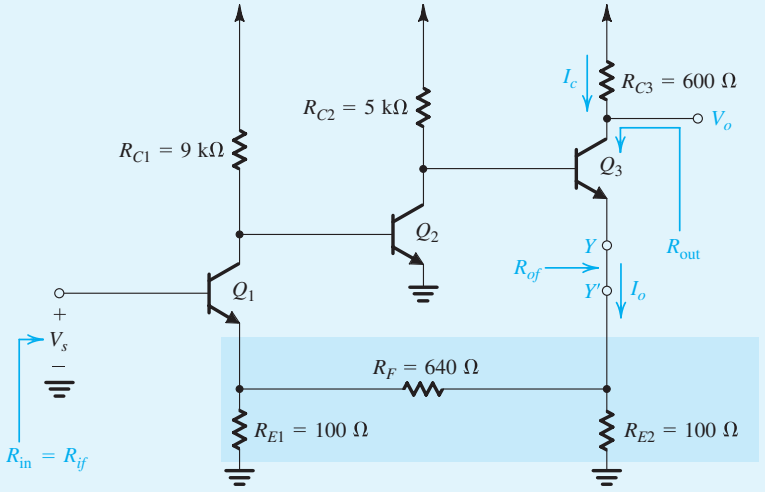
[5]To avoid possible confusion of the BJT current gain β and the feedback factor β, we sometimes use h_{fe} to denote the transistor β.




(a)

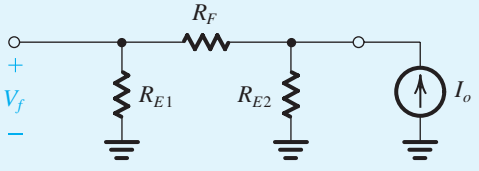

(b)

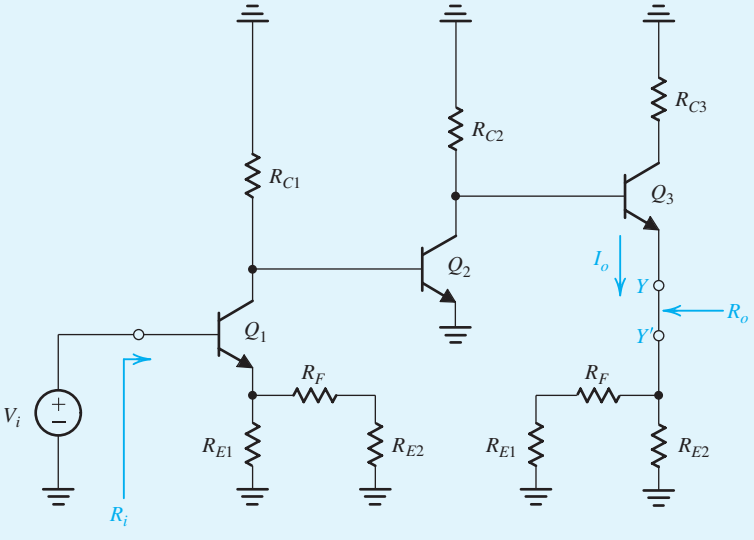

(c)

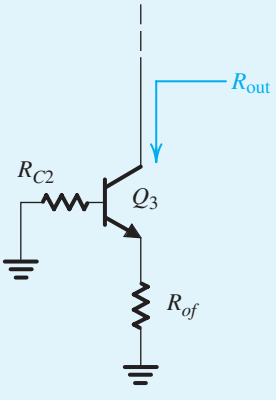

(d)

Figure 11.21 Circuits for Example 11.8.

Example 11.8 *continued*

(a) Anticipating that the loop gain will be large, find an approximate expression and value for the closed-loop gain $A_f \equiv I_o/V_s$ and hence for I_c/V_s. Also find V_o/V_s.
(b) Use feedback analysis to find A, β, A_f, V_o/V_s, R_{in}, and R_{out}. For the calculation of R_{out}, assume that r_o of Q_3 is 25 kΩ.

Solution

(a) When $A\beta \gg 1$,

$$A_f \equiv \frac{I_o}{V_s} \simeq \frac{1}{\beta}$$

where the feedback factor β can be found from the feedback network. The feedback network is highlighted in Fig. 11.21(a), and the determination of the value of β is illustrated in Fig. 11.21(b), from which we find

$$\beta \equiv \frac{V_f}{I_o} = \frac{R_{E2}}{R_{E2} + R_F + R_{E1}} \times R_{E1}$$
$$= \frac{100}{100 + 640 + 100} \times 100 = 11.9\ \Omega$$

Thus,

$$A_f \simeq \frac{1}{\beta}$$
$$= \frac{1}{R_{E2}}\left(1 + \frac{R_{E2} + R_F}{R_{E1}}\right)$$
$$= \frac{1}{11.9} = 84\ \text{mA/V}$$
$$\frac{I_c}{V_s} \simeq \frac{I_o}{V_s} = 84\ \text{mA/V}$$
$$\frac{V_o}{V_s} = \frac{-I_c R_{C3}}{V_s} = -84 \times 0.6 = -50.4\ \text{V/V}$$

(b) Employing the loading rules given in Fig. 11.19, we obtain the A circuit shown in Fig. 11.21(c). To find $A \equiv I_o/V_i$ we first determine the gain of the first stage. This can be written by inspection as

$$\frac{V_{c1}}{V_i} = \frac{-\alpha_1 (R_{C1} \parallel r_{\pi 2})}{r_{e1} + [R_{E1} \parallel (R_F + R_{E2})]}$$

Since Q_1 is biased at 0.6 mA, $r_{e1} = 41.7\ \Omega$. Transistor Q_2 is biased as 1 mA; thus $r_{\pi 2} = h_{fe}/g_{m2} = 100/40 = 2.5$ kΩ. Substituting these values together with $\alpha_1 = 0.99$, $R_{C1} = 9$ kΩ, $R_{E1} = 100\ \Omega$, $R_F = 640\ \Omega$, and $R_{E2} = 100\ \Omega$, results in

$$\frac{V_{c1}}{V_i} = -14.92\ \text{V/V}$$

Next, we determine the gain of the second stage, which can be written by inspection (noting that $V_{b2} = V_{c1}$) as

$$\frac{V_{c2}}{V_{c1}} = -g_{m2}\{R_{C2} \| (h_{fe}+1)[r_{e3} + (R_{E2} \| (R_F + R_{E1}))]\}$$

Substituting $g_{m2} = 40\,\text{mA/V}$, $R_{C2} = 5\,\text{k}\Omega$, $h_{fe} = 100$, $r_{e3} = 25/4 = 6.25\,\Omega$, $R_{E2} = 100\,\Omega$, $R_F = 640\,\Omega$, and $R_{E1} = 100\,\Omega$ results in

$$\frac{V_{c2}}{V_{c1}} = -131.2\ \text{V/V}$$

Finally, for the third stage we can write by inspection

$$\frac{I_o}{V_{c2}} = \frac{I_{e3}}{V_{b3}} = \frac{1}{r_{e3} + (R_{E2} \| (R_F + R_{E1}))}$$

$$= \frac{1}{6.25 + (100 \| 740)} = 10.6\ \text{mA/V}$$

Combining the gains of the three stages results in

$$A \equiv \frac{I_o}{V_i} = -14.92 \times -131.2 \times 10.6 \times 10^{-3}$$

$$= 20.7\ \text{A/V}$$

The closed-loop gain A_f can now be found from

$$A_f \equiv \frac{I_o}{V_s} = \frac{A}{1 + A\beta}$$

$$= \frac{20.7}{1 + 20.7 \times 11.9} = 83.7\ \text{mA/V}$$

which we note is very close to the ideal value found in (a) above. This is not surprising, since the loop gain $A\beta = 20.7 \times 11.9 = 246.3$ is large ($\gg 1$).

The voltage gain is found from

$$\frac{V_o}{V_s} = \frac{-I_c R_{C3}}{V_s} \simeq \frac{-I_o R_{C3}}{V_s} = -A_f R_{C3}$$

$$= -83.7 \times 10^{-3} \times 600 = -50.2\ \text{V/V}$$

which is also very close to the approximate value found in (a) above.

Example 11.8 *continued*

The input resistance of the feedback amplifier is given by

$$R_{\text{in}} = R_{if} = R_i(1 + A\beta)$$

where R_i is the input resistance of the A circuit. The value of R_i can be found from the circuit in Fig. 11.21(c) as follows:

$$\begin{aligned} R_i &= (h_{fe} + 1)\left[r_{e1} + \left(R_{E1} \parallel (R_F + R_{E2})\right)\right] \\ &= 13.11 \text{ k}\Omega \end{aligned}$$

Thus,

$$R_{if} = 13.11(1 + 20.7 \times 11.9) = 3.24\,\text{M}\Omega$$

To determine the output resistance R_{out}, which is the resistance looking into the collector of Q_3, we face a dilemma. The feedback does not sample I_c and thus we cannot employ the feedback formulas directly.[6] Nevertheless, we present a somewhat indirect solution to this problem below. Here we note parenthetically that had Q_1 been a MOSFET, this problem would not have existed, since $I_d = I_s$.

Since the feedback senses the emitter current I_o, the output resistance given by the feedback analysis will be the resistance seen in the emitter circuit, say between Y and Y',

$$R_{of} = R_o(1 + A\beta)$$

where R_o can be determined from the A circuit in Fig. 11.21(c) by breaking the circuit between Y and Y'. The resistance looking between these two nodes can be found to be

$$R_o = \left[R_{E2} \parallel (R_F + R_{E1})\right] + r_{e3} + \frac{R_{C2}}{h_{fe} + 1}$$

which, for the values given, yields $R_o = 143.9\,\Omega$. The output resistance R_{of} of the feedback amplifier can now be found as

$$R_{of} = R_o(1 + A\beta) = 143.9(1 + 20.7 \times 11.9) = 35.6 \text{ k}\Omega$$

[6] This important point was first brought to the authors' attention by Gordon Roberts (see Roberts and Sedra, 1992).

We can now use the value of R_{of} to obtain an approximate value for R_{out}. To do this, we assume that the effect of the feedback is to place a resistance R_{of} (35.6 kΩ) in the emitter of Q_3, and find the output resistance from the equivalent circuit shown in Fig. 11.21(d). This is the output resistance of a BJT with a resistance R_{of} in its emitter and a resistance R_{C2} in its base. The formula we have for this (Eq. 8.66) does not unfortunately account for a resistance in the base. The formula, however, can be modified (see Problem 11.54) to obtain

$$\begin{aligned} R_{\text{out}} &= r_{o3} + \left[R_{of} \| \left(r_{\pi 3} + R_{C2}\right)\right]\left[1 + g_{m3} r_{o3} \frac{r_{\pi 3}}{r_{\pi 3} + R_{C2}}\right] \\ &= 25 + [35.6 \| (0.625 + 5)]\left[1 + 160 \times 25 \times \frac{0.625}{0.625 + 5}\right] \\ &= 2.19\,\text{M}\Omega \end{aligned}$$

Thus R_{out} is increased (from r_{o3}) but not by $(1 + A\beta)$.

EXERCISES

D11.16 For the feedback triple in Fig. 11.21(a), analyzed in Example 11.8, modify the value of R_F to obtain a closed-loop transconductance I_o/V_s of approximately 100 mA/V. Assume that the loop gain remains large. What is the new value of R_F? For this value, what is the approximate value of the voltage gain if the output voltage is taken at the collector of Q_3?

Ans. 800 Ω; –60 V/V


11.17 Determine the loop gain of the feedback amplifier of Fig. 11.21(a). Set $V_s = 0$, break the loop between the collector of Q_1 and the base of Q_2, apply a voltage V_t to the base of Q_2, and connect a resistance equal to $r_{\pi 2}$ between the collector of Q_1 and ground. Find $A\beta$ as $(-V_r/V_t)$ where $V_r = V_{c1}$.

Ans. $A\beta = 248.9$ (slightly different from the value found in Example 11.8 because of the approximations inherent in the systematic feedback-analysis method).


11.5.3 The Feedback Transresistance Amplifier (Shunt–Shunt)

Figure 11.22(a) shows the ideal feedback transresistance amplifier, which, as expected, utilizes the shunt–shunt topology. The amplifier equivalent circuit is shown in Fig. 11.22(b), with the formulas for determining A_f, R_{if}, and R_{of} given in Fig. 11.22(c).

(a) Ideal Structure

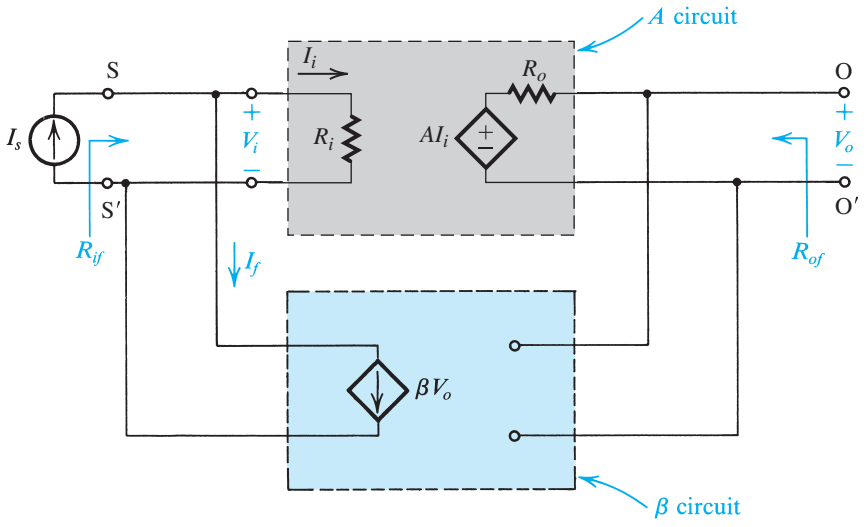

(b) Equivalent Circuit

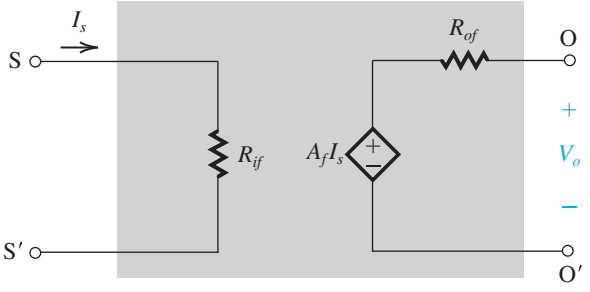

(c) Formulas

$$A_f \equiv \frac{V_o}{I_s} = \frac{A}{1 + A\beta}$$


$$R_{if} = R_i/(1 + A\beta)$$

$$R_{of} = R_o/(1 + A\beta)$$

Figure 11.22 The feedback transresistance amplifier (shunt–shunt).


Application of the feedback-analysis method to a general transresistance amplifier is shown in Fig. 11.23, which presents all the steps and formulas needed. The method is now illustrated by a detailed example.

(a) General Structure

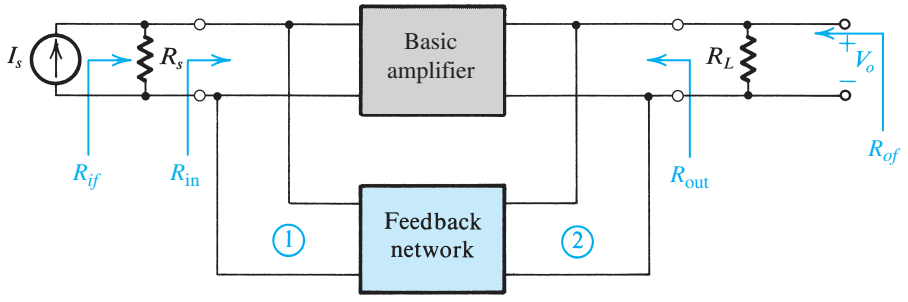


(b) Finding the A Circuit and β


(i) The A circuit is

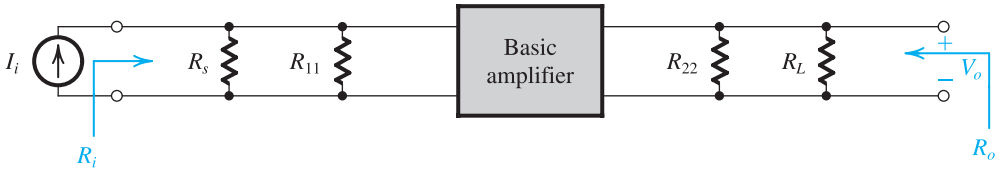

where R_{11} is obtained from

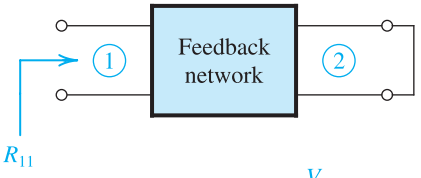


and R_{22} is obtained from

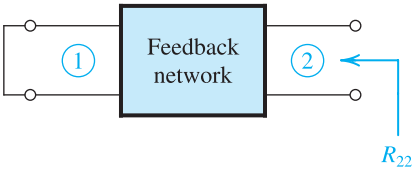

and the gain A is defined $A \equiv \dfrac{V_o}{I_i}$

(ii) β is obtained from

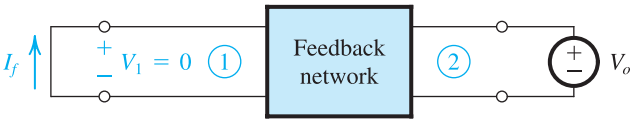

$$\beta \equiv \left.\frac{I_f}{V_o}\right|_{V_1 = 0}$$

(c) Gain, Input, and Output Resistance

- Use the formulas in Fig. 11.21 to find A_f, R_{if}, and R_{of}.
- R_{in} and R_{out} can then be found from

$$R_{\text{in}} = 1 \Big/ \left(\frac{1}{R_{if}} - \frac{1}{R_s}\right)$$

$$R_{\text{out}} = 1 \Big/ \left(\frac{1}{R_{of}} - \frac{1}{R_L}\right)$$

Figure 11.23 The feedback transresistance amplifier (shunt–shunt).

Example 11.9

Figure 11.24(a) shows a feedback transresistance amplifier. It is formed by connecting a resistance R_F in the negative-feedback path of a voltage amplifier with gain μ, an input resistance R_{id}, and an output resistance r_o. The amplifier μ can be implemented with an op amp, a simple differential amplifier, a single-ended inverting amplifier, or, in the limit, a single-transistor CE or CS amplifier. The latter case will be considered in Exercise 11.18. Of course, the higher the gain μ, the more ideal the characteristics of the feedback transresistance amplifier will be, simply because of the concomitant increase in loop gain.

(a) If the loop gain is large, find an approximate expression for the closed-loop transresistance V_o/I_s of the feedback amplifier.
(b) Find the A circuit and expressions for A, R_i, and R_o.
(c) Find expressions for the loop gain, A_f, R_{if}, R_{in}, R_{of}, and R_{out}.
(d) Find the values of R_i, R_o, A, β, $A\beta$, A_f, R_{if}, R_{in}, R_{of}, and R_{out} for the case $\mu = 10^4$ V/V, $R_{id} = \infty$, $r_o = 100\ \Omega$, $R_F = 10$ kΩ, and $R_s = R_L = 1$ kΩ.
(e) If instead of a current source I_s having a source resistance $R_s = 1$ kΩ, the amplifier is fed from a voltage source V_s having a source resistance $R_s = 1$ kΩ, find an expression for and the value of the voltage gain V_o/V_s.

Solution

(a) If the loop gain $A\beta$ is large,

$$A_f \equiv \frac{V_o}{I_s} \simeq \frac{1}{\beta}$$

where β can be found from the β circuit in Fig. 11.24(b) as shown in Fig. 11.24(c),

$$\beta \equiv \frac{I_f}{V_o} = -\frac{1}{R_F} \tag{11.37}$$

Thus,

$$\frac{V_o}{I_s} \simeq -R_F$$

Note that in this case the voltage at the input node (the inverting input terminal of μ) will be very close to ground and thus very little, if any, current flows into the input terminal of the amplifier. Nearly all of I_s will flow through R_F, resulting in $V_o \simeq 0 - I_s R_F = -I_s R_F$. This should be reminiscent of the inverting op-amp configuration studied in Section 2.2.

(b) From the feedback network in Fig. 11.24(b), we see that the loading effect at the amplifier input and output will simply be R_F. This is indicated in the A circuit shown in Fig. 11.24(c), where we have replaced the amplifier μ with its equivalent-circuit model. The open-loop transresistance A can be obtained as follows:

$$V_{id} = I_i R_i \tag{11.38}$$

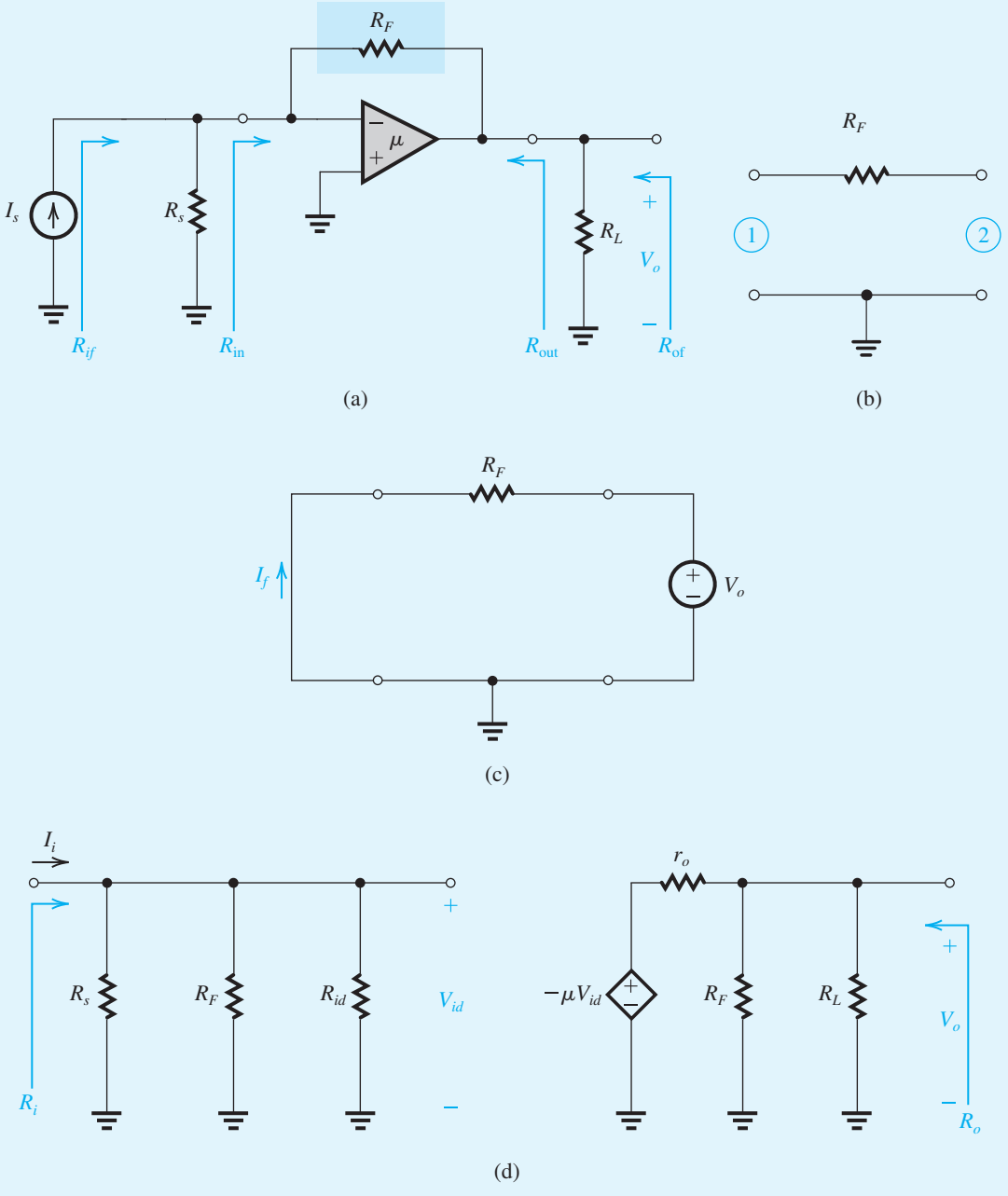


Figure 11.24 (**a**) A feedback transresistance amplifier; (**b**) the β circuit; (**c**) determining β; (**d**) the A circuit.

Example 11.9 *continued*

where

$$R_i = R_{id} \| R_F \| R_s \tag{11.39}$$

$$V_o = -\mu V_{id} \frac{(R_F \| R_L)}{r_o + (R_F \| R_L)} \tag{11.40}$$

Combining Eqs. (11.38) and (11.40) gives

$$A \equiv \frac{V_o}{I_i} = -\mu R_i \frac{(R_F \| R_L)}{r_o + (R_F \| R_L)} \tag{11.41}$$

The open-loop output resistance can be obtained by inspection of the A circuit with I_i set to 0. We see that $V_{id} = 0$, and

$$R_o = r_o \| R_F \| R_L \tag{11.42}$$

(c) The loop gain $A\beta$ can be obtained by combining Eqs. (11.37) and (11.41),

$$A\beta = \mu \left(\frac{R_i}{R_F} \right) \frac{(R_F \| R_L)}{r_o + (R_F \| R_L)} \tag{11.43}$$

Observe that although both A and β are negative, $A\beta$ is positive, a comforting fact confirming that the feedback is negative. Also note that $A\beta$ is dimensionless, as it must always be.

The closed-loop gain A_f can now be found as

$$A_f \equiv \frac{V_o}{I_s} = \frac{A}{1 + A\beta}$$

Thus

$$A_f = \frac{-\mu R_i \dfrac{(R_F \| R_L)}{r_o + (R_F \| R_L)}}{1 + \mu \dfrac{R_i}{R_F} \dfrac{(R_F \| R_L)}{r_o + (R_F \| R_L)}} \tag{11.44}$$

Note that the condition of $A\beta \gg 1$ that results in $A_f \simeq -R_F$ corresponds to

$$\mu \left(\frac{R_i}{R_F} \right) \frac{(R_F \| R_L)}{r_o + (R_F \| R_L)} \gg 1 \tag{11.45}$$

The input resistance with feedback, R_{if}, is obtained by dividing R_i by $(1+A\beta)$ with the result

$$R_{if} = \frac{R_i}{1+A\beta}$$

or

$$\frac{1}{R_{if}} = \frac{1}{R_i} + \frac{A\beta}{R_i} = \frac{1}{R_i} + \frac{\mu}{R_F}\frac{(R_F \parallel R_L)}{r_o + (R_F \parallel R_L)}$$

Substituting for R_i from Eq. (11.39) and replacing $\mu(R_F \parallel R_L)/[r_o + (R_F \parallel R_L)]$ by μ', where μ' is lower than but usually close to the value of μ, results in

$$R_{if} = R_{id} \parallel R_F \parallel R_s \parallel (R_F/\mu')$$

The two terms containing R_F can be combined,

$$R_{if} = R_s \parallel R_{id} \parallel [R_F/(\mu'+1)] \tag{11.46}$$

Since $R_{if} = R_s \parallel R_{\text{in}}$, we see that

$$R_{\text{in}} = R_{id} \parallel [R_F/(\mu'+1)]$$

Usually R_{id} is large and thus

$$R_{\text{in}} \simeq \frac{R_F}{\mu'+1} \simeq \frac{R_F}{\mu'} \tag{11.47}$$

from which we observe that for large amplifier gain μ, the input resistance will be low.

The output resistance with feedback R_{of} can be found by dividing R_o by $(1+A\beta)$:

$$R_{of} = \frac{R_o}{1+A\beta}$$

Thus,

$$\frac{1}{R_{of}} = \frac{1}{R_o} + \frac{A\beta}{R_o}$$

$$= \frac{1}{R_o} + \mu\frac{R_i}{R_F}\frac{(R_F \parallel R_L)}{r_o + (R_F \parallel R_L)}\frac{1}{R_o}$$

Example 11.9 *continued*

Substituting for R_o from Eq. (11.42),

$$\frac{1}{R_{of}} = \frac{1}{R_L} + \frac{1}{R_F} + \frac{1}{r_o} + \mu\frac{R_i}{R_F}\frac{1}{r_o}$$

$$= \frac{1}{R_L} + \frac{1}{R_F} + \frac{1}{r_o}\left(1 + \mu\frac{R_i}{R_F}\right)$$

Thus,

$$R_{of} = R_L \| R_F \| \frac{r_o}{1 + \mu\dfrac{R_i}{R_F}}$$

Since, moreover,

$$R_{of} = R_L \| R_{\text{out}}$$

we obtain for R_{out}

$$R_{\text{out}} = R_F \| \frac{r_o}{1 + \mu\dfrac{R_i}{R_F}}$$

Usually $R_F \gg r_o/\left[1 + \mu\left(R_i/R_F\right)\right]$; thus,

$$R_{\text{out}} \simeq \frac{r_o}{1 + \mu\dfrac{R_i}{R_F}} \simeq \left(\frac{R_F}{R_i}\right)\left(\frac{r_o}{\mu}\right)$$

from which we see that for large μ, the output resistance will be considerably reduced.
(d) For the numerical values given:

$$R_i = R_{id} \| R_F \| R_s$$

$$= \infty \| 10 \| 1 = 0.91 \text{ k}\Omega$$

$$R_o = r_o \| R_F \| R_s$$

$$= 0.1 \| 10 \| 1 = 90 \ \Omega$$

$$A = -\mu R_i \frac{\left(R_F \| R_L\right)}{r_o + \left(R_F \| R_L\right)}$$

$$= -10^4 \times 0.91 \times \frac{(10 \| 1)}{0.1 + (10 \| 1)} = -8198 \text{ k}\Omega$$

$$\beta = -\frac{1}{R_F} = -\frac{1}{10} = -0.1 \text{ mA/V}$$

$$A\beta = 819.8$$

$$1 + A\beta = 820.8$$

$$A_f = \frac{A}{1 + A\beta} = -\frac{8198}{820.8} = -9.99 \text{ k}\Omega$$

which is very close to the ideal value of $-R_F = -10$ kΩ.

$$R_{if} = \frac{R_i}{1 + A\beta} = \frac{910}{820.8} = 1.11 \ \Omega$$

$$R_{\text{in}} = \frac{1}{\frac{1}{R_{if}} - \frac{1}{R_i}} - \frac{1}{\frac{1}{1.11} - \frac{1}{1000}} \simeq 1.11 \ \Omega$$

which is very low, a highly desirable property. We also have

$$R_{of} = \frac{R_o}{1 + A\beta} = \frac{90}{820.8} = 0.11 \ \Omega$$

$$R_{\text{out}} = \frac{1}{\frac{1}{R_{of}} - \frac{1}{R_L}} = \frac{1}{\frac{1}{0.11} - \frac{1}{1000}} \simeq 0.11 \ \Omega$$

which as well is very low, another highly desirable property.

(e) If the amplifier is fed with a voltage source V_s having a resistance $R_s = 1$ kΩ, the output voltage can be found from

$$V_o = A_f I_s = A_f \frac{V_s}{R_s}$$

Thus,

$$\frac{V_o}{V_s} = \frac{A_f}{R_s} = \frac{9.99 \text{ k}\Omega}{1 \text{ k}\Omega} = -9.99 \text{ V/V}$$

EXERCISES

11.18 It is required to determine the loop gain of the amplifier of Fig. 11.24(a) directly. Set $I_s = 0$, replace the amplifier μ with its equivalent circuit, and break the loop at the amplifier input, ensuring that a resistance equal to R_{id} is connected across R_s. Show that

$$A\beta = \frac{\mu R_L (R_{id} \parallel R_s)}{r_o[R_L + R_F + (R_{id} \parallel R_s)] + R_L[R_F + (R_{id} \parallel R_s)]}$$

Evaluate $A\beta$ using the numerical values given in Example 11.9.

Ans. $A\beta = 819.7$

11.19 For the transresistance amplifier in Fig. E11.19, replace the MOSFET with its small-signal equivalent-circuit model and use feedback analysis to show the following:

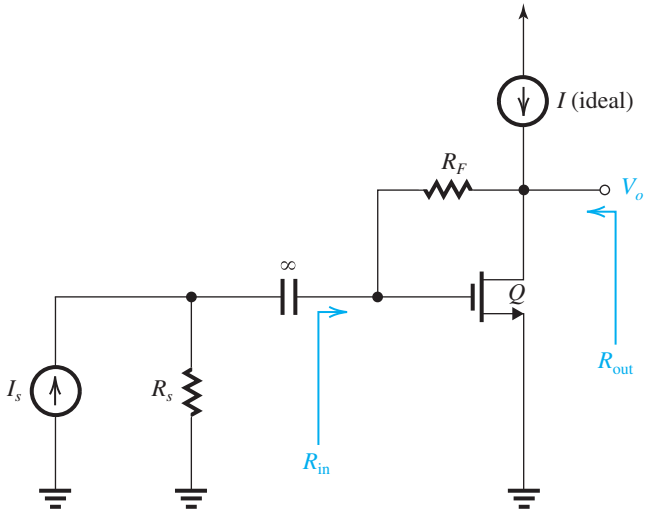


Figure E11.19

(a) For large loop gain (which cannot be achieved here), $A_f \equiv V_o/I_s \simeq -R_F$.

(b) $A_f = \dfrac{-(R_s \parallel R_F) g_m (r_o \parallel R_F)}{1 + (R_s \parallel R_F) g_m (r_o \parallel R_F)/R_F}$

(c) $R_{in} = \dfrac{R_F}{[1 + g_m (r_o \parallel R_F)]}$

(d) $R_{out} = r_o \parallel \dfrac{R_F}{1 + g_m (R_s \parallel R_F)}$

(e) For $g_m = 5$ mA/V, $r_o = 20$ kΩ, $R_F = 10$ kΩ, and $R_s = 1$ kΩ, find A, β, $A\beta$, A_f R_i, R_o, R_{if}, R_{in}, R_{of}, and R_{out}.


Ans. (e) −30.3 kΩ; −0.1 mA/V; 3.03; −7.52 kΩ (compare to the ideal value of −10 kΩ); 909 Ω; 6.67 kΩ; 226 Ω; 291 Ω; 1.66 kΩ; 1.66 kΩ

11.5.4 The Feedback Current Amplifier (Shunt–Series)


Figure 11.25(a) shows the ideal feedback current amplifier, which, as expected, utilizes the shunt–series topology. The amplifier equivalent circuit is shown in Fig. 11.25(b), with the formulas for determining A_f, R_{if}, and R_{of} given in Fig. 11.25(c).

Figure 11.26 shows how the feedback-analysis method can be applied to a general feedback current amplifier. All the necessary analysis steps and the formulas are given. The method is now illustrated by a detailed example.

(a) Ideal Structure

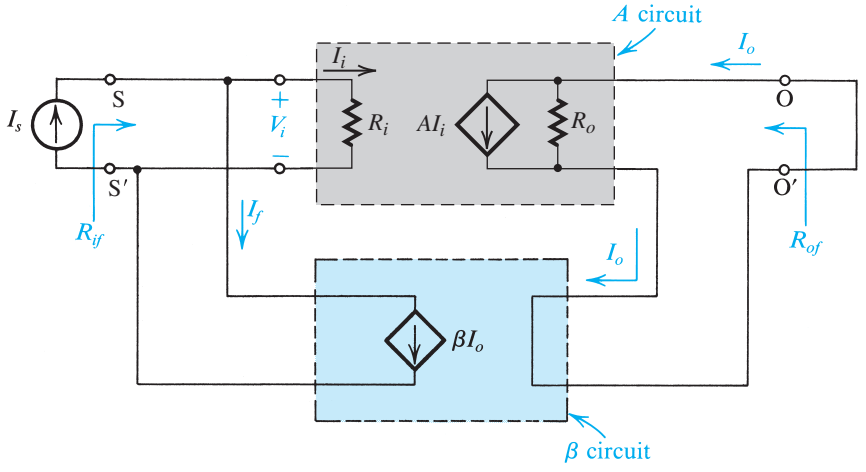

(b) Equivalent Circuit

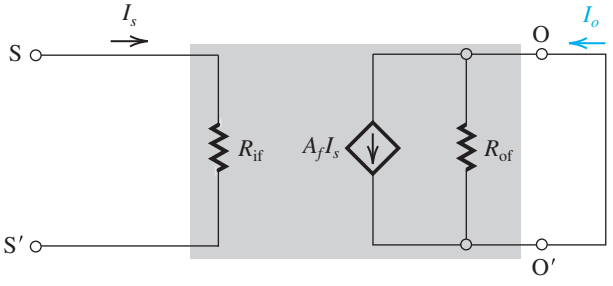

(c) Formulas


$$A_f \equiv \frac{I_o}{I_s} = \frac{A}{1+A\beta}$$

$$R_{if} = R_i/(1+A\beta)$$

$$R_{of} = (1+A\beta)R_o$$


Figure 11.25 The feedback current amplifier (shunt–series).

(a) General Structure

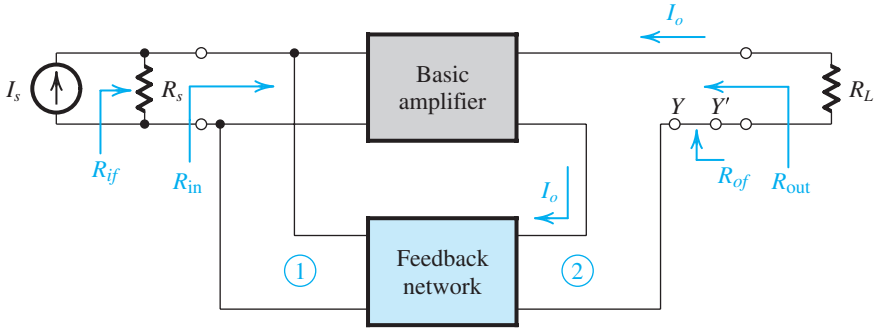


(b) Finding the A Circuit and β


(i) The A circuit is

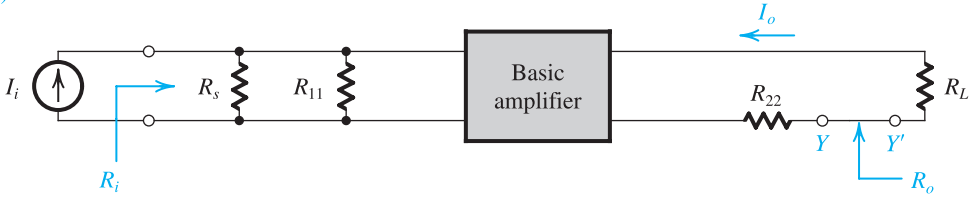

where R_{11} is obtained from

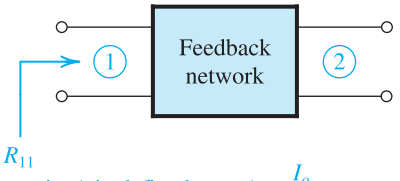


and R_{22} is obtained from

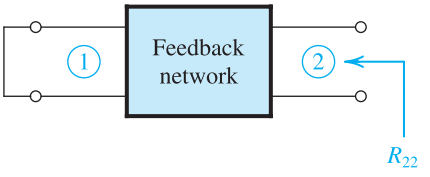

and the gain A is defined as $A \equiv \dfrac{I_o}{I_i}$

(ii) β is obtained from

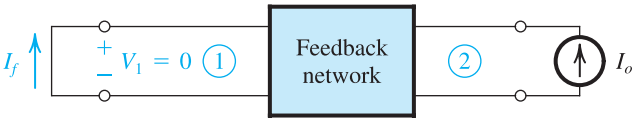

$$\beta \equiv \left.\frac{I_f}{I_o}\right|_{V_1 = 0}$$

(c) Gain, Input, and Output Resistance

- Use the formulas in Fig. 11.25 to find A_f, R_{if}, and R_{of}.
- R_{in} and R_{out} can then be found from

$$R_{\text{in}} = 1 \Big/ \left(\frac{1}{R_{if}} - \frac{1}{R_s}\right)$$

$$R_{\text{out}} = R_{of} - R_L$$

Figure 11.26 The feedback current amplifier (shunt–series).

Example 11.10

Figure 11.27 shows a feedback current amplifier formed by cascading an inverting voltage amplifier μ with a MOSFET Q. The output current I_o is the drain current of Q. The feedback network, consisting of resistors R_1 and R_2, senses an exactly equal current, namely, the source current of Q, and provides a feedback current signal that is mixed with I_s at the input node. Note that the bias arrangement is *not* shown.

The amplifier μ can be implemented in a variety of ways, including by means of an op amp, a differential amplifier, or a single-ended inverting amplifier. The simplest approach is to implement μ with a CS

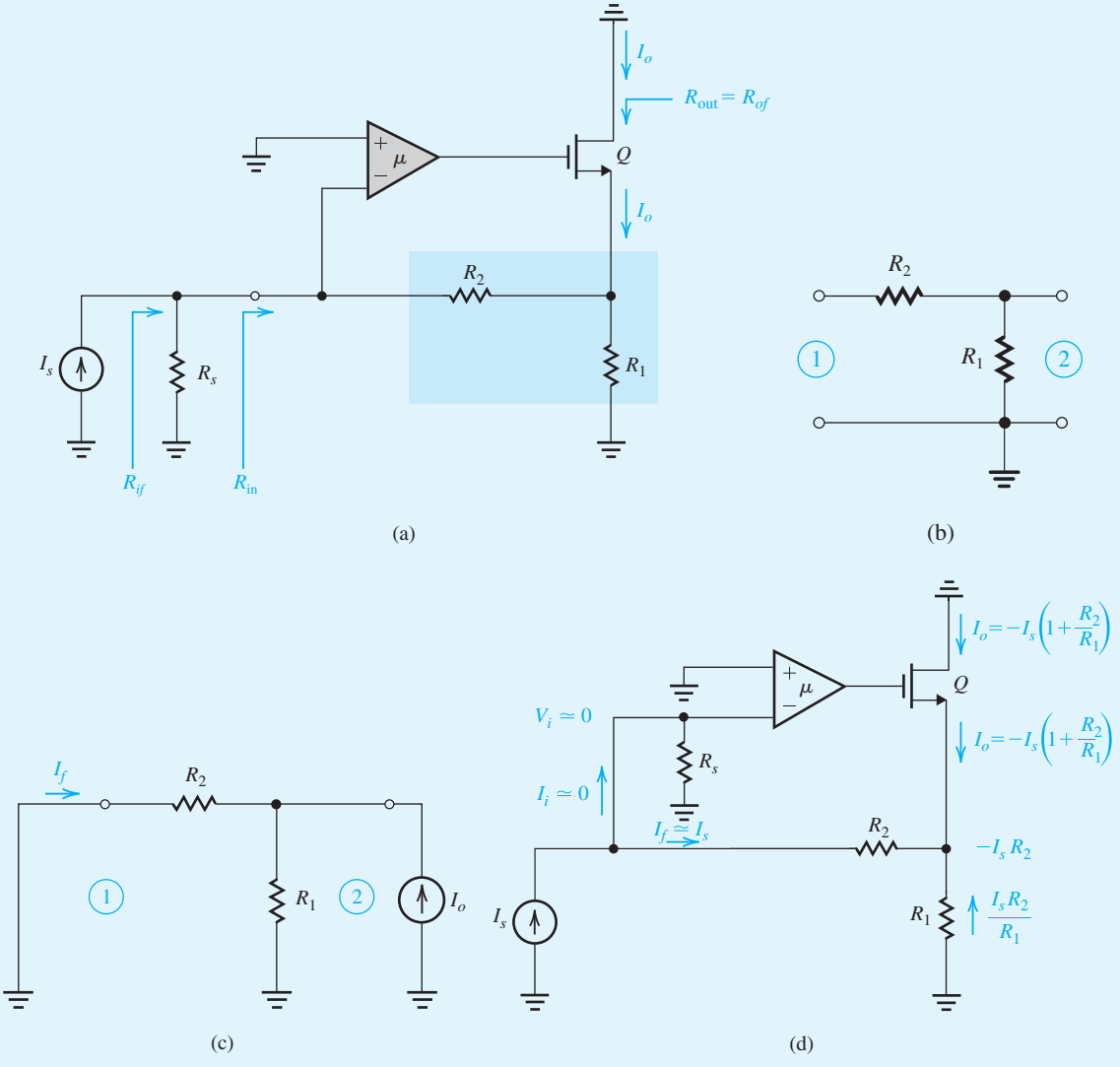


Figure 11.27 Circuit for Example 11.10.

Example 11.10 *continued*

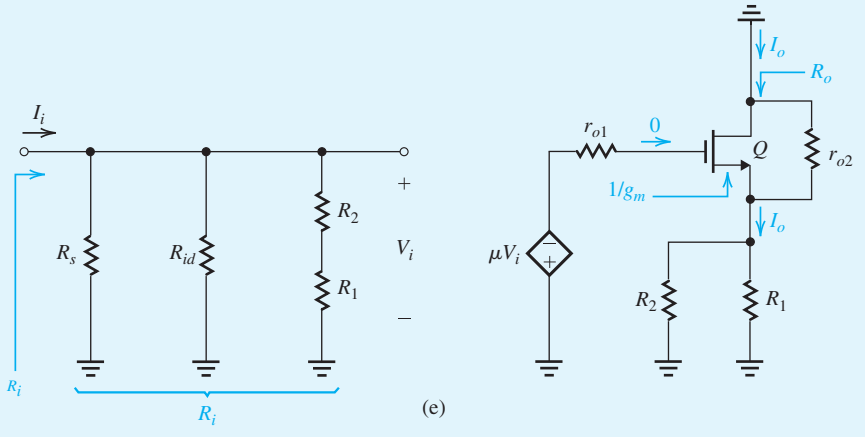


Figure 11.27 *continued*

MOSFET amplifier. However, in such a case the loop gain will be very limited. Assume that the amplifier μ has an input resistance R_{id}, an open-circuit voltage gain μ, and an output resistance r_{o1}.

(a) If the loop gain is large, find an approximate expression for the closed-loop gain $A_f \equiv I_o/I_s$.
(b) Find the A circuit and derive expressions for A, R_i, and R_o.
(c) Give expressions for $A\beta$, A_f, R_{if}, R_{in}, R_{of}, and R_{out}.
(d) Find numerical values for A, β, $A\beta$, A_f, R_i, R_{if}, R_{in}, R_o, R_{of}, and R_{out} for the following case: $\mu = 1000$ V/V, $R_s = \infty$, $R_{id} = \infty$, $r_{o1} = 1$ kΩ, $R_1 = 10$ kΩ, $R_2 = 90$ kΩ; for Q: $g_m = 5$ mA/V and $r_o = 20$ kΩ.

Solution

(a) When the loop gain $A\beta \gg 1$, $A_f \simeq 1/\beta$. The β circuit, shown in Fig. 11.27(b), is used to determine β as shown in Fig. 11.27(c),

$$\beta \equiv \frac{I_f}{I_o} = -\frac{R_1}{R_1 + R_2} \tag{11.48}$$

Thus,

$$A_f \simeq \frac{1}{\beta} = -\left(1 + \frac{R_2}{R_1}\right) \tag{11.49}$$

To see what happens in this case more clearly, refer to Fig. 11.27(d). Here we have assumed the loop gain to be large, so that $I_i \simeq 0$ and thus $I_f \simeq I_s$. Also note that because $I_i \simeq 0$, V_i will be close to zero. Thus, we can easily determine the voltage at the source of Q as $-I_f R_2 \simeq -I_s R_2$. The current through R_1 will then be $I_s R_2/R_1$. The source current of Q will be $-\left(I_s + I_s R_2/R_1\right)$, which means that the output current I_o will be

$$I_o = -I_s\left(1 + \frac{R_2}{R_1}\right)$$

which confirms the expression for A_f obtained above (Eq. 11.49).

(b) To obtain the A circuit we load the input side of the basic amplifier with R_s and R_{11}. The latter in this case is simply $R_1 + R_2$ (because port 2 of the feedback network is opened). We also load the output of the basic amplifier with R_{22}, which in this case is $R_1 \| R_2$ (because port 1 of the feedback network is shorted). The resulting A circuit is shown in Fig. 11.27(e), where we have replaced the amplifier μ with its equivalent circuit. Analysis of the A circuit is straightforward and proceeds as follows:

$$R_i = R_s \| R_{id} \| \left(R_1 + R_2\right) \tag{11.50}$$

$$V_i = I_i R_i \tag{11.51}$$

$$I_o = -\mu V_i \frac{1}{1/g_m + \left(R_1 \| R_2 \| r_{o2}\right)} \frac{r_{o2}}{r_{o2} + \left(R_1 \| R_2\right)} \tag{11.52}$$

Combining Eqs. (11.51) and (11.52) results in A:

$$A \equiv \frac{I_o}{I_i} = -\mu \frac{R_i}{1/g_m + \left(R_1 \| R_2 \| r_{o2}\right)} \frac{r_{o2}}{r_{o2} + \left(R_1 \| R_2\right)} \tag{11.53}$$

which with some manipulation can be expressed in the form

$$A = -\mu \frac{R_i}{(R_1 \| R_2)} \frac{(R_1 \| R_2 \| r_{o2})}{1/g_m + (R_1 \| R_2 \| r_{o2})} \tag{11.54}$$

Noting that R_o is the output resistance of Q, which has a resistance $(R_1 \| R_2)$ in its source lead, we can write

$$R_o = r_{o2} + (R_1 \| R_2) + \left(g_m r_{o2}\right)(R_1 \| R_2) \tag{11.55}$$

(c) The loop gain is obtained by combining Eqs. (11.48) and (11.53),

$$A\beta = \mu \frac{R_i}{R_2} \frac{(R_1 \| R_2 \| r_{o2})}{1/g_m + (R_1 \| R_2 \| r_{o2})} \tag{11.56}$$

The closed-loop gain A_f can be obtained by substituting the expressions of A and $A\beta$ (Eqs. 11.54 and 11.56) in $A_f = A/(1 + A\beta)$.

The input resistance R_{if} is found as

$$R_{if} = R_i/(1 + A\beta)$$

Since by definition,

$$R_{if} = R_s \| R_{\text{in}}$$

we can easily find R_{in}.

For the output resistance, we have

$$R_{\text{out}} = R_{of} = R_o(1 + A\beta)$$

(d) For the numerical values given,

$$R_i = \infty \| \infty \| (10 + 90) = 100 \text{ k}\Omega$$

Example 11.10 *continued*

The open-loop gain A can be determined by using Eq. (11.54),

$$A = -10,764 \text{ A/A}$$

and the feedback factor β can be found by using Eq. (11.48),

$$\beta = -\frac{R_1}{R_1 + R_2} = -\frac{10}{10 + 90} = -0.1 \text{ A/A}$$

Thus,

$$A\beta = 1076.4$$

and

$$A_f = -\frac{10,764}{1 + 1076.4} = -9.99 \text{ A/A}$$

which is very close to the ideal value of

$$A_f \simeq -\left(1 + \frac{R_2}{R_1}\right) = -\left(1 + \frac{90}{10}\right) = -10 \text{ A/A}$$

$$R_{if} = \frac{R_i}{1 + A\beta} = \frac{100 \text{ k}\Omega}{1 + 1076.4} = 92.8 \ \Omega$$

since $R_s = \infty$,

$$R_{\text{in}} = R_{if} = 92.8 \ \Omega$$

$$R_o = r_{o2} + (R_1 \parallel R_2) + g_m r_{o2}(R_1 \parallel R_2) = 929 \text{ k}\Omega$$

$$R_{\text{out}} = R_{of} = (1 + A\beta)R_o = 1077.4 \times 929 = 1001 \text{ M}\Omega$$

EXERCISES

11.20 For the amplifier in Example 11.10, find the values of A_f, R_{in}, and R_{out} when the value of μ is 10 times lower, that is, when $\mu = 100$.

Ans. -9.91 A/A; 920 Ω; 101 MΩ

11.21 If in the circuit in Fig. 11.27(a), R_2 is short-circuited, find the ideal value of A_f. For the case $R_s = R_{id} = \infty$, give expressions for R_i, R_o, A, β, A_f, R_{in}, and R_{out}.

Ans. $A_f = -1$ A/A; $R_i = R_1$; $R_o = r_{o2}$, $A = -\mu g_m R_1$; $\beta = -1$; $A_f = -\mu g_m R_1/(1 + \mu g_m R_1)$; $R_{\text{in}} \simeq 1/\mu g_m$; $R_{\text{out}} \simeq \mu(g_m r_{o2})R_1$.

11.6 Summary of the Feedback-Analysis Method

Table 11.2 provides a summary of the rules and relationships employed in the analysis and design of the four types of feedback amplifier. In addition to the wealth of information in Table 11.2, we offer the following important analysis tips.

1. Always begin the analysis by determining an approximate value for the closed-loop gain A_f, assuming that the loop gain $A\beta$ is large and thus

$$A_f \simeq 1/\beta$$

This value should serve as a check on the final value you find for A_f. How close the actual A_f is to this ideal value will depend on how large $A\beta$ is compared to unity.

2. The shunt connection at input or output always results in reducing the corresponding resistance (input or output). The series connection at input or output always results in increasing the corresponding resistance (input or output).
3. In utilizing negative feedback to improve the properties of an amplifier under design, the starting point in the design is the selection of the feedback topology appropriate for the application at hand. Then the required amount of negative feedback $(1 + A\beta)$ can be ascertained utilizing the fact that it is this quantity that determines the magnitude of improvement in the various amplifier parameters. Also, the feedback factor β can be determined from the required closed-loop gain A_f,

$$\beta \simeq 1/A_f$$

11.7 The Stability Problem

11.7.1 Transfer Function of the Feedback Amplifier

In a feedback amplifier such as that represented by the general structure of Fig. 11.1, the open-loop gain A is generally a function of frequency, and it should therefore be more accurately called the **open-loop transfer function**, $A(s)$. Also, we have been assuming for the most part that the feedback network is resistive and hence that the feedback factor β is constant, but this need not be always the case. We shall therefore assume that in the general case the **feedback transfer function** is $\beta(s)$. It follows that the **closed-loop transfer function** $A_f(s)$ is given by

$$A_f(s) = \frac{A(s)}{1 + A(s)\beta(s)} \tag{11.57}$$

To focus attention on the points central to our discussion in this section, we shall assume that the amplifier is direct coupled with constant dc gain A_0 and with poles and zeros occurring in the high-frequency band. Also, for the time being let us assume that at low frequencies $\beta(s)$ reduces to a constant value. Thus at low frequencies the loop gain $A(s)\beta(s)$ becomes a constant, which should be a positive number; otherwise the feedback would not be negative. The question then is: What happens at higher frequencies?

Table 11.2 Summary of Relationships for the Four Feedback-Amplifier Topologies

Feedback Amplifier	Feedback Topology	x_i	x_o	x_f	x_s	A	β	A_f	Source Form	Loading of Feedback Network Is Obtained: At Input	Loading of Feedback Network Is Obtained: At Output	To Find β, Apply to Port 2 of Feedback Network	R_{if}	R_{of}	Refer to Figs.
Voltage	Series–shunt	V_i	V_o	V_f	V_s	$\frac{V_o}{V_i}$	$\frac{V_f}{V_o}$	$\frac{V_o}{V_s}$	Thévenin	By short-circuiting port 2 of feedback network	By open-circuiting port 1 of feedback network	a voltage, and find the open-circuit voltage at port 1	$R_i(1+A\beta)$	$\frac{R_o}{1+A\beta}$	11.12 11.14
Current	Shunt–series	I_i	I_o	I_f	I_s	$\frac{I_o}{I_i}$	$\frac{I_f}{I_o}$	$\frac{I_o}{I_s}$	Norton	By open-circuiting port 2 of feedback network	By short-circuiting port 1 of feedback network	a current, and find the short-circuit current at port 1	$\frac{R_i}{1+A\beta}$	$R_o(1+A\beta)$	11.25 11.26
Transconductance	Series–series	V_i	I_o	V_f	V_s	$\frac{I_o}{V_i}$	$\frac{V_f}{I_o}$	$\frac{I_o}{V_s}$	Thévenin	By open-circuiting port 2 of feedback network	By open-circuiting port 1 of feedback network	a current, and find the open-circuit voltage at port 1	$R_i(1+A\beta)$	$R_o(1+A\beta)$	11.18 11.19
Transresistance	Shunt–shunt	I_i	V_o	I_f	I_s	$\frac{V_o}{I_i}$	$\frac{I_f}{V_o}$	$\frac{V_o}{I_s}$	Norton	By short-circuiting port 2 of feedback network	By short-circuiting port 1 of feedback network	a voltage, and find the short-circuit current at port 1	$\frac{R_i}{1+A\beta}$	$\frac{R_o}{1+A\beta}$	11.22 11.23

For physical frequencies $s = j\omega$, Eq. (11.57) becomes

$$A_f(j\omega) = \frac{A(j\omega)}{1 + A(j\omega)\beta(j\omega)} \tag{11.58}$$

Thus the loop gain $A(j\omega)\beta(j\omega)$ is a complex number that can be represented by its magnitude and phase,

$$\begin{aligned} L(j\omega) &\equiv A(j\omega)\beta(j\omega) \\ &= |A(j\omega)\beta(j\omega)|e^{j\phi(\omega)} \end{aligned} \tag{11.59}$$

It is the manner in which the loop gain varies with frequency that determines the stability or instability of the feedback amplifier. To appreciate this fact, consider the frequency at which the phase angle $\phi(\omega)$ becomes 180°. At this frequency, ω_{180}, the loop gain $A(j\omega)\beta(j\omega)$ will be a real number with a negative sign. Thus at this frequency the feedback will become positive. If at $\omega = \omega_{180}$ the magnitude of the loop gain is less than unity, then from Eq. (11.58) we see that the closed-loop gain $A_f(j\omega)$ will be greater than the open-loop gain $A(j\omega)$, since the denominator of Eq. (11.58) will be smaller than unity. Nevertheless, the feedback amplifier will be stable.

On the other hand, if at the frequency ω_{180} the magnitude of the loop gain is equal to unity, it follows from Eq. (11.58) that $A_f(j\omega)$ will be infinite. This means that the amplifier will have an output for zero input; this is by definition an **oscillator**. To visualize how this feedback loop may oscillate, consider the general loop of Fig. 11.1 with the external input x_s set to zero. Any disturbance in the circuit, such as the closure of the power-supply switch, will generate a signal $x_i(t)$ at the input to the amplifier. Such a noise signal usually contains a wide range of frequencies, and we shall now concentrate on the component with frequency $\omega = \omega_{180}$, that is, the signal $X_i \sin(\omega_{180}t)$. This input signal will result in a feedback signal given by

$$X_f = A(j\omega_{180})\beta(j\omega_{180})X_i = -X_i$$

Since X_f is further multiplied by –1 in the summer block at the input, we see that the feedback causes the signal X_i at the amplifier input to be *sustained*. That is, from this point on, there will be sinusoidal signals at the amplifier input and output of frequency ω_{180}. Thus the amplifier is said to oscillate at the frequency ω_{180}.

The question now is: What happens if at ω_{180} the magnitude of the loop gain is greater than unity? We shall answer this question, not in general, but for the restricted yet very important class of circuits in which we are interested here. The answer, which is not obvious from Eq. (11.58), is that the circuit will oscillate, and the oscillations will grow in amplitude until some nonlinearity (which is always present in some form) reduces the magnitude of the loop gain to exactly unity, at which point sustained oscillations will be obtained. This mechanism for starting oscillations by using positive feedback with a loop gain greater than unity, and then using a nonlinearity to reduce the loop gain to unity at the desired amplitude, will be exploited in the design of sinusoidal oscillators in Chapter 18. Our objective here is just the opposite: Now that we know how oscillations could occur in a negative-feedback amplifier, we wish to find methods to prevent their occurrence.

11.7.2 The Nyquist Plot

The Nyquist plot is a formalized approach for testing for stability based on the discussion above. It is simply a polar plot of loop gain, with frequency used as a parameter. Figure 11.28

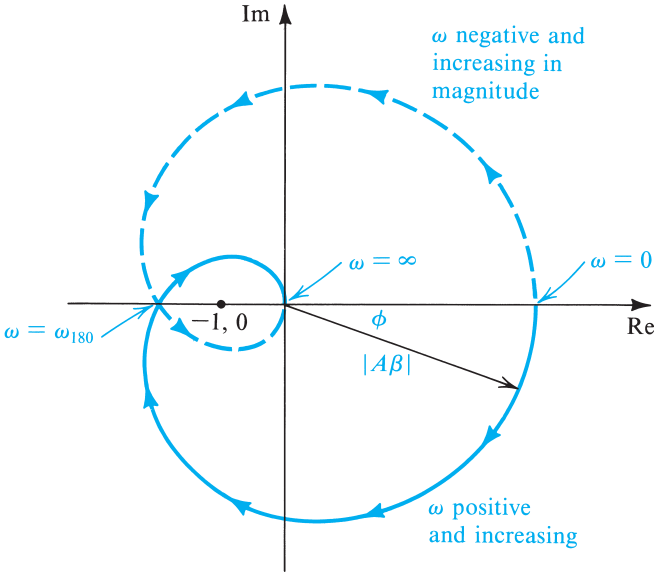


Figure 11.28 The Nyquist plot of an unstable amplifier.

shows such a plot. Note that the radial distance is $|A\beta|$ and the angle is the phase angle ϕ. The solid-line plot is for positive frequencies. Since the loop gain—and for that matter any gain function of a physical network—has a magnitude that is an even function of frequency and a phase that is an odd function of frequency, the $A\beta$ plot for negative frequencies (shown in Fig. 11.28 as a broken line) can be drawn as a mirror image through the Re axis.

The Nyquist plot intersects the negative real axis at the frequency ω_{180}. Thus, if this intersection occurs to the left of the point (–1, 0), we know that the magnitude of loop gain at this frequency is greater than unity and the amplifier will be unstable. On the other hand, if the intersection occurs to the right of the point (–1, 0) the amplifier will be stable. It follows that if the Nyquist plot *encircles* the point (–1, 0) then the amplifier will be unstable. It should be mentioned, however, that this statement is a simplified version of the **Nyquist criterion**; nevertheless, it applies to all the circuits in which we are interested. For the full theory behind the Nyquist method and for details of its application, consult Haykin (1970).

EXERCISE

11.22 Consider a feedback amplifier for which the open-loop transfer function $A(s)$ is given by

$$A(s) = \left(\frac{10}{1 + s/10^4}\right)^3$$

Let the feedback factor β be a constant independent of frequency. Find the frequency ω_{180} at which the phase shift is 180°. Then, show that the feedback amplifier will be stable if the feedback

factor β is less than a critical value β_{cr} and unstable if $\beta \geq \beta_{cr}$, and find the value of β_{cr}. Hence, find the minimum value of the closed-loop gain for which the amplifier is stable.

Ans. $\omega_{180} = \sqrt{3} \times 10^4$ rad/s; $\beta_{cr} = 0.008$; $A_{f\,min} = 111.1$

HARRY NYQUIST—A DIVERSE ELECTRONICS FUNDAMENTALIST:

Harry Nyquist, a Swedish-born electrical engineer working for Bell Labs and its predecessor, was responsible for developments in communications electronics involving thermal noise, feedback-amplifier stability, telegraphy, facsimile, television, and many other areas.

In *The Idea Factory*, an excellent book on the history of Bell Labs, Jon Gertner notes that

> [S]ome lawyers in the patent office of the Bell Labs decided to study whether there was an organizing principle that could explain why certain individuals were more productive than others. They discerned only one common thread: Workers with the most patents often shared lunch or breakfast with a Bell Labs electrical engineer named Harry Nyquist. It wasn't the case that Nyquist gave them specific ideas. Rather, as one scientist recalled, "he drew people out, got them thinking." More than anything, Nyquist asked good questions.

11.8 Effect of Feedback on the Amplifier Poles

The amplifier frequency response and stability are determined directly by its poles. Therefore we shall investigate the effect of feedback on the poles of the amplifier.[7]

11.8.1 Stability and Pole Location

We shall begin by considering the relationship between stability and pole location. For an amplifier or any other system to be stable, its poles should lie in the left half of the s plane. A pair of complex-conjugate poles on the $j\omega$ axis gives rise to sustained sinusoidal oscillations. Poles in the right half of the s plane give rise to growing oscillations.

To verify the statement above, consider an amplifier with a pole pair at $s = \sigma_0 \pm j\omega_n$. If this amplifier is subjected to a disturbance, such as that caused by closure of the power-supply switch, its transient response will contain terms of the form

$$v(t) = e^{\sigma_0 t}\left[e^{+j\omega_n t} + e^{-j\omega_n t}\right] = 2e^{\sigma_0 t}\cos(\omega_n t) \tag{11.60}$$

This is a sinusoidal signal with an envelope $e^{\sigma_0 t}$. Now if the poles are in the left half of the s plane, then σ_0 will be negative and the oscillations will decay exponentially toward zero, as shown in Fig. 11.29(a), indicating that the system is stable. If, on the other hand, the poles are in

[7] For a brief review of poles and zeros and related concepts, refer to Appendix F.

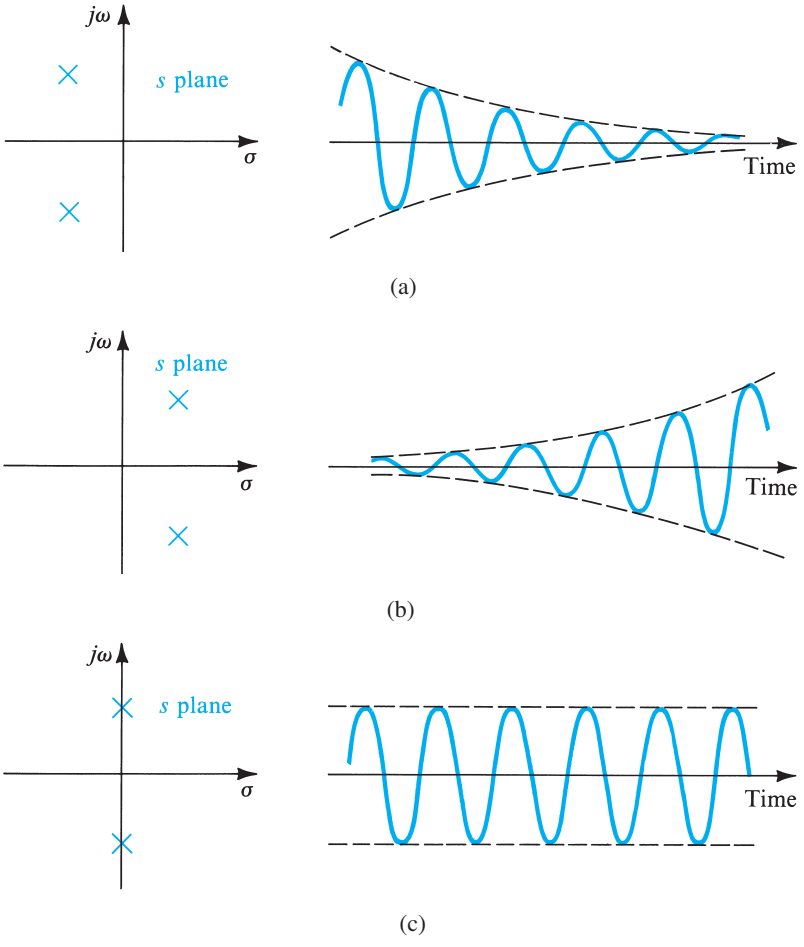


Figure 11.29 Relationship between pole location and transient response.

the right half-plane, then σ_0 will be positive, and the oscillations will grow exponentially (until some nonlinearity limits their growth), as shown in Fig. 11.29(b). Finally, if the poles are on the $j\omega$ axis, then σ_0 will be zero and the oscillations will be sustained, as shown in Fig. 11.29(c).

Although the discussion above is in terms of complex-conjugate poles, it can be shown that the existence of any right-half-plane poles results in instability.

11.8.2 Poles of the Feedback Amplifier

From the closed-loop transfer function in Eq. (11.57), we see that the poles of the feedback amplifier are the zeros of $1 + A(s)\beta(s)$. That is, the feedback amplifier poles are obtained by solving the equation

$$1 + A(s)\beta(s) = 0 \tag{11.61}$$

which is called the **characteristic equation** of the feedback loop. It should therefore be apparent that applying feedback to an amplifier changes its poles.

In the following, we shall consider how feedback affects the amplifier poles. For this purpose we shall assume that the open-loop amplifier has real poles and no finite zeros (i.e., all the zeros are at $s = \infty$). This will simplify the analysis and enable us to focus our attention on the fundamental concepts involved. We shall also assume that the feedback factor β is independent of frequency.

11.8.3 Amplifier with a Single-Pole Response

Consider first the case of an amplifier whose open-loop transfer function is characterized by a single pole:

$$A(s) = \frac{A_0}{1 + s/\omega_P} \tag{11.62}$$

The closed-loop transfer function is given by

$$A_f(s) = \frac{A_0/(1 + A_0\beta)}{1 + s/\omega_P(1 + A_0\beta)} \tag{11.63}$$

Thus the feedback moves the pole along the negative real axis to a frequency ω_{Pf},

$$\omega_{Pf} = \omega_P(1 + A_0\beta) \tag{11.64}$$

This process is illustrated in Fig. 11.30(a). Figure 11.30(b) shows Bode plots for $|A|$ and $|A_f|$. Note that while at low frequencies the difference between the two plots is $20 \log(1 + A_0\beta)$, the two curves coincide at high frequencies. One can show that this indeed is the case by approximating Eq. (11.63) for frequencies $\omega \gg \omega_P(1 + A_0\beta)$:

$$A_f(s) \simeq \frac{A_0\omega_P}{s} \simeq A(s) \tag{11.65}$$

Physically speaking, at such high frequencies the loop gain is much smaller than unity and the feedback is ineffective.

Figure 11.30(b) clearly illustrates the fact that applying negative feedback to an amplifier results in extending its bandwidth at the expense of a reduction in gain. Since the pole of the

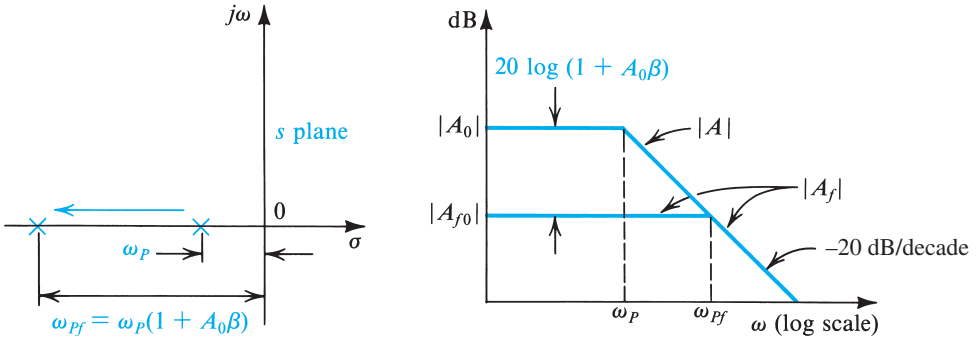


Figure 11.30 Effect of feedback on **(a)** the pole location and **(b)** the frequency response of an amplifier having a single-pole, open-loop response.

closed-loop amplifier never enters the right half of the s plane, the single-pole amplifier is stable for any value of β. Thus this amplifier is said to be **unconditionally stable**. This result, however, is hardly surprising, since the phase lag associated with a single-pole response can never be greater than 90°. Thus the loop gain never achieves the 180° phase shift required for the feedback to become positive.

EXERCISE

11.23 An op amp having a single-pole rolloff at 100 Hz and a low-frequency gain of 10^5 is operated in a feedback loop with $\beta = 0.01$. What is the factor by which feedback shifts the pole? To what frequency? If β is changed to a value that results in a nominal closed-loop gain of +1, to what frequency does the pole shift?

Ans. 1001; 100.1 kHz; 10 MHz

11.8.4 Amplifier with a Two-Pole Response

Consider next an amplifier whose open-loop transfer function is characterized by two real-axis poles:

$$A(s) = \frac{A_0}{(1 + s/\omega_{P1})(1 + s/\omega_{P2})} \tag{11.66}$$

In this case, the closed-loop poles are obtained from $1 + A(s)\beta = 0$, which leads to

$$s^2 + s(\omega_{P1} + \omega_{P2}) + (1 + A_0\beta)\omega_{P1}\omega_{P2} = 0 \tag{11.67}$$

Thus the closed-loop poles are given by

$$s = -\frac{1}{2}(\omega_{P1} + \omega_{P2}) \pm \frac{1}{2}\sqrt{(\omega_{P1} + \omega_{P2})^2 - 4(1 + A_0\beta)\omega_{P1}\omega_{P2}} \tag{11.68}$$

From Eq. (11.68) we see that as the loop gain $A_0\beta$ is increased from zero, the poles are brought closer together. Then a value of loop gain is reached at which the poles become coincident. If the loop gain is further increased, the poles become complex conjugate and move along a vertical line. Figure 11.31 shows the locus of the poles for increasing loop gain. This plot is called a **root-locus diagram**, where "root" refers to the fact that the poles are the roots of the characteristic equation.

From the root-locus diagram of Fig. 11.31 we see that this feedback amplifier also is unconditionally stable. Again, this result should come as no surprise; the maximum phase shift of $A(s)$ in this case is 180° (90° per pole), but this value is reached at $\omega = \infty$. Thus there is no finite frequency at which the phase shift reaches 180°.

Another observation to make on the root-locus diagram of Fig. 11.31 is that the open-loop amplifier might have a dominant pole, but this is not necessarily the case for the closed-loop amplifier. The response of the closed-loop amplifier can, of course, always be plotted once the poles have been found from Eq. (11.68). As is the case with second-order responses generally, the closed-loop response can show a peak (see Chapter 17). To be more specific,

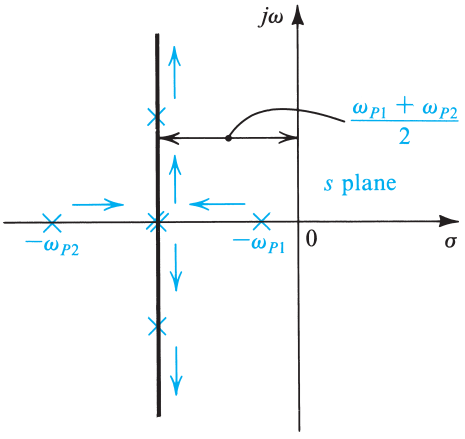


Figure 11.31 Root-locus diagram for a feedback amplifier whose open-loop transfer function has two real poles.

the characteristic equation of a second-order network can be written in the standard form

$$s^2 + s\frac{\omega_0}{Q} + \omega_0^2 = 0 \tag{11.69}$$

where ω_0 is called the **pole frequency** and Q is called **pole Q factor**. The poles are complex if Q is greater than 0.5. A geometric interpretation for ω_0 and Q of a pair of complex-conjugate poles is given in Fig. 11.32, from which we note that ω_0 is the radial distance of the poles from the origin and that Q indicates the distance of the poles from the $j\omega$ axis. Poles on the $j\omega$ axis have $Q = \infty$.

By comparing Eqs. (11.67) and (11.69), we obtain the Q factor for the poles of the feedback amplifier as

$$Q = \frac{\sqrt{(1+A_0\beta)\omega_{P1}\omega_{P2}}}{\omega_{P1}+\omega_{P2}} \tag{11.70}$$

From the study of second-order network responses in Chapter 17, it will be seen that the response of the feedback amplifier under consideration shows no peaking for $Q \leq 0.707$. The boundary case corresponding to $Q = 0.707$ (poles at 45° angles) results in the **maximally flat** response. Figure 11.33 shows a number of possible responses obtained for various values of Q (or, correspondingly, various values of $A_0\beta$).

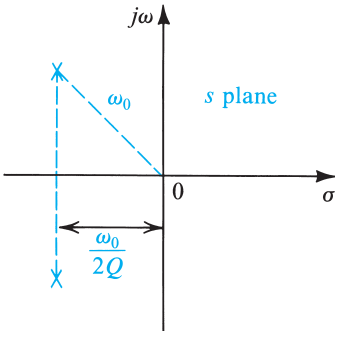


Figure 11.32 Definition of ω_0 and Q of a pair of complex-conjugate poles.

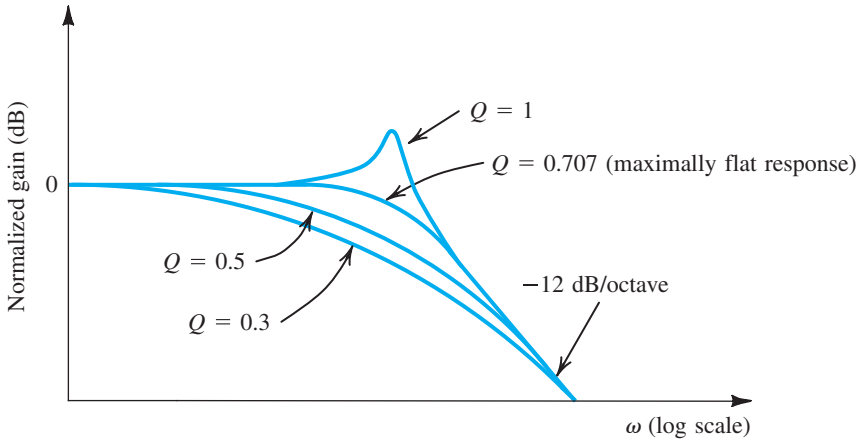


Figure 11.33 Normalized gain of a two-pole feedback amplifier for various values of Q. Note that Q is determined by the loop gain according to Eq. (11.70).

EXERCISE

11.24 An amplifier with a low-frequency gain of 100 and poles at 10^4 rad/s and 10^6 rad/s is incorporated in a negative-feedback loop with feedback factor β. For what value of β do the poles of the closed-loop amplifier coincide? What is the corresponding Q of the resulting second-order system? For what value of β is a maximally flat response achieved? What is the low-frequency closed-loop gain in the maximally flat case?

Ans. 0.245; 0.5; 0.5; 1.96 V/V

Example 11.11

As an illustration of some of the ideas just discussed, we consider the positive-feedback circuit shown in Fig. 11.34(a). Find the loop transmission $L(s)$ and the characteristic equation. Sketch a root-locus diagram for varying K, and find the value of K that results in a maximally flat response and the value of K that makes the circuit oscillate. Assume that the amplifier has frequency-independent gain, infinite input impedance, and zero output impedance.

Solution

To obtain the loop transmission, we short-circuit the signal source and break the loop at the amplifier input. We then apply a test voltage V_t and find the returned voltage V_r, as indicated in Fig. 11.34(b). The

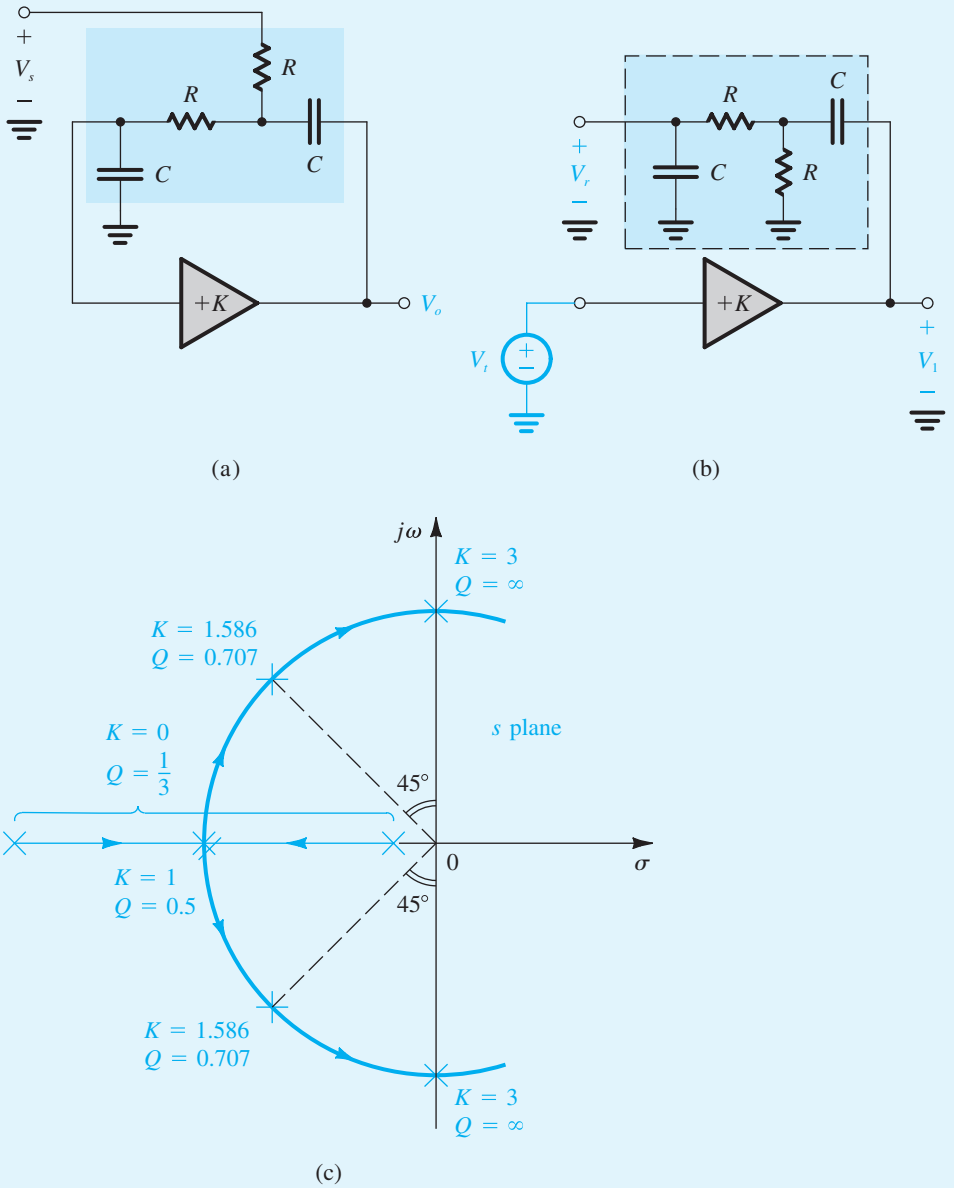


Figure 11.34 Circuits and plot for Example 11.11.

loop transmission $L(s) \equiv A(s)\beta(s)$ is given by

$$L(s) = -\frac{V_r}{V_t} = -KT(s) \tag{11.71}$$

Example 11.11 *continued*

where $T(s)$ is the transfer function of the two-port RC network shown inside the broken-line box in Fig. 11.34(b):

$$T(s) \equiv \frac{V_r}{V_1} = \frac{s(1/CR)}{s^2 + s(3/CR) + (1/CR)^2} \tag{11.72}$$

Thus,

$$L(s) = \frac{-s(K/CR)}{s^2 + s(3/CR) + (1/CR)^2} \tag{11.73}$$

The characteristic equation is

$$1 + L(s) = 0 \tag{11.74}$$

that is,

$$s^2 + s\frac{3}{CR} + \left(\frac{1}{CR}\right)^2 - s\frac{K}{CR} = 0$$

$$s^2 + s\frac{3-K}{CR} + \left(\frac{1}{CR}\right)^2 = 0 \tag{11.75}$$

By comparing this equation to the standard form of the second-order characteristic equation (Eq. 11.69), we see that the pole frequency ω_0 is given by

$$\omega_0 = \frac{1}{CR} \tag{11.76}$$

and the Q factor is

$$Q = \frac{1}{3-K} \tag{11.77}$$

Thus for $K = 0$, the poles have $Q = \frac{1}{3}$ and are therefore located on the negative real axis. As K is increased, the poles are brought closer together and eventually coincide ($Q = 0.5$, $K = 1$). Further increasing K results in the poles becoming complex and conjugate. The root locus is then a circle because the radial distance ω_0 remains constant (Eq. 11.76) independent of the value of K.

The maximally flat response is obtained when $Q = 0.707$, which results when $K = 1.586$. In this case the poles are at 45° angles, as indicated in Fig. 11.34(c). The poles cross the $j\omega$ axis into the right half of the s plane at the value of K that results in $Q = \infty$, that is, $K = 3$. Thus for $K \geq 3$ this circuit becomes unstable. This might appear to contradict our earlier conclusion that the feedback amplifier with a second-order response is unconditionally stable. Note, however, that the circuit in this example is quite different from the negative-feedback amplifier that we have been studying. Here we have an amplifier with a positive gain K and a feedback network whose transfer function $T(s)$ is frequency dependent. This feedback is in fact *positive,* and the circuit will oscillate at the frequency for which the phase of $T(j\omega)$ is zero (which is $1/CR$).

Example 11.11 illustrates the use of feedback (positive feedback in this case) to move the poles of an RC network from their negative real-axis locations to complex-conjugate locations. One can accomplish the same task using negative feedback, as the root-locus diagram of

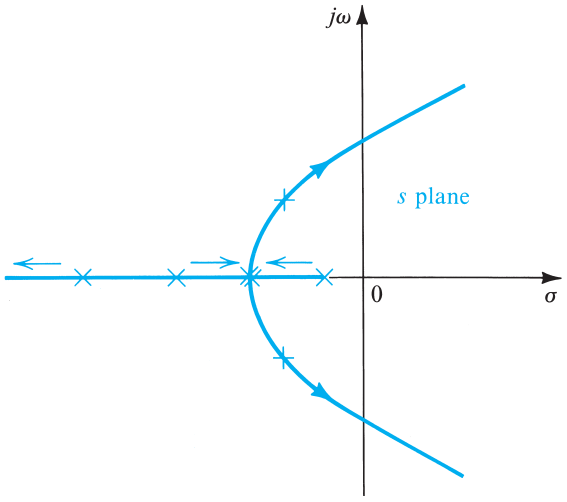


Figure 11.35 Root-locus diagram for an amplifier with three poles. The arrows indicate the pole movement as $A_0\beta$ is increased.

Fig. 11.31 demonstrates. The process of pole control is the essence of *active-filter design,* as will be discussed in Chapter 17.

11.8.5 Amplifiers with Three or More Poles

Figure 11.35 shows the root-locus diagram for a feedback amplifier whose open-loop response is characterized by three poles. As indicated, increasing the loop gain from zero moves the highest-frequency pole outward while the two other poles are brought closer together. As $A_0\beta$ is increased further, the two poles become coincident and then become complex and conjugate. A value of $A_0\beta$ exists at which this pair of complex-conjugate poles enters the right half of the s plane, thus causing the amplifier to become unstable.

This result is not entirely unexpected, since an amplifier with three poles has a phase shift that reaches –270° as ω approaches ∞. Thus there exists a finite frequency, ω_{180}, at which the loop gain has 180° phase shift.

From the root-locus diagram of Fig. 11.35, we observe that one can always maintain amplifier stability by keeping the loop gain $A_0\beta$ smaller than the value corresponding to the poles entering the right half-plane. In terms of the Nyquist diagram, the critical value of $A_0\beta$ is that for which the diagram passes through the (–1, 0) point. Reducing $A_0\beta$ below this value causes the Nyquist plot to shrink and thus intersect the negative real axis to the right of the (–1, 0) point, indicating stable amplifier performance. On the other hand, increasing $A_0\beta$ above the critical value causes the Nyquist plot to expand, thus encircling the (–1, 0) point and indicating unstable performance.

For a given open-loop gain A_0 the conclusions above can be stated in terms of the feedback factor β. That is, there exists a *maximum value* for β above which the feedback amplifier becomes unstable. Alternatively, we can state that there exists a *minimum value* for the closed-loop gain A_{f0} below which the amplifier becomes unstable. To obtain lower values of closed-loop gain, one needs therefore to alter the loop transfer function $L(s)$. This is the process known as *frequency compensation*. We shall study the theory and techniques of frequency compensation in Section 11.10.

Before leaving this section, we point out that construction of the root-locus diagram for amplifiers having three or more poles as well as finite zeros is an involved process for which a systematic procedure exists. However, such a procedure will not be presented here, and the interested reader should consult Haykin (1970). Although the root-locus diagram provides the amplifier designer with considerable insight, other, simpler techniques based on Bode plots can be effectively employed, as will be explained in Section 11.9.

EXERCISE

11.25 Consider a feedback amplifier for which the open-loop transfer function $A(s)$ is given by

$$A(s) = \left(\frac{10}{1 + s/10^4}\right)^3$$

Let the feedback factor β be frequency independent. Find the closed-loop poles as functions of β, and show that the root locus is that of Fig. E11.26. Also find the value of β at which the amplifier becomes unstable. (*Note:* This is the same amplifier that was considered in Exercise 11.22.)

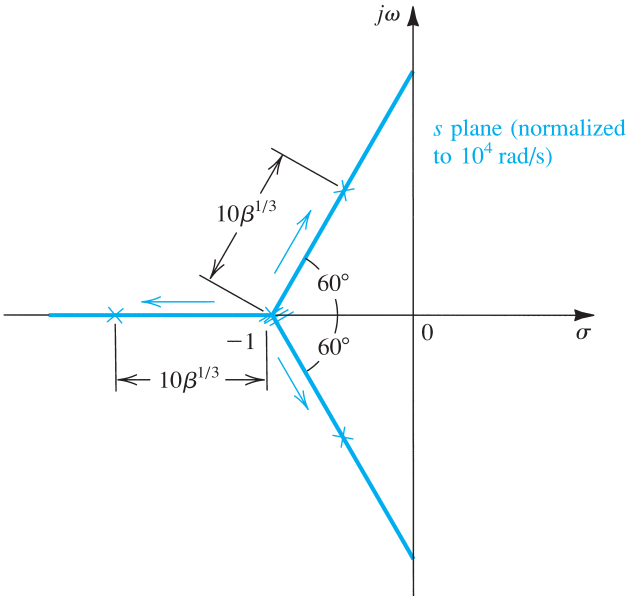


Figure E11.26

Ans. See Fig. E11.26; $\beta_{\text{critical}} = 0.008$

11.9 Stability Study Using Bode Plots

11.9.1 Gain and Phase Margins

From Sections 11.17 and 11.18 we know that whether a feedback amplifier is or is not stable can be determined by examining its loop gain $A\beta$ as a function of frequency. One of the simplest and most effective means for doing this is through the use of a Bode plot for $A\beta$, such as the one shown in Fig. 11.36. (Note that because the phase approaches –360°, the circuit examined is a fourth-order one.) The feedback amplifier whose loop gain is plotted in Fig. 11.36 will be stable, since at the frequency of 180° phase shift, ω_{180}, the magnitude of the loop gain is less than unity (negative dB). The difference between the value of $|A\beta|$ at ω_{180} and unity, called the **gain margin**, is usually expressed in decibels. The gain margin represents the amount by which the loop gain can be increased while stability is maintained. Feedback amplifiers are usually designed to have sufficient gain margin to allow for the inevitable changes in loop gain with temperature, time, and so on.

Another way to investigate the stability and to express its degree is to examine the Bode plot at the frequency for which $|A\beta| = 1$, which is the point at which the magnitude plot crosses the 0-dB line. If at this frequency the phase angle is less (in magnitude) than 180°, then the amplifier is stable. This is the situation illustrated in Fig. 11.36. The difference between the phase angle at this frequency and 180° is termed the **phase margin**. On the other hand, if at the frequency of unity loop-gain magnitude, the phase lag is in excess of 180°, the amplifier will be unstable.

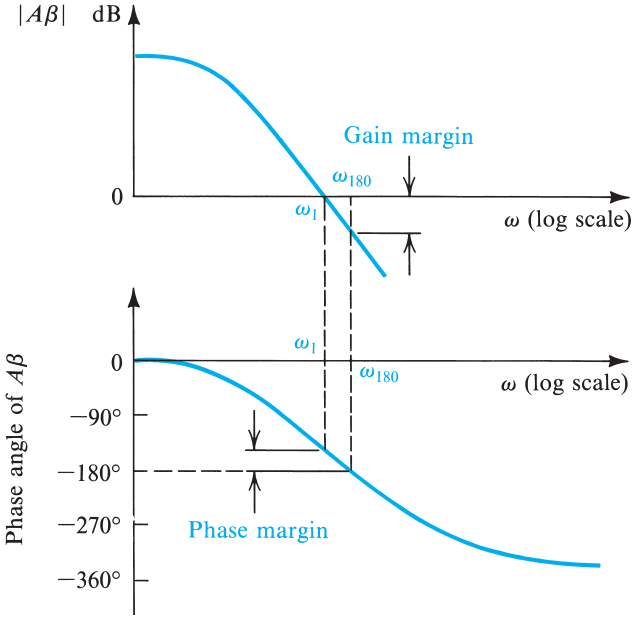


Figure 11.36 Bode plot for the loop gain $A\beta$ illustrating the definitions of the gain and phase margins.

EXERCISE

11.26 Consider an op amp having a single-pole, open-loop response with $A_0 = 10^5$ and $f_P = 10$ Hz. Let the op amp be ideal otherwise (infinite input impedance, zero output impedance, etc.). If this amplifier is connected in the noninverting configuration with a nominal low-frequency, closed-loop gain of 100, find the frequency at which $|A\beta| = 1$. Also, find the phase margin.
Ans. 10^4 Hz; 90°

11.9.2 Effect of Phase Margin on Closed-Loop Response

Feedback amplifiers are normally designed with a phase margin of at least 45°. The amount of phase margin has a profound effect on the shape of the closed-loop gain response. To see this relationship, consider a feedback amplifier with a large low-frequency loop gain, $A_0\beta \gg 1$. It follows that the closed-loop gain at low frequencies is approximately $1/\beta$. Denoting the frequency at which the magnitude of loop gain is unity by ω_1, we have (refer to Fig. 11.36)

$$A(j\omega_1)\beta = 1 \times e^{-j\theta} \tag{11.78}$$

where

$$\theta = 180° - \text{phase margin} \tag{11.79}$$

At ω_1 the closed-loop gain is

$$A_f(j\omega_1) = \frac{A(j\omega_1)}{1 + A(j\omega_1)\beta} \tag{11.80}$$

Substituting from Eq. (11.78) gives

$$A_f(j\omega_1) = \frac{(1/\beta)e^{-j\theta}}{1 + e^{-j\theta}} \tag{11.81}$$

Thus the magnitude of the gain at ω_1 is

$$|A_f(j\omega_1)| = \frac{1/\beta}{|1 + e^{-j\theta}|} \tag{11.82}$$

For a phase margin of 45°, $\theta = 135°$; and we obtain

$$|A_f(j\omega_1)| = 1.3\frac{1}{\beta} \tag{11.83}$$

That is, the gain peaks by a factor of 1.3 above the low-frequency value of $1/\beta$. This peaking increases as the phase margin is reduced, eventually reaching ∞ when the phase margin is zero. Zero phase margin, of course, implies that the amplifier can sustain oscillations [poles on the $j\omega$ axis; Nyquist plot passing through (–1, 0)].

EXERCISE

11.27 Find the closed-loop gain at ω_1 relative to the low-frequency gain when the phase margin is 30°, 60°, and 90°.
Ans. 1.93; 1; 0.707

11.9.3 An Alternative Approach for Investigating Stability

Investigating stability by constructing Bode plots for the loop gain $A\beta$ can be a tedious and time-consuming process, especially if we have to investigate the stability of a given amplifier for a variety of feedback networks. An alternative approach, which is much simpler, is to construct a Bode plot for the open-loop gain $A(j\omega)$ only. Assuming for the time being that β is independent of frequency, we can plot $20\log(1/\beta)$ as a horizontal straight line on the same plane used for $20\log|A|$. The difference between the two curves will be

$$20\log|A(j\omega)| - 20\log\frac{1}{\beta} = 20\log|A\beta| \tag{11.84}$$

which is the loop gain (in dB). We may therefore study stability by examining the difference between the two plots. If we wish to evaluate stability for a different feedback factor, we simply draw another horizontal straight line at the level $20\log(1/\beta)$.

To illustrate, consider an amplifier whose open-loop transfer function is characterized by three poles. For simplicity let the three poles be widely separated—say, at 0.1 MHz, 1 MHz, and 10 MHz, as shown in Fig. 11.37. Note that because the poles are widely separated, the phase is approximately –45° at the first pole frequency, –135° at the second, and –225° at the third. The frequency at which the phase of $A(j\omega)$ is –180° lies on the –40-dB/decade segment, as indicated in Fig. 11.37.

The open-loop gain of this amplifier can be expressed as

$$A = \frac{10^5}{(1+jf/10^5)(1+jf/10^6)(1+jf/10^7)} \tag{11.85}$$

from which $|A|$ can be easily determined for any frequency f (in Hz), and the phase can be obtained as

$$\phi = -\left[\tan^{-1}(f/10^5) + \tan^{-1}(f/10^6) + \tan^{-1}(f/10^7)\right] \tag{11.86}$$

The magnitude and phase graphs shown in Fig. 11.37 are obtained using the method for constructing Bode plots (Appendix F). These graphs provide approximate values for important amplifier parameters, with more exact values obtainable from Eqs. (11.85) and (11.86). For example, the frequency f_{180} at which the phase angle is 180° can be found from Fig. 11.37 to be approximately 3.2×10^6 Hz. Using this value as a starting point, a more exact value can be found by trial and error using Eq. (11.86). The result is $f_{180} = 3.34 \times 10^6$ Hz. At this frequency, Eq. (11.85) gives a gain magnitude of 58.2 dB, which is reasonably close to the approximate value of 60 dB given by Fig. 11.37.

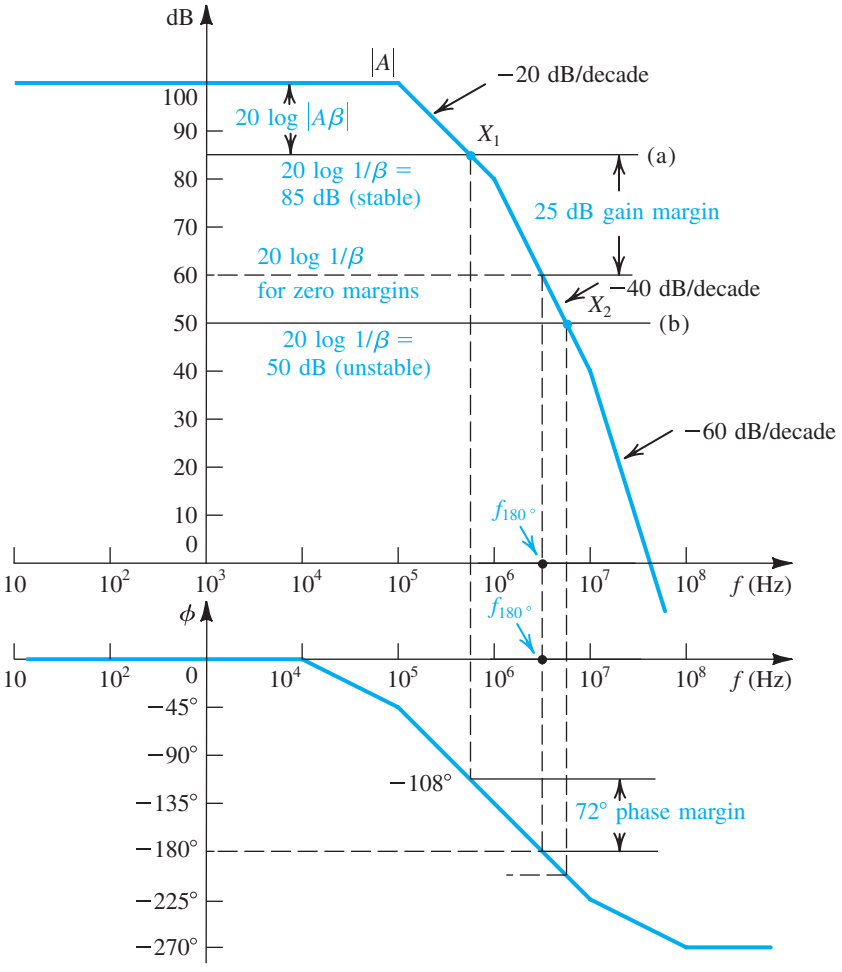


Figure 11.37 Stability analysis using Bode plot of |A|.

Consider next the straight line labeled (a) in Fig. 11.37. This line represents a feedback factor for which $20\log(1/\beta) = 85$ dB, which corresponds to $\beta = 5.623 \times 10^{-5}$ and a closed-loop gain of 83.6 dB. Since the loop gain is the difference between the $|A|$ curve and the $1/\beta$ line, the point of intersection X_1 corresponds to the frequency at which $|A\beta| = 1$. Using the graphs of Fig. 11.37, this frequency can be found to be approximately 5.6×10^5 Hz. A more exact value of 4.936×10^5 can be obtained using the transfer function equations. At this frequency the phase angle is approximately –108°. Thus the closed-loop amplifier, for which $20\log(1/\beta) = 85$ dB, will be stable with a phase margin of 72°. The gain margin can be easily obtained from Fig. 11.37; it is 25 dB.

Next, suppose that we wish to use this amplifier to obtain a closed-loop gain of 50-dB nominal value. Since $A_0 = 100$ dB, we see that $A_0\beta \gg 1$ and $20\log(A_0\beta) \simeq 50$ dB, resulting in $20\log(1/\beta) \simeq 50$ dB. To see whether this closed-loop amplifier is or is not stable, we draw line (b) in Fig. 11.37 with a height of 50 dB. This line intersects the open-loop gain curve at point X_2, where the corresponding phase is greater than 180°. Thus the closed-loop amplifier with 50-dB gain will be unstable.

In fact, it can easily be seen from Fig. 11.37 that the *minimum* value of $20\log(1/\beta)$ that can be used, with the resulting amplifier being stable, is 60 dB. In other words, the minimum value of stable closed-loop gain obtained with this amplifier is approximately 60 dB. At this value of gain, however, a manufactured version of this amplifier may still oscillate, since no margin is left to allow for possible changes in gain.

Since the 180°-phase point always occurs on the –40-dB/decade segment of the Bode plot for $|A|$, a rule of thumb to guarantee stability is as follows: *The closed-loop amplifier will be stable if the* $20\log(1/\beta)$ *line intersects the* $20\log|A|$ *curve at a point on the* –20-dB/decade *segment*. Following this rule ensures that a phase margin of at least 45° is obtained. For the example of Fig. 11.37, the rule implies that the maximum value of β is 10^{-4}, which corresponds to a closed-loop gain of approximately 80 dB.

The rule of thumb above can be generalized for the case in which β is a function of frequency. The general rule states that *at the intersection of* $20\log[1/|\beta(j\omega)|]$ *and* $20\log|A(j\omega)|$ *the difference of slopes* (called the **rate of closure**) *should not exceed* 20 dB/decade.

EXERCISE

11.28 Consider an op amp whose open-loop gain is identical to that of Fig. 11.37. Assume that the op amp is ideal otherwise. Let the op amp be connected as a differentiator. Use the rule of thumb above to show that for stable performance the differentiator time constant should be greater than 159 ms. [*Hint:* Recall that for a differentiator, the Bode plot for $1/|\beta(j\omega)|$ has a slope of +20 dB/decade and intersects the 0-dB line at $1/\tau$, where τ is the differentiator time constant.]

11.10 Frequency Compensation

In this section, we shall discuss methods for modifying the open-loop transfer function $A(s)$ of an amplifier having three or more poles so that the closed-loop amplifier is stable for a given desired value of closed-loop gain. This process is referred to as frequency compensation.

11.10.1 Theory

The simplest method of frequency compensation consists of introducing a new pole in the function $A(s)$ at a frequency, f_D, sufficiently low that the modified open-loop gain, $A'(s)$, intersects the $20\log(1/|\beta|)$ curve with a slope difference of 20 dB/decade. As an example, let it be required to compensate the amplifier whose $A(s)$ is shown in Fig. 11.38 such that closed-loop amplifiers with β as high as 10^{-2} (i.e., closed-loop gains as low as approximately 40 dB) will be stable. First, we draw a horizontal straight line at the 40-dB level to represent $20\log(1/\beta)$, as shown in Fig. 11.38. We then locate point Y on this line at the frequency of the first pole, f_{P1}. From Y we draw a line with –20-dB/decade slope and determine the point at which this line intersects the dc gain line, point Y'. This latter point

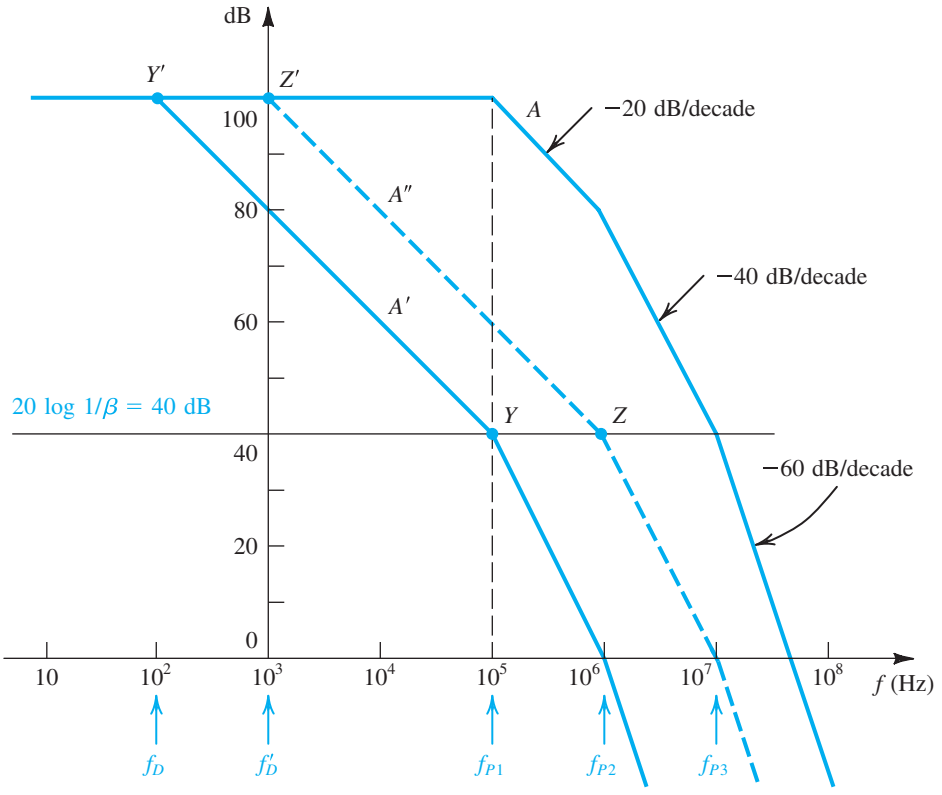


Figure 11.38 Frequency compensation for $\beta = 10^{-2}$. The response labeled A' is obtained by introducing an additional pole at f_D. The A'' response is obtained by moving the original low-frequency pole to f_D'.

gives the frequency f_D of the new pole that has to be introduced in the open-loop transfer function.

The compensated open-loop response $A'(s)$ is indicated in Fig. 11.38. It has four poles: at f_D, f_{P1}, f_{P2}, and f_{P3}. Thus $|A'|$ begins to roll off with a slope of –20 dB/decade at f_D. At f_{P1} the slope changes to – 40 dB/decade, at f_{P2} it changes to – 60 dB/decade, and so on. Since the 20 log(1/β) line intersects the $20\log|A'|$ curve at point Y on the –20-dB/decade segment, the closed-loop amplifier with this β value (or lower values) will be stable.

A serious disadvantage of this compensation method is that at most frequencies the open-loop gain has been drastically reduced. This means that at most frequencies the amount of feedback available will be small. Since all the advantages of negative feedback are directly proportional to the amount of feedback, the performance of the compensated amplifier will be impaired.

Careful examination of Fig. 11.38 shows that the gain $A'(s)$ is low because of the pole at f_{P1}. If we can somehow eliminate this pole, then—rather than locating point Y, drawing YY', and so on—we can start from point Z (at the frequency of the second pole) and draw the line ZZ'. This would result in the open-loop curve $A''(s)$, which shows considerably higher gain than $A'(s)$.

Although it is not possible to eliminate the pole at f_{P1}, it is usually possible to shift that pole from $f = f_{P1}$ to $f = f_D'$. This makes the pole dominant and eliminates the need for introducing an additional lower-frequency pole, as will be explained next.

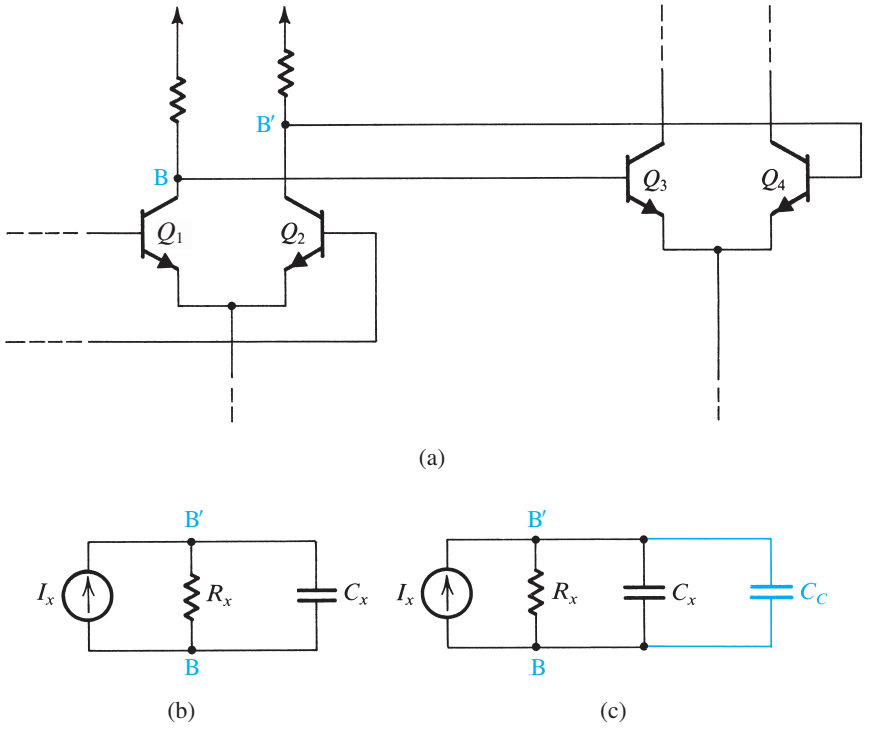


Figure 11.39 **(a)** Two cascaded gain stages of a multistage amplifier. **(b)** Equivalent circuit for the interface between the two stages in **(a)**. **(c)** Same circuit as in **(b)**, but with a compensating capacitor C_C added. Note that the analysis here applies equally well to MOS amplifiers.

11.10.2 Implementation

We shall now address the question of implementing the frequency-compensation scheme discussed above. The amplifier circuit normally consists of a number of cascaded gain stages, with each stage responsible for one or more of the transfer function poles. Through manual and/or computer analysis of the circuit, one identifies the stage that introduces each of the important poles f_{P1}, f_{P2}, and so on. For the purpose of our discussion, assume that the first pole f_{P1} is introduced at the interface between the two cascaded differential stages shown in Fig. 11.39(a). In Fig. 11.39(b) we show a simple small-signal model of the circuit at this interface. Current source I_x represents the output-signal current of the Q_1–Q_2 stage. Resistance R_x and capacitance C_x represent the total resistance and capacitance between the two nodes B and B′. It follows that the pole f_{P1} is given by

$$f_{P1} = \frac{1}{2\pi C_x R_x} \tag{11.87}$$

Let us now connect the compensating capacitor C_C between nodes B and B′. This will result in the modified equivalent circuit shown in Fig. 11.39(c), from which we see that the pole introduced will no longer be at f_{P1}; rather, the pole can be at any desired lower frequency f_D' :

$$f_D' = \frac{1}{2\pi (C_x + C_C) R_x} \tag{11.88}$$

We thus conclude that one can select an appropriate value for C_C to shift the pole frequency from f_{P1} to the value f_D' determined by point Z' in Fig. 11.38.

At this juncture it should be pointed out that adding the capacitor C_C will usually result in changes in the location of the other poles (those at f_{P2} and f_{P3}). One might therefore need to calculate the new location of f_{P2} and perform a few iterations to arrive at the required value for C_C.

A disadvantage of this implementation method is that the required value of C_C is usually quite large. Thus if the amplifier to be compensated is an IC op amp, it will be difficult, and probably impossible, to include this compensating capacitor on the IC chip. (As pointed out in Chapter 8 and in Appendix A, the maximum practical size of a monolithic capacitor is about 100 pF.) An elegant solution to this problem is to connect the compensating capacitor in the feedback path of an inverting amplifier stage. Because of the Miller effect (Section 10.3), the compensating capacitance will be multiplied by the stage gain, resulting in a much larger effective capacitance. Furthermore, as explained later, another unexpected benefit accrues.

11.10.3 Miller Compensation and Pole Splitting

Figure 11.40(a) shows one gain stage in a multistage amplifier. For simplicity, the stage is shown as a common-emitter amplifier, but in practice it can be a more elaborate circuit. In the feedback path of this common-emitter stage we have placed a compensating capacitor C_f.

Figure 11.40(b) shows a simplified equivalent circuit of the gain stage of Fig. 11.40(a). Here R_1 and C_1 represent the total resistance and total capacitance between node B and ground. Similarly, R_2 and C_2 represent the total resistance and total capacitance between node C and ground. Furthermore, it is assumed that C_1 includes the Miller component due to capacitance C_μ, and C_2 includes the input capacitance of the succeeding amplifier stage. Finally, I_i represents the output signal current of the preceding stage.

In the absence of the compensating capacitor C_f, we can see from Fig. 11.40(b) that there are two poles—one at the input and one at the output. Let us assume that these two poles are f_{P1} and f_{P2} of Fig. 11.38; thus,

$$f_{P1} = \frac{1}{2\pi C_1 R_1} \qquad f_{P2} = \frac{1}{2\pi C_2 R_2} \tag{11.89}$$

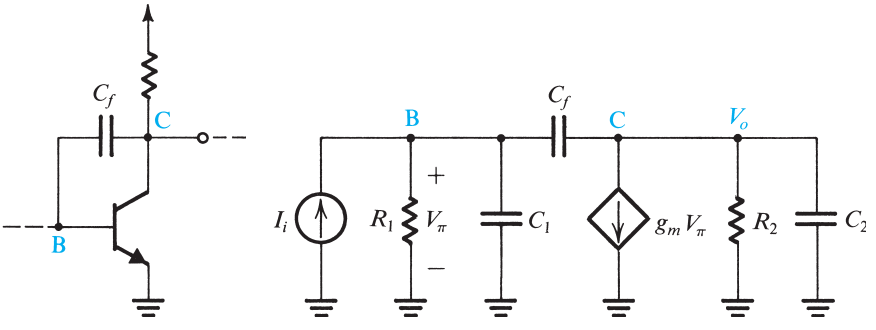


Figure 11.40 **(a)** A gain stage in a multistage amplifier with a compensating capacitor connected in the feedback path, and **(b)** equivalent circuit. Note that although a BJT is shown, the analysis applies equally well to the MOSFET case.

With C_f present, analysis of the circuit yields the transfer function

$$\frac{V_o}{I_i} = \frac{(sC_f - g_m)R_1R_2}{1 + s[C_1R_1 + C_2R_2 + C_f(g_mR_1R_2 + R_1 + R_2)] + s^2[C_1C_2 + C_f(C_1 + C_2)]R_1R_2} \tag{11.90}$$

The zero is usually at a much higher frequency than the dominant pole, and we shall neglect its effect. The denominator polynomial $D(s)$ can be written in the form

$$D(s) = \left(1 + \frac{s}{\omega'_{P1}}\right)\left(1 + \frac{s}{\omega'_{P2}}\right) = 1 + s\left(\frac{1}{\omega'_{P1}} + \frac{1}{\omega'_{P2}}\right) + \frac{s^2}{\omega'_{P1}\omega'_{P2}} \tag{11.91}$$

where ω'_{P1} and ω'_{P2} are the new frequencies of the two poles. Normally one of the poles will be dominant; $\omega'_{P1} \ll \omega'_{P2}$. Thus,

$$D(s) \simeq 1 + \frac{s}{\omega'_{P1}} + \frac{s^2}{\omega'_{P1}\omega'_{P2}} \tag{11.92}$$

Equating the coefficients of s in the denominator of Eq. (11.90) and in Eq. (11.92) results in

$$\omega'_{P1} = \frac{1}{C_1R_1 + C_2R_2 + C_f(g_mR_1R_2 + R_1 + R_2)}$$

which can be approximated by

$$\omega'_{P1} \simeq \frac{1}{g_mR_2C_fR_1} \tag{11.93}$$

To obtain ω'_{P2} we equate the coefficients of s^2 in the denominator of Eq. (11.90) and in Eq. (11.92) and use Eq. (11.93):

$$\omega'_{P2} \simeq \frac{g_mC_f}{C_1C_2 + C_f(C_1 + C_2)} \tag{11.94}$$

From Eqs. (11.93) and (11.94), we see that as C_f is increased, ω'_{P1} is reduced and ω'_{P2} is increased. This action is referred to as **pole splitting**. Note that the increase in ω'_{P2} is highly beneficial; it allows us to move point Z (see Fig. 11.38) further to the right, thus resulting in higher compensated open-loop gain. Finally, note from Eq. (11.93) that C_f is multiplied by the Miller effect factor g_mR_2, thus resulting in a much larger effective capacitance, $g_mR_2C_f$. In other words, the required value of C_f will be much smaller than that of C_C in Fig. 11.39.

Example 11.12

Consider an op amp whose open-loop transfer function is identical to that shown in Fig. 11.37. We wish to compensate this op amp so that the closed-loop amplifier with resistive feedback is stable for any gain (i.e., for β up to unity). Assume that the op-amp circuit includes a stage such as that of Fig. 11.40 with $C_1 = 100$ pF, $C_2 = 5$ pF, and $g_m = 40$ mA/V, that the pole at f_{P1} is caused by the input circuit of that stage, and that the pole at f_{P2} is introduced by the output circuit. Find the value of the compensating capacitor

Example 11.12 *continued*

for two cases: either if it is connected between the input node B and ground or in the feedback path of the transistor.

Solution

First we determine R_1 and R_2 from

$$f_{P1} = 0.1 \text{ MHz} = \frac{1}{2\pi C_1 R_1}$$

Thus,

$$R_1 = \frac{10^5}{2\pi} \ \Omega$$

$$f_{P2} = 1 \text{ MHz} = \frac{1}{2\pi C_2 R_2}$$

Thus,

$$R_2 = \frac{10^5}{\pi} \ \Omega$$

If a compensating capacitor C_C is connected across the input terminals of the transistor stage, then the frequency of the first pole changes from f_{P1} to f_D':

$$f_D' = \frac{1}{2\pi (C_1 + C_C) R_1}$$

The second pole remains unchanged at 1 MHz. The required value for f_D' is determined by drawing a –20-dB/decade line from the 1-MHz frequency point on the $20 \log(1/\beta) = 20 \log 1 = 0$ dB line. This line will intersect the 100-dB dc gain line at 10 Hz. Thus,

$$f_D' = 10 \text{ Hz} = \frac{1}{2\pi (C_1 + C_C) R_1}$$

which results in $C_C \simeq 1$ μF, which is quite large and certainly cannot be included on the IC chip.

Next, if a compensating capacitor C_f is connected in the feedback path of the transistor, then both poles change location to the values given by Eqs. (11.93) and (11.94):

$$f_{P1}' \simeq \frac{1}{2\pi g_m R_2 C_f R_1} \qquad f_{P2}' \simeq \frac{g_m C_f}{2\pi \left[C_1 C_2 + C_f (C_1 + C_2) \right]} \tag{11.95}$$

To determine where we should locate the first pole, we need to know the value of f_{P2}'. As an approximation, let us assume that $C_f \gg C_2$, which enables us to obtain

$$f_{P2}' \simeq \frac{g_m}{2\pi (C_1 + C_2)} = 60.6 \text{ MHz}$$

Thus it appears that this pole will move to a frequency higher than f_{P3} (which is 10 MHz). Let us therefore assume that the second pole will be at f_{P3}. This requires that the modified first pole be located at

$$f_{P1}' = \frac{f_{P3}}{A_0} = \frac{10^7 \text{ Hz}}{10^5} = 100 \text{ Hz}$$

Thus,

$$f'_{P1} = 100\,\text{Hz} = \frac{1}{2\pi g_m R_2 C_f R_1}$$

which results in $C_f = 78.5$ pF. Although this value is indeed much greater than C_2, we can determine the location of the pole f'_{P2} from Eq. (11.95), which yields $f'_{P2} = 57.2$ MHz, confirming that this pole has indeed been moved past f_{P3}.

We conclude that using Miller compensation not only results in a much smaller compensating capacitor but, owing to pole splitting, also enables us to place the dominant pole a decade higher in frequency. This results in a wider bandwidth for the compensated op amp.

EXERCISES

11.29 A multipole amplifier having a first pole at 1 MHz and an open-loop gain of 100 dB is to be compensated for closed-loop gains as low as 20 dB by the introduction of a new dominant pole. At what frequency must the new pole be placed?

Ans. 100 Hz

11.30 For the amplifier described in Exercise 11.29, rather than introducing a new dominant pole, we can use additional capacitance at the circuit node at which the first pole is formed to reduce the frequency of the first pole. If the frequency of the second pole is 10 MHz and if it remains unchanged while additional capacitance is introduced as mentioned, find the frequency to which the first pole must be lowered so that the resulting amplifier is stable for closed-loop gains as low as 20 dB. By what factor must the capacitance at the controlling node be increased?

Ans. 1000 Hz; 1000

Summary

- Negative feedback is employed to make the amplifier gain less sensitive to component variations; to control input and output resistances; to extend bandwidth; to reduce nonlinear distortion; and to enhance signal-to-interference ratio.
- The advantages above are obtained at the expense of a reduction in gain and at the risk of the amplifier becoming unstable (that is, oscillating). The latter problem is solved by careful design.
- The structure of an ideal negative-feedback amplifier is shown in Fig. 11.1. Table 11.1 summarizes the parameters and relationships governing the operation of the ideal structure.
- For each of the four basic types of amplifier, there is an appropriate feedback topology. The four topologies, together with their analysis procedure and their effects on input and output impedances, are summarized in Table 11.2 in Section 11.6.
- The key feedback parameters are the loop gain ($A\beta$), which for negative feedback must be a positive dimensionless number, and the amount of feedback ($1 + A\beta$). The latter directly determines gain reduction, gain

desensitivity, bandwidth extension, and changes in R_i and R_o.

- The loop gain $A\beta$ can be determined by breaking the feedback loop, as illustrated in Figs. 11.2 and 11.9. The value of $A\beta$ can be used together with the feedback factor β to determine A and hence A_f. This method, though simple, is incomplete as it does not enable the determination of the input and output resistances. For these, we utilize the systematic method for feedback analysis (refer to Table 11.2).
- The ideal or upper-bound value of the closed-loop gain A_f is $1/\beta$ and is approached when $A\beta \gg 1$.
- Since A and β are in general frequency dependent, the poles of the feedback amplifier are obtained by solving the characteristic equation $1 + A(s)\beta(s) = 0$.
- For the feedback amplifier to be stable, its poles must all be in the left half of the s plane.
- Stability is guaranteed if at the frequency for which the phase angle of $A\beta$ is 180° (i.e., ω_{180}), $|A\beta|$ is less than unity; the amount by which it is less than unity, expressed in decibels, is the gain margin. Alternatively, the amplifier is stable if, at the frequency at which $|A\beta| = 1$, the phase angle is less than 180°; the difference is the phase margin.
- The stability of a feedback amplifier can be analyzed by constructing a Bode plot for $|A|$ and superimposing on it a plot for $20 \log 1/|\beta|$. Stability is guaranteed if the two plots intersect with a difference in slope no greater than 6 dB/octave.
- To make a given amplifier stable for a given feedback factor β, the open-loop frequency response is suitably modified by a process known as frequency compensation.
- A popular method for frequency compensation involves connecting a feedback capacitor across an inverting stage in the amplifier. This causes the pole formed at the input of the amplifier stage to shift to a lower frequency and thus become dominant, while the pole formed at the output of the amplifier stage is moved to a very high frequency and thus becomes unimportant. This process is known as pole splitting.

PROBLEMS

Computer Simulation Problems

SIM Problems identified by the Multisim/PSpice icon are intended to demonstrate the value of using SPICE simulation to verify hand analysis and design, and to investigate important issues such as allowable signal swing and amplifier nonlinear distortion. Instructions to assist in setting up PSpice and Multisim simulations for all the indicated problems can be found in the corresponding files on the website. Note that if a particular parameter value is not specified in the problem statement, you are to make a reasonable assumption.

Section 11.1: The General Feedback Structure

11.1 A negative-feedback amplifier has a closed-loop gain $A_f = 200$ and an open-loop gain $A = 10^4$. What is the feedback factor β? If a manufacturing error results in a reduction of A to 10^3, what closed-loop gain results? What is the percentage change in A_f corresponding to this factor of 10 reduction in A?

11.2 Consider the op-amp circuit shown in Fig. P11.2, where the op amp has infinite input resistance and zero output resistance but finite open-loop gain A.

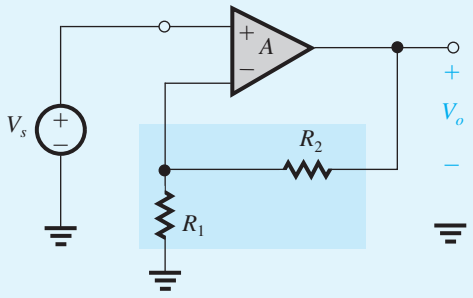


Figure P11.2

(a) Convince yourself that $\beta = R_1/(R_1 + R_2)$.
(b) If $R_1 = 10$ kΩ, find R_2 that results in $A_f = 10$ V/V for the following three cases: (i) $A = 1000$ V/V; (ii) $A = 200$ V/V; (iii) $A = 15$ V/V.

SIM = Multisim/PSpice; * = difficult problem; ** = more difficult; *** = very challenging; D = design problem

(c) For each of the three cases in (b), find the percentage change in A_f that results when A decreases by 20%. Comment on the results.

11.3 The noninverting buffer op-amp configuration shown in Fig. P11.3 provides a direct implementation of the feedback loop of Fig. 11.1. Assuming that the op amp has infinite input resistance and zero output resistance, what is β? If $A = 1000$, what is the closed-loop voltage gain? What is the amount of feedback (in dB)? For $V_s = 1$ V, find V_o and V_i. If A decreases by 10%, what is the corresponding percentage decrease in A_f?

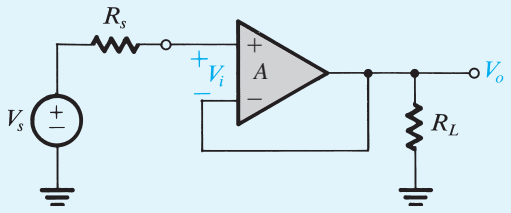


Figure P11.3

11.4 In a particular circuit represented by the block diagram of Fig. 11.1, a signal of 1 V from the source results in a difference signal of 10 mV being provided to the amplifying element A, and 5 V appearing at the output. For this arrangement, identify the values of A and β that apply.

11.5 (a) Show that in a negative-feedback amplifier with loop gain $A\beta \gg 1$, the closed-loop gain A_f is lower than its ideal value of $1/\beta$ by $(100/A\beta)\%$.

(b) What is the minimum loop gain required so that A_f is within (i) 0.1%, (ii) 1%, and (iii) 5% of its ideal value?

11.6 In a particular amplifier design, the β network consists of a linear potentiometer for which β is 0.00 at one end, 1.00 at the other end, and 0.50 in the middle. As the potentiometer is adjusted, find the three values of closed-loop gain that result when the amplifier open-loop gain is (a) 1 V/V, (b) 10 V/V, (c) 100 V/V, (d) 1000 V/V, and (e) 10,000 V/V. Provide your results in a table in which there is a row for each value of A and a column for each value of β.

11.7 A newly constructed feedback amplifier undergoes a performance test with the following results: With the feedback connection removed, a source signal of 2 mV is required to provide a 5-V output; with the feedback connected, a 5-V output requires a 100-mV source signal. For this amplifier, identify values of A, β, $A\beta$, the closed-loop gain, and the amount of feedback (in dB).

D 11.8 An amplifier has an open-loop gain with a nominal value of 1000 but can vary from unit to unit by as much as $\pm 50\%$ of nominal. It is required to apply negative feedback to this amplifier so that the variability of the closed-loop gain of the resulting feedback amplifier is limited to $\pm 1\%$. What is the largest possible nominal value of closed-loop gain that can be achieved? Now if three of these feedback amplifiers are placed in cascade, what is the nominal value of the gain of the resulting cascade amplifier? What is the expected variability of this gain?

11.9 The op amp in the circuit of Fig. P11.9 has an open-circuit voltage gain μ, a differential input resistance R_{id}, and a negligibly small output resistance. It is connected in the noninverting configuration with a feedback network consisting of a voltage divider (R_1, R_2). While β is still determined by the divider ratio [i.e., $\beta = R_1/(R_1 + R_2)$], the open-loop gain A is no longer simply equal to μ. This is because the feedback network now loads the input of the amplifier (because of the finite R_{id}). To determine the value of A, use the method outlined in Section 11.1.3 to determine the loop gain $A\beta$. Thus show that

$$A = \mu \frac{R_{id}}{R_{id} + (R_1 \parallel R_2)}$$

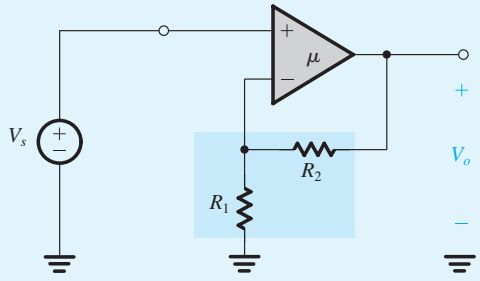


Figure P11.9

Section 11.2: Some Properties of Negative Feedback

11.10 For the negative-feedback loop of Fig. 11.1, find the loop gain $A\beta$ for which the sensitivity of closed-loop gain to open-loop gain [i.e., $(dA_f/A_f)/(dA/A)$] is –40 dB. For what value of $A\beta$ does the sensitivity become 1/5?

SIM = Multisim/PSpice; * = difficult problem; ** = more difficult; *** = very challenging; D = design problem

D 11.11 A designer is considering two possible designs of a feedback amplifier. The ultimate goal is $A_f = 10$ V/V. One design employs an amplifier for which $A = 1000$ V/V and the other uses $A = 500$ V/V. Find β and the desensitivity factor in both cases. If the $A = 1000$ amplifier units have a gain uncertainty of $\pm 10\%$, what is the gain uncertainty for the closed-loop amplifiers utilizing this amplifier type? If the same result is to be achieved with the $A = 500$ amplifier, what is the maximum allowable uncertainty in its gain?

D 11.12 A designer is required to achieve a closed-loop gain of $10 \pm 0.1\%$ V/V using a basic amplifier whose gain variation is $\pm 10\%$. What nominal value of A and β (assumed constant) are required?

D 11.13 A circuit designer requires a gain of $25 \pm 1\%$ V/V using an amplifier whose gain varies by a factor of 10 over temperature and time. What is the lowest gain required? The value of β? (*Hint*: Since the change in the open-loop gain is very large, do *not* use differential analysis.)

D 11.14 A power amplifier employs an output stage whose gain varies from 2 to 12 for various reasons. What is the gain of an ideal (nonvarying) amplifier connected to drive it so that an overall gain with feedback of $100 \pm 5\%$ V/V can be achieved? What is the value of β to be used? What are the requirements if A_f must be held within $\pm 0.5\%$? For each of these situations, what preamplifier gain and feedback factor β are required if A_f is to be 10 V/V (with the two possible tolerances)? (*Hint*: Since the change in the open-loop gain is very large, do *not* use differential analysis.)

D 11.15 It is required to design an amplifier with a gain of 100 that is accurate to within $\pm 1\%$. You have available amplifier stages with a gain of 1000 that is accurate to within $\pm 30\%$. Provide a design that uses a number of these gain stages in cascade, with each stage employing negative feedback of an appropriate amount. Obviously, your design should use the lowest possible number of stages while meeting specification.

D *11.16 It is required to design an amplifier to have a nominal closed-loop gain of 10 V/V using a battery-operated amplifier whose gain reduces to half its normal full-battery value over the life of the battery. If only 2% drop in closed-loop gain is desired, what nominal open-loop amplifier gain must be used in the design? (Note that since the change in A is large, it is inaccurate to use differentials.) What value of β should be chosen? If component-value variation in the β network may produce as much as a $\pm 1\%$ variation in β, to what value must A be raised to ensure the required minimum gain?

D 11.17 Design a feedback amplifier that has a closed-loop gain of 100 V/V and is relatively insensitive to change in basic-amplifier gain. In particular, it should provide a reduction in A_f to 99 V/V for a reduction in A to one-tenth its nominal value. What is the required loop gain? What nominal value of A is required? What value of β should be used? What would the closed-loop gain become if A were increased tenfold? If A were made infinite?

11.18 Consider an amplifier having a midband gain A_M and a low-frequency response characterized by a pole at $s = -\omega_L$ and a zero at $s = 0$. Let the amplifier be connected in a negative-feedback loop with a feedback factor β. Find an expression for the midband gain and the lower 3-dB frequency of the closed-loop amplifier. By what factor have both changed?

11.19 A capacitively coupled amplifier has a midband gain of 1000 V/V, a single high-frequency pole at 10 kHz, and a single low-frequency pole at 100 Hz. Negative feedback is employed so that the midband gain is reduced to 10. What are the upper and lower 3-dB frequencies of the closed-loop gain?

D 11.20 Low-cost audio power amplifiers often avoid direct coupling of the loudspeaker to the output stage because any resulting dc bias current in the speaker can use up (and thereby waste) its limited mechanical dynamic range. Unfortunately, the coupling capacitor needed can be large! But feedback helps. For example, for an 8-Ω loudspeaker and $f_L = 100$ Hz, what size capacitor is needed? Now, if feedback is arranged around the amplifier and the speaker so that a closed-loop gain $A_f = 10$ V/V is obtained from an amplifier whose open-loop gain is 1000 V/V, what value of f_{Lf} results? If the ultimate product-design specification requires a 50-Hz cutoff, what capacitor can be used?

D *11.21 It is required to design a dc amplifier with a low-frequency gain of 1000 and a 3-dB frequency of 1 MHz. You have available gain stages with a gain of 1000 but with a dominant high-frequency pole at 20 kHz. Provide a design that employs a number of such stages in cascade, each with negative feedback of an appropriate amount. Use identical stages.


Hint: The 3-dB frequency of a cascade of N identical gain stages, each with a 3-dB frequency $f_{3dB}|_{stage}$ is given by

$$f_{3dB}|_{cascade} = f_{3dB}|_{stage}\sqrt{2^{1/N}-1}$$


D 11.22 Design a supply-ripple-reduced power amplifier for which the output stage can be modeled by the block diagram of Fig. 11.5, where $A_1 = 0.9$ V/V, and the power-supply ripple $V_N = \pm 1$ V. A closed-loop gain of 10 V/V is desired. What is the gain of the low-ripple preamplifier needed to reduce the output ripple to ±100 mV? To ±10 mV? To ±1 mV? For each case, specify the value required for the feedback factor β.

D 11.23 A feedback amplifier is to be designed using a feedback loop connected around a two-stage amplifier. The first stage is a direct-coupled, small-signal amplifier with a high upper 3-dB frequency. The second stage is a power-output stage with a midband gain of 10 V/V and upper and lower 3-dB frequencies of 8 kHz and 80 Hz, respectively. The feedback amplifier should have a midband gain of 100 V/V and an upper 3-dB frequency of 40 kHz. What is the required gain of the small-signal amplifier? What value of β should be used? What does the lower 3-dB frequency of the overall amplifier become?

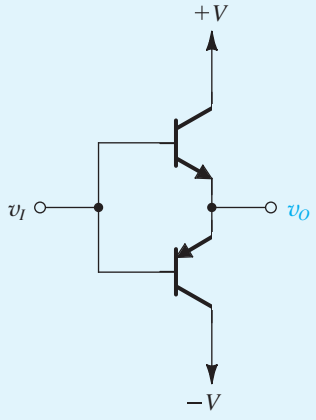***11.24** The complementary BJT follower shown in Fig. P11.24(a) has the approximate transfer characteristic shown in Fig. P11.24(b). Observe that for $-0.7\text{ V} \le v_I \le +0.7\text{ V}$, the output is zero. This "dead band" leads to crossover distortion (see Section 12.3). Consider this follower to be driven by the output of a differential amplifier of gain 100



(a)

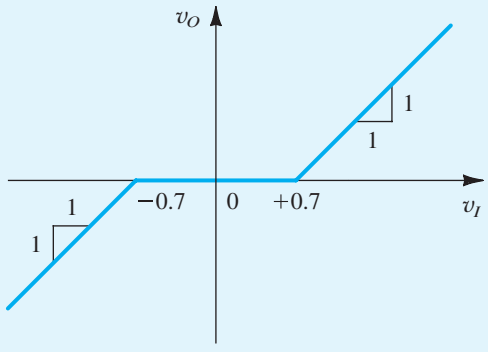

(b)

Figure P11.24 *continued*

whose positive-input terminal is connected to the input signal source v_S and whose negative-input terminal is connected to the emitters of the follower. Sketch the transfer characteristic v_O versus v_S of the resulting feedback amplifier. What are the limits of the dead band, and what are the gains outside the dead band?

D 11.25 A particular amplifier has a nonlinear transfer characteristic that can be approximated as follows:

(a) For small input signals, $|v_I| \le 10$ mV, $v_O/v_I = 10^3$.
(b) For intermediate input signals, 10 mV $\le |v_I| \le 60$ mV, $\Delta v_O/\Delta v_I = 10^2$.
(c) For large input signals, $|v_I| \ge 60$ mV, the output saturates.

If the amplifier is connected in a negative-feedback loop, find the feedback factor β that reduces the factor-of-10 change in gain (occurring at $|v_I| = 10$ mV) to only a 10% change. What is the transfer characteristic v_O versus v_S of the amplifier with feedback?

Section 11.3: The Feedback Voltage Amplifier

D 11.26 For the feedback voltage amplifier of Fig. 11.8(a), let the op amp have an infinite input resistance, a zero output resistance, and a finite open-loop gain of 1000 V/V. If $R_1 = 10$ kΩ, what value should R_2 have to obtain an ideal closed-loop gain of 10? Now, calculate the loop gain $A\beta$ and use it to find the actual value of the closed-loop gain A_f. If A_f is to be exactly 10, what must the value of R_2 be?

D 11.27 Consider the series–shunt feedback amplifier in Fig. 11.11(a), which is analyzed in Example 11.3.

(a) If $R_1 = 10$ kΩ, find the value of R_2 that results in an ideal closed-loop gain of 10.

Figure P11.24

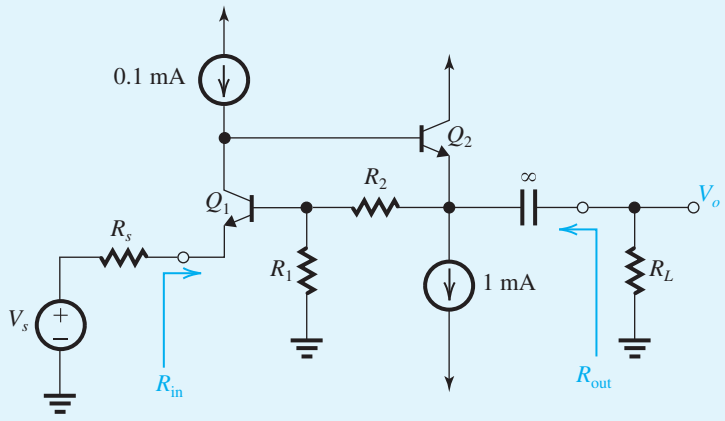


Figure P11.29

(b) Use the expression for $A\beta$ derived in Example 11.3 to find the value of the loop gain for the case $\mu = 1000$, $R_{id} = 100\,\text{k}\Omega$, $r_o = 1\,\text{k}\Omega$, $R_s = 100\,\text{k}\Omega$, and $R_L = 10\,\text{k}\Omega$. Hence determine the value of the closed-loop gain A_f.

(c) By what factor must μ be increased to ensure that A_f is within 1% of the ideal value of 10?

D 11.28 Consider the series–shunt feedback amplifier of Fig. 11.8(b) that is analyzed in Example 11.2.

(a) If $R_1 = 1\,\text{k}\Omega$, what value should R_2 have to obtain a closed-loop gain whose ideal value is 5 V/V?

(b) If $g_{m1} = g_{m2} = 4\,\text{mA/V}$, $R_{D1} = R_{D2} = 10\,\text{k}\Omega$, and the MOSFET's r_o is very large, use the expression for $A\beta$ derived in Example 11.2 to find the value of $A\beta$ and hence determine the closed-loop gain A_f.

***11.29** In the series–shunt feedback amplifier shown in Fig. P11.29, the devices operate with $V_{BE} = 0.7$ V and have $\beta_1 = \beta_2 = 100$. The input signal V_s has a zero dc component. Resistances $R_s = 100\ \Omega$, $R_1 = 1\,\text{k}\Omega$, $R_2 = 10\,\text{k}\Omega$, and $R_L = 1\,\text{k}\Omega$.

(a) If the loop gain is large, what do you expect the closed-loop gain to be? Give both an expression and its value.

(b) Find the dc emitter current in each of Q_1 and Q_2. Also, find the dc voltage at the emitter of Q_2.

(c) Calculate the value of the loop gain $A\beta$. (*Hint*: Set $V_s = 0$ and break the loop at the base of Q_1. Simplify the circuit by eliminating dc sources.)

(d) Calculate the value of A_f.

D 11.30 Consider the series–shunt feedback amplifier of Fig. 11.8(c), which was the subject of Exercise 11.6. Assume that the voltage divider (R_1, R_2) is implemented with a 1-MΩ potentiometer. Assume that the MOSFET is biased so that $g_m = 4$ mA/V and r_o is large. Also, $R_D = 10\,\text{k}\Omega$. Find the value of R_1 that results in a closed-loop gain of 5 V/V.

D 11.31 Figure P11.31 shows a series–shunt feedback amplifier known as a "feedback triple." All three MOSFETs are biased to operate at $g_m = 4$ mA/V. You may neglect their r_o's.

(a) Select a value for R_F that results in a closed-loop gain that is ideally 10 V/V.

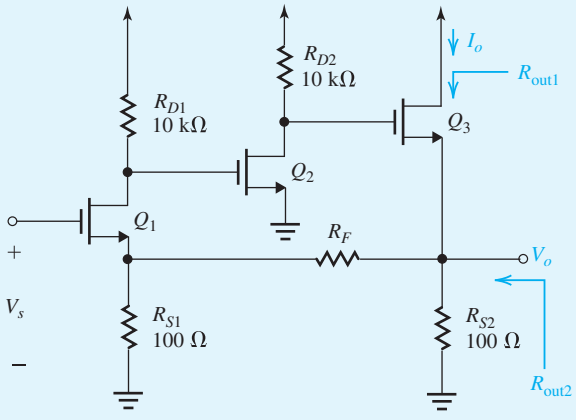


Figure P11.31

(b) Determine the loop gain $A\beta$ and hence the value of A_f. By what percentage does A_f differ from the ideal value you designed for? How can you adjust the circuit to make A_f equal to 10?

11.32 Figure P11.32 shows a series–shunt feedback amplifier without details of the bias circuit.

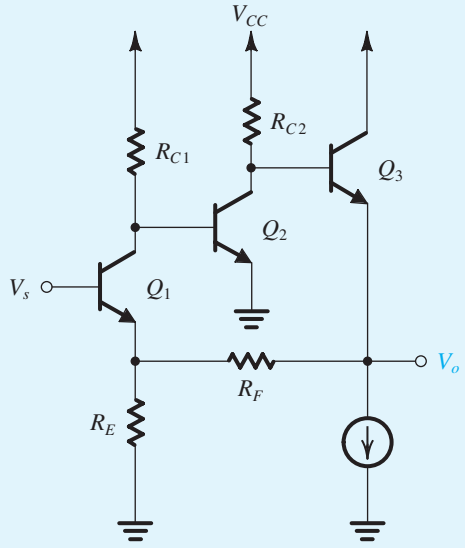


Figure P11.32

(a) If R_E is selected to be 50 Ω, find the value for R_F that results in a closed-loop gain with an ideal value of 25 V/V.

(b) If Q_1 is biased at 1 mA, Q_2 at 2 mA, and Q_3 at 5 mA, and assuming that the transistors have $h_{fe} = 100$ and large r_o, and that $R_{C1} = 2$ kΩ and $R_{C2} = 1$ kΩ, find the value of the loop gain $A\beta$ and hence of the closed-loop gain A_f.

D 11.33 The current-mirror-loaded differential amplifier in Fig. P11.33 has a feedback network consisting of the voltage divider (R_1, R_2), with $R_1 + R_2 = 1$ MΩ. The devices are sized to operate at $|V_{OV}| = 0.2$ V. For all devices, $|V_A| = 10$ V. The input signal source has a zero dc component.

(a) Find the loop gain $A\beta$ and hence the value of A.

(b) Find the values of R_1 and R_2 that result in a closed-loop gain of exactly 5 V/V.

Section 11.4: Systematic Analysis of Feedback Voltage Amplifiers (Series–Shunt)

11.34 A series–shunt feedback amplifier employs a basic amplifier with input and output resistances each of 2 kΩ and gain $A = 1000$ V/V. The feedback factor $\beta = 0.1$ V/V. Find

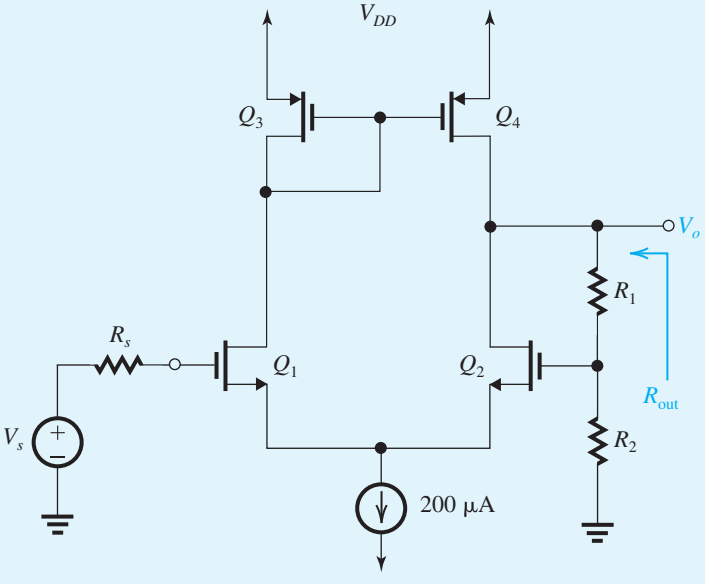


Figure P11.33

SIM = Multisim/PSpice; * = difficult problem; ** = more difficult; *** = very challenging; D = design problem

the gain A_f, the input resistance R_{if}, and the output resistance R_{of} of the closed-loop amplifier.

11.35 For a particular amplifier connected in a feedback loop in which the output voltage is sampled, measurement of the output resistance before and after the loop is connected shows a change by a factor of 200. Is the resistance with feedback higher or lower? What is the value of the loop gain $A\beta$? If R_{of} is 100 Ω, what is R_o without feedback?

11.36 The formulas for R_{if} and R_{of} in Eqs. (11.20) and (11.23), respectively, also apply for the case in which A is a function of frequency. In this case, the resulting impedances Z_{if} and Z_{of} will be functions of frequency. Consider the case of a series–shunt amplifier that has an input resistance R_i, an output resistance R_o, and open-loop gain $A = A_0/[1 + (s/\omega_H)]$, and a feedback factor β that is independent of frequency. Find Z_{if} and Z_{of} and give an equivalent circuit for each, together with the values of all the elements in the equivalent circuits.

11.37 A feedback amplifier utilizing voltage sampling and employing a basic voltage amplifier with a gain of 1000 V/V and an input resistance of 1000 Ω has a closed-loop input resistance of 10 kΩ. What is the closed-loop gain? If the basic amplifier is used to implement a unity-gain voltage buffer, what input resistance do you expect?

11.38 Consider the noninverting op-amp circuit of Example 11.4 for the case $R_1 = \infty$ and $R_2 = 0$.

(a) What is the value of β, and what is the ideal value of the closed-loop gain?
(b) Adapt the expressions found in Example 11.4 to obtain expressions for A and $A\beta$ for this case.
(c) For $\mu = 10^4$, $R_{id} = 100$ kΩ, $R_s = 10$ kΩ, $r_o = 1$ kΩ, and $R_L = 2$ kΩ, find A, $A\beta$, A_f, R_{in}, and R_{out}.

***11.39** This problem deals with the series–shunt feedback amplifier of Fig. P11.29 and overlaps somewhat with Problem 11.29. Thus, if you have already solved 11.29, you can use some of the results in the solution of this problem. The devices operate with $V_{BE} = 0.7$ V and have $\beta_1 = \beta_2 = 100$. The input signal V_s has a zero dc component. Resistances $R_s = 100$ Ω, $R_1 = 1$ kΩ, $R_2 = 10$ kΩ, and $R_L = 1$ kΩ.

(a) If the loop gain is large, what do you expect the closed-loop gain V_o/V_s to be? Give both an expression and its approximate value.
(b) Find the dc emitter current in each of Q_1 and Q_2. Also find the dc voltage at the emitter of Q_2.
(c) Sketch the A circuit without the dc sources. Derive expressions for A, R_i, and R_o, and find their values.
(d) Give an expression for β and find its value.
(e) Find the closed-loop gain V_o/V_s, the input resistance R_{in}, and the output resistance R_{out}. By what percentage does the value of A_f differ from the approximate value found in (a)?

SIM **D** ***11.40** Figure P11.40 shows a series–shunt amplifier with a feedback factor $\beta = 1$. The amplifier is designed so that $v_O = 0$ for $v_S = 0$, with small deviations in v_O from 0 V dc being minimized by the negative-feedback action. The technology utilized has $k_n' = 2k_p' = 120\ \mu\text{A/V}^2$, $|V_t| = 0.7$ V, and $|V_A'| = 24$ V/μm.

(a) Show that the feedback is negative.
(b) With the feedback loop opened at the gate of Q_2, and the gate terminals of Q_1 and Q_2 grounded, find the dc current and the overdrive voltage at which each of Q_1 to Q_5 is operating. Ignore the Early effect. Also find the dc voltage at the output.
(c) Find g_m and r_o of each of the five transistors.
(d) Find expressions and values of A and R_o. Assume that the bias current sources are ideal.
(e) Find the gain with feedback, A_f, and the output resistance R_{out}.
(f) How would you modify the circuit to realize a closed-loop voltage gain of 5 V/V? What is the value of output resistance obtained?

***11.41** Figure P11.41 shows a series–shunt amplifier in which the three MOSFETs are sized to operate at $|V_{OV}| = 0.2$ V. Let $|V_t| = 0.5$ V and $|V_A| = 10$ V. The current sources utilize single transistors and thus have output resistances equal to r_o.

(a) Show that the feedback is negative.
(b) Assuming the loop gain to be large, what do you expect the closed-loop voltage gain V_o/V_s to be approximately?
(c) If V_s has a zero dc component, find the dc voltages at nodes S_1, G_2, S_3, and G_3. Verify that each of the current sources has the minimum required dc voltage across it for proper operation.
(d) Find the A circuit. Calculate the gain of each of the three stages and the overall voltage gain, A.

SIM = Multisim/PSpice; * = difficult problem; ** = more difficult; *** = very challenging; D = design problem

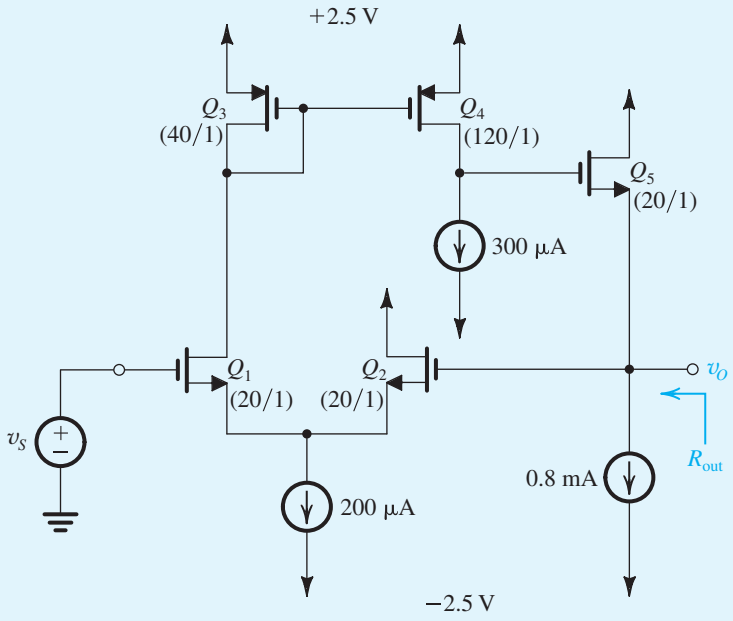


Figure P11.40

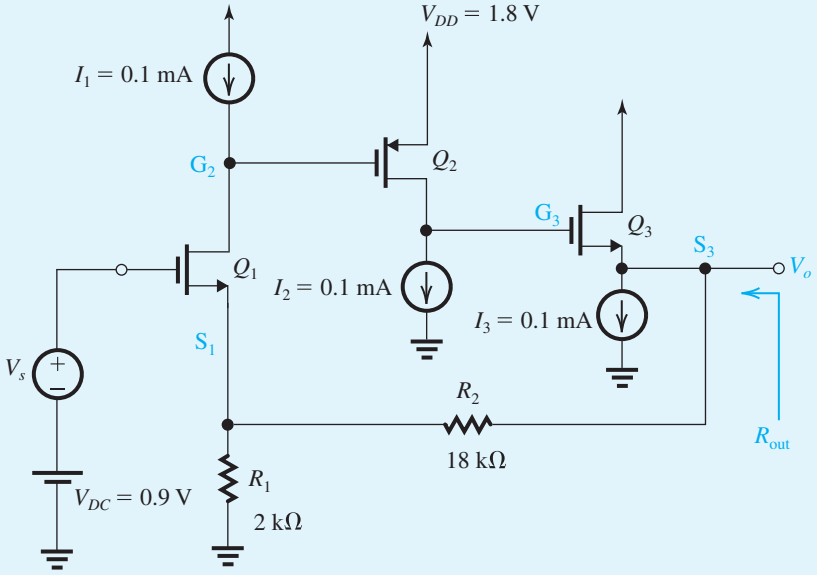


Figure P11.41

[*Hint*: A CS amplifier with a resistance R_s in the source lead has an effective transconductance $g_m/(1+g_mR_s)$ and an output resistance $r_o(1+g_mR_s)$.]

(e) Find β.

(f) Find $A_f = V_o/V_s$. By what percentage does this value differ from the approximate value obtained in (b)?

(g) Find the output resistance R_{out}.

SIM = Multisim/PSpice; * = difficult problem; ** = more difficult; *** = very challenging; D = design problem

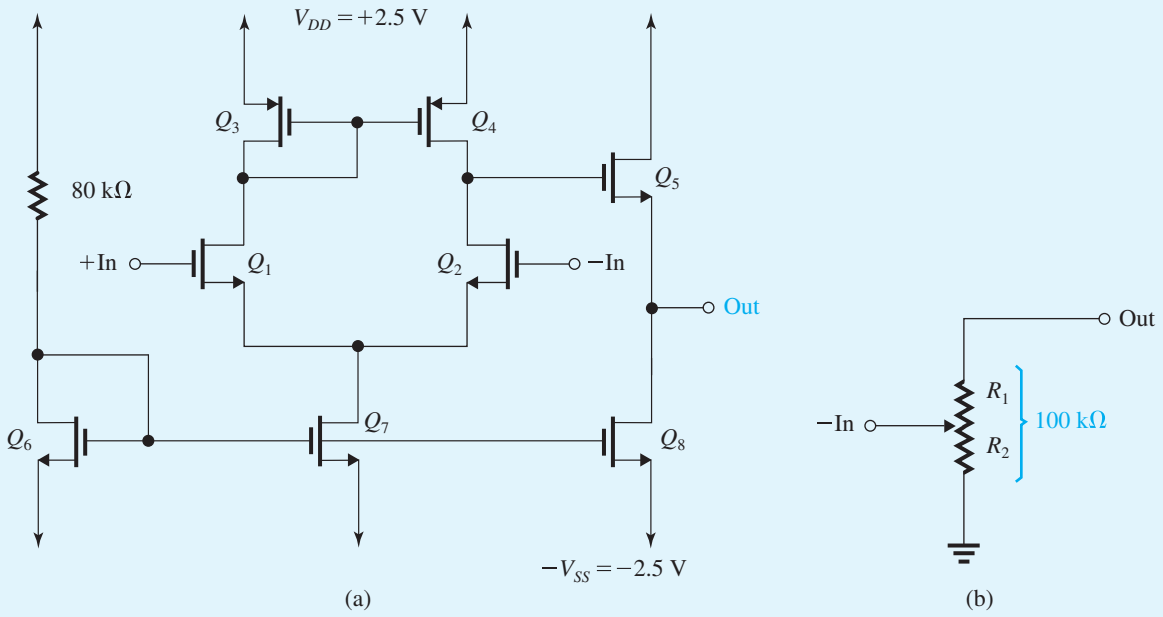


Figure P11.43

D *11.42 This problem deals with the series–shunt feedback amplifier of Fig. P11.33. Certain aspects of this amplifier were considered in Problem 11.33. If you have already solved problem 11.33, you will have the opportunity to compare results. The current-mirror-loaded differential amplifier has a feedback network consisting of the voltage divider (R_1, R_2), with $R_1 + R_2 = 1$ MΩ. The devices are sized to operate at $|V_{OV}| = 0.2$ V. For all devices, $|V_A| = 10$ V. The input signal source has a zero dc component.

(a) Show that the feedback is negative.
(b) What do you expect the dc voltage at the gate of Q_2 to be? At the output? (Neglect the Early effect.)
(c) Find the A circuit. Derive an expression for A and find its value.
(d) Select values for R_1 and R_2 to obtain a closed-loop voltage gain $V_o/V_s = 5$ V/V.
(e) Find the value of R_{out}.
(f) Utilizing the open-circuit, closed-loop gain (5 V/V) and the value of R_{out} found in (e), find the value of gain obtained when a resistance $R_L = 10$ kΩ is connected to the output.
(g) As an alternative approach to (f) above, redo the analysis of the A circuit including R_L. Then utilize the values of R_1 and R_2 found in (d) to determine β and A_f. Compare the value of A_f to that found in (f).

D **11.43 The CMOS op amp in Fig. P11.43(a) is fabricated in a 1-μm technology for which $V_{tn} = -V_{tp} = 0.75$ V, $\mu_n C_{ox} = 2\mu_p C_{ox} = 100$ μA/V^2, and $V_A' = 10$ V/μm. All transistors in the circuit have $L = 1$ μm.

(a) It is required to perform a dc bias design of the circuit. For this purpose, let the two input terminals be at zero volts dc and neglect channel-length modulation (i.e., let $V_A = \infty$). Design to obtain $I_{D1} = I_{D2} = 50$ μA, $I_{D5} = 250$ μA, and $V_O = 0$, and operate all transistors except for the source follower Q_5 at $V_{OV} = 0.25$ V. Assume that Q_1 and Q_2 are perfectly matched, and similarly for Q_3 and Q_4. For each transistor, find I_D and W/L.
(b) What is the allowable range of input common-mode voltage?
(c) Find g_m for each of Q_1, Q_2, and Q_5.
(d) For each transistor, calculate r_o.
(e) The 100-kΩ potentiometer shown in Fig. 11.43(b) is connected between the output terminal (Out) and the inverting input terminal (–In) to provide negative

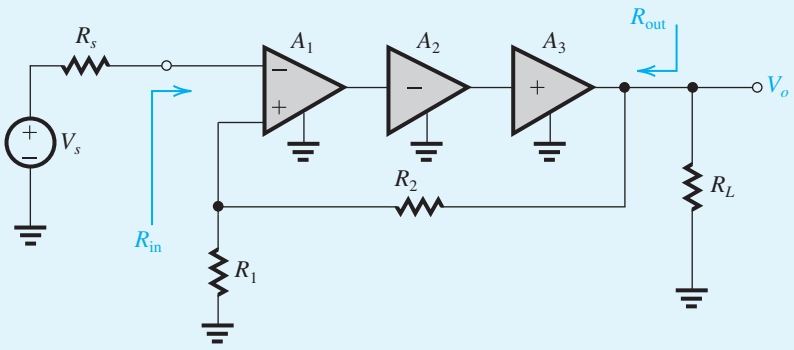


Figure P11.45

feedback whose amount is controlled by the setting of the wiper. A voltage signal V_s is applied between the noninverting input (+In) and ground. A load resistance $R_L = 100$ kΩ is connected between the output terminal and ground. The potentiometer is adjusted to obtain a closed-loop gain $A_f \equiv V_o/V_s \simeq 10$ V/V.

Specify the required setting of the potentiometer by giving the values of R_1 and R_2. Toward this end, find the A circuit (supply a circuit diagram), the value of A, the β circuit (supply a circuit diagram), and the value of β.

(f) What is the output resistance of the feedback amplifier, excluding R_L?

D ***11.44** Figure P11.32 shows a series–shunt feedback amplifier without details of the bias circuit.

(a) Eliminating the dc sources, sketch the A circuit and the circuit for determining β.

(b) Show that if $A\beta$ is large then the closed-loop voltage gain is given approximately by

$$A_f \equiv \frac{V_o}{V_s} \simeq \frac{R_F + R_E}{R_E}$$

(c) If R_E is selected equal to 50 Ω, find R_F that will result in a closed-loop gain of approximately 25 V/V.

(d) If Q_1 is biased at 1 mA, Q_2 at 2 mA, and Q_3 at 5 mA, and assuming that the transistors have $h_{fe} = 100$, find approximate values for R_{C1} and R_{C2} to obtain gains from the stages of the A circuit as follows: a voltage gain of Q_1 of about –10 and a voltage gain of Q_2 of about –50.

(e) For your design, what is the closed-loop voltage gain realized?

(f) Calculate the input and output resistances of the closed-loop amplifier designed.

D ***11.45** Figure P11.45 shows a three-stage feedback amplifier:

A_1 has an 82-kΩ differential input resistance, a 20-V/V open-circuit differential voltage gain, and a 3.2-kΩ output resistance.

A_2 has a 5-kΩ input resistance, a 20-mA/V short-circuit transconductance, and a 20-kΩ output resistance.

A_3 has a 20-kΩ input resistance, unity open-circuit voltage gain, and a 1-kΩ output resistance.

The feedback amplifier feeds a 1-kΩ load resistance and is fed by a signal source with a 9-kΩ resistance.

(a) Show that the feedback is negative.

(b) If $R_1 = 20$ kΩ, find the value of R_2 that results in a closed-loop gain V_o/V_s that is ideally 5 V/V.

(c) Supply the small-signal equivalent circuit.

(d) Sketch the A circuit and determine A.

(e) Find β and the amount of feedback.

(f) Find the closed-loop gain $A_f \equiv V_o/V_s$.

(g) Find the feedback amplifier's input resistance R_{in}.

(h) Find the feedback amplifier's output resistance R_{out}.

(i) If the high-frequency response of the open-loop gain A is dominated by a pole at 100 Hz, what is the upper 3-dB frequency of the closed-loop gain?

(j) If for some reason A_1 drops to half its nominal value, what is the percentage change in A_f?

Section 11.5: Other Feedback-Amplifier Types

D 11.46 Refer to the circuit in Fig. 11.17(a), which is analyzed in Example 11.6. Select a value for R_F that results in a closed-loop transconductance $A_f \equiv I_o/V_s \simeq 10$ mA/V. Use the formulas derived in Example 11.6 to find the actual value of A_f realized. Let $\mu = 1000$, $R_{id} = 100\,\text{k}\Omega$, $g_m = 2$ mA/V, and $r_{o2} = 20\,\text{k}\Omega$.

D 11.47 Figure P11.47 shows a feedback current amplifier. The feedback network consists of the highlighted two-port network comprising R_M and R_F. It is fed with the output current I_o and delivers a feedback current I_f at its port 1 to the input node. The feedback factor β is the current ratio I_f/I_o measured with port 1 short-circuited (because it is connected in shunt with the amplifier input).

(a) Find an expression for β and hence for the ideal value of $A_f \equiv I_o/I_s$.

(b) Setting $I_s = 0$, break the loop at the gate of Q_2 and thus determine the loop gain $A\beta$. Show that

$$A = -\frac{g_{m2}R_D}{1 + 1/[g_{m1}(R_M + R_F)]}$$

(c) For $g_{m1} = g_{m2} = 4$ mA/V, $R_D = 10\,\text{k}\Omega$, and $(R_M + R_F) = 1\,\text{k}\Omega$, find the value of R_M that results in a closed-loop current gain of 5 A/A.

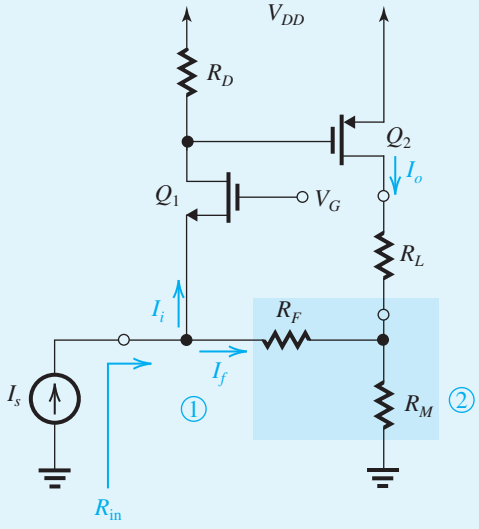


Figure P11.47

D 11.48 Figure P11.48(a) shows a feedback transresistance amplifier formed by an op amp and a feedback resistance R_F. Assume that the op amp is modeled by an input resistance R_{id}, an open-circuit voltage gain μ, and an output resistance r_o.

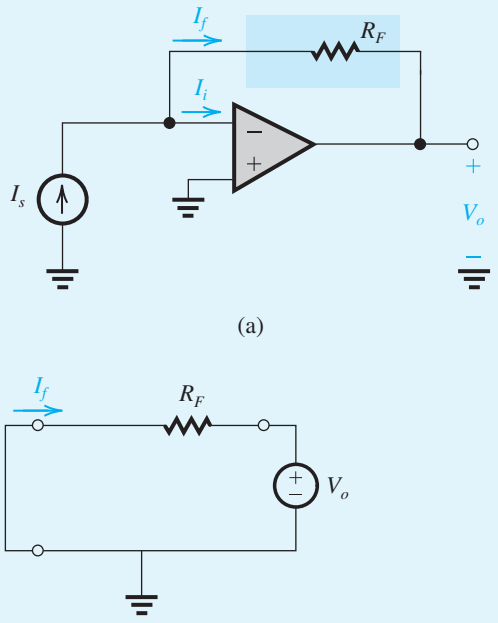


Figure P11.48

(a) Show that the feedback factor β, determined as shown in Fig. P11.48(b), is given by $\beta = -1/R_F$. Hence find the ideal value of the closed-loop gain $A_f \equiv V_o/I_s$. Find R_F that results in A_f of approximately 1 kΩ.

(b) By setting $I_s = 0$ and breaking the loop at the input terminals of the op amp, show that the loop gain is given by

$$A\beta = \mu \frac{R_{id}}{R_{id} + R_F + r_o}$$

(c) For $\mu = 1000$, $R_{id} = 100\,\text{k}\Omega$, $r_o = 1\,\text{k}\Omega$, and R_F having the value found in (a), what is the actual value of A_f realized?

Feedback Transconductance Amplifiers (Series–Series)

11.49 A series–series feedback amplifier employs a transconductance amplifier having a short-circuit transconductance G_m of 0.6 A/V, input resistance of 10 kΩ, and output resistance of 100 kΩ. The feedback network has $\beta = 200\ \Omega$,

an input resistance (with port 1 open-circuited) of 200 Ω, and an input resistance (with port 2 open-circuited) of 10 kΩ. The amplifier operates with a signal source having a resistance of 10 kΩ and with a load resistance of 10 kΩ. Find A_f, R_{in}, and R_{out}.

11.50 Reconsider the circuit in Fig. 11.21(a), analyzed in Example 11.8, this time with the output voltage taken at the emitter of Q_3. In this case the feedback can be considered to be of the series–shunt type. Note that R_{E2} should now be considered part of the basic amplifier and not of the feedback network.

(a) Determine β.
(b) Find an approximate value for $A_f \equiv V_{e3}/V_s$ assuming that the loop gain remains large (a safe assumption, since the loop in fact does not change).
[*Note*: If you continue with the feedback analysis, you'll find that $A\beta$ in fact changes somewhat; this is a result of the different approximations made in the feedback analysis approach.]
(c) If the loop gain remains at the value calculated in Example 11.8 (i.e., 246.3), find the output resistance R_{out} (measured between the emitter of Q_3 and ground). (Neglect the effect of r_{03}.)

D ***11.51** Figure P11.31 (page 851) shows a feedback triple utilizing MOSFETs. All three MOSFETs are biased and sized to operate at $g_m = 4$ mA/V. You may neglect their r_o's (except for the calculation of R_{out1} as indicated below).

(a) Considering the feedback amplifier as a transconductance amplifier with output current I_o, find the value of R_F that results in a closed-loop transconductance of approximately 100 mA/V.
(b) Sketch the A circuit and find the value of $A \equiv I_o/V_i$.
(c) Find $1 + A\beta$ and $A_f \equiv I_o/V_s$. Compare to the value of A_f you designed for. What is the percentage difference? What resistance can you change to make A_f exactly 100 mA/V, and in which direction (increase or decrease)?
(d) Assuming that $r_{o3} = 20$ kΩ, find R_o of the A circuit. For this purpose, recall that the resistance looking into the drain of a MOSFET having a resistance R_s in its source is $(r_o + R_s + g_m r_o R_s)$. Hence find the output resistance R_{out1}. Since the current sampled by the feedback network is exactly equal to the output current, you can use the feedback formula.
(e) If the voltage V_o is taken as the output, in which case the amplifier becomes series–shunt feedback, what is the value of the closed-loop voltage gain V_o/V_s? Assume that R_F has the original value you selected in (a). Note that in this case R_{S2} should be considered part of the amplifier and not the feedback network. The feedback analysis will reveal that $A\beta$ changes somewhat, which may be puzzling given that the feedback loop did not change. The change is due to the different approximation used.
(f) What is the closed-loop output resistance R_{out2} of the voltage amplifier in (e) above?

11.52 Consider the circuit in Fig. P11.52 as a transconductance amplifier with input V_s and output I_o. The transistor is specified in terms of its g_m and r_o.

(a) Sketch the small-signal equivalent circuit using the hybrid-π model of the MOSFET and convince yourself that the feedback circuit is comprised of resistor R_F.
(b) Find the A circuit and the β circuit.
(c) Derive expressions for A, β, $(1 + A\beta)$, A_f, R_o, and R_{of}.

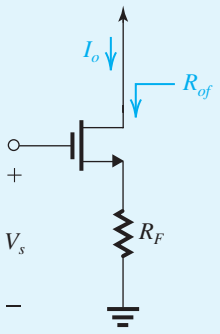


Figure P11.52

D **11.53** The transconductance amplifier in Fig. P11.53 utilizes a differential amplifier with gain μ and a very high input resistance. The differential amplifier drives a transistor Q characterized by its g_m and r_o. A resistor R_F senses the output current I_o.

(a) For $A\beta \gg 1$, find an approximate expression for the closed-loop transconductance $A_f \equiv I_o/V_s$. Hence, select a value for R_F that results in $A_f \simeq 5$ mA/V.
(b) Find the A circuit and derive an expression for A. Evaluate A for the case $\mu = 1000$ V/V, $g_m = 2$ mA/V, $r_o = 20$ kΩ, and the value of R_F you selected in (a).
(c) Give an expression for $A\beta$ and evaluate its value and that of $1 + A\beta$.

(d) Find the closed-loop gain A_f and compare to the value you designed for in (a) above.

(e) Find expressions and values for R_o and R_{of}. [*Hint*: The resistance looking into the drain of a MOSFET with a resistance R_s in its source is $(r_o + R_s + g_m r_o R_s)$.]

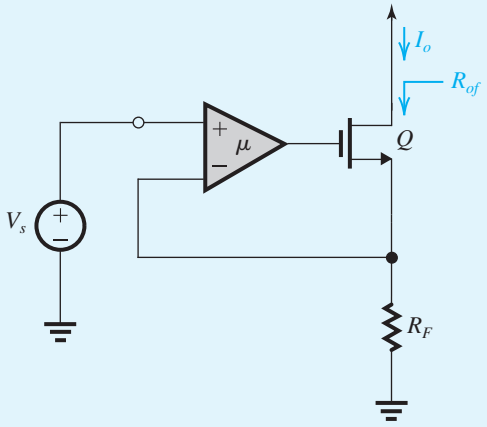


Figure P11.53

***11.54** It is required to show that the output resistance of the BJT circuit in Fig. P11.54 is given by

$$R_o = r_o + \left[R_e \| \left(r_\pi + R_b\right)\right]\left(1 + g_m r_o \frac{r_\pi}{r_\pi + R_b}\right)$$


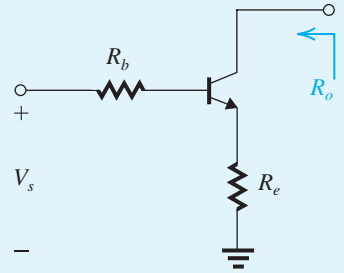



Figure P11.54

To derive this expression, set $V_s = 0$, replace the BJT with its small-signal, hybrid-π model, apply a test voltage V_x to the collector, and find the current I_x drawn from V_x and hence R_o as V_x/I_x. Note that the bias arrangement is not shown. For the case of $R_b = 0$, find the maximum possible value for R_o. Note that this theoretical maximum is obtained when R_e is so large that the signal current in the emitter is nearly zero. In this case, with V_x applied and $V_s = 0$, what is the current in the base, in the $g_m V_\pi$ generator, and in r_o, all in terms of I_x? Show these currents on a sketch of the equivalent circuit with R_e set to ∞.

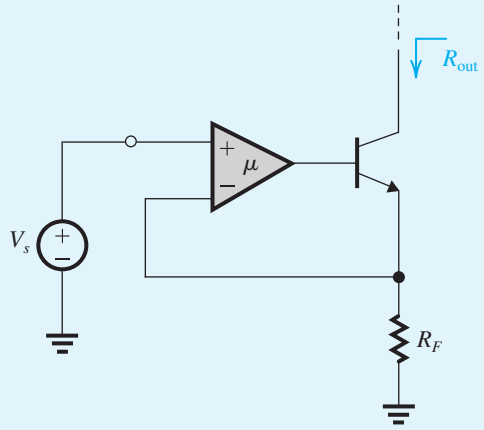11.55 As we found out in Example 11.8, whenever the feedback network senses the emitter current of the BJT, the feedback output resistance formula cannot predict the output resistance looking into the collector. To understand this issue more clearly, consider the feedback transconductance amplifier shown in Fig. P11.55(a). To determine the output resistance, we set $V_s = 0$ and apply a test voltage V_x to the collector, as shown in Fig. P11.55(b). Now, let μ be increased to the point where the feedback signal across R_F almost equals the input to the positive terminal of the differential amplifier,



(a)

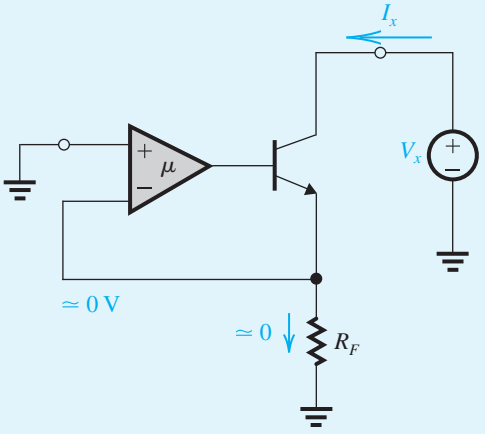

(b)

Figure P11.55

SIM = Multisim/PSpice; * = difficult problem; ** = more difficult; *** = very challenging; D = design problem

now zero. Thus the signal current through R_F will be almost zero. By replacing the BJT with its hybrid-π model, show that

$$R_{\text{out}} = r_\pi + (h_{fe} + 1)r_o \simeq h_{fe} r_o$$

where h_{fe} is the transistor β. Thus for large amounts of feedback, R_{out} is limited to a maximum of $h_{fe} r_o$ independent of the amount of feedback. This phenomenon does *not* occur in the MOSFET version of this circuit, where the output resistance can be theoretically made infinite.

11.56 For the feedback transconductance amplifier of Fig. P11.56 derive expressions for A, β, $A\beta$, A_f, R_o, and R_{of}. Evaluate A_f and R_{of} for the case of $g_{m1} = g_{m2} = 4$ mA/V, $R_D = 20$ kΩ, $r_{o2} = 20$ kΩ, $R_F = 100$ Ω, and $R_L = 1$ kΩ. For simplicity, neglect r_{o1} and take r_{o2} into account only when calculating output resistances.

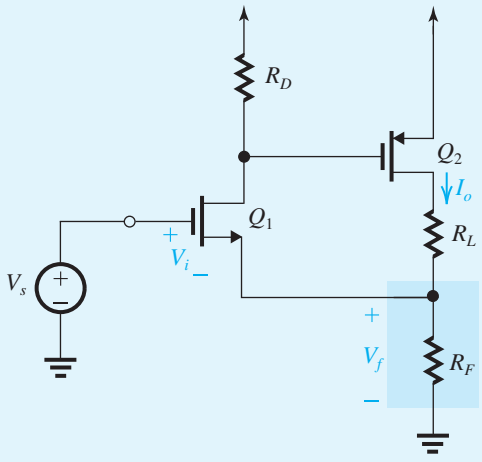


Figure P11.56

D 11.57 For the feedback transconductance amplifier in Fig. P11.57, derive an approximate expression for the closed-loop transconductance $A_f \equiv I_o/V_s$ for the case of $A\beta \gg 1$. Hence select a value for R_2 to obtain $A_f = 100$ mA/V. If Q is biased to obtain $g_m = 1$ mA/V, specify the value of the gain μ of the differential amplifier to obtain an amount of feedback of 60 dB. If Q has $r_o = 50$ kΩ, find the output resistance R_{out}. [*Hint*: Recall that for a MOSFET with a resistance R_s in its source, the resistance looking into the drain is $(r_o + R_s + g_m r_o R_s)$.]

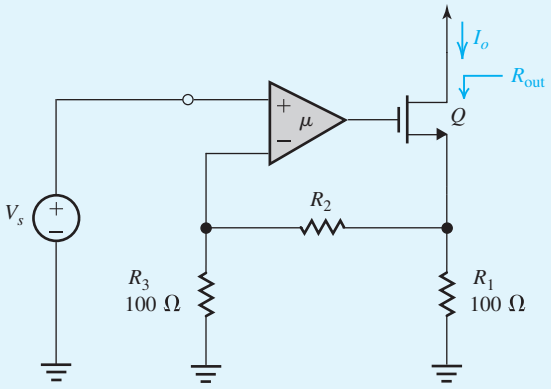


Figure P11.57

SIM **11.58** All the MOS transistors in the feedback transconductance amplifier (series–series) of Fig. P11.58 are sized to operate at $|V_{OV}| = 0.2$ V. For all transistors, $|V_t| = 0.4$ V and $|V_A| = 20$ V.

(a) If V_s has a zero dc component, find the dc voltage at the output, at the drain of Q_1, and at the drain of Q_2.
(b) Find an approximate expression and value for $A_f \equiv I_o/V_s$ for the case $A\beta \gg 1$.
(c) Use feedback analysis to obtain a more precise value for A_f.
(d) Find the value of R_{out}.
(e) If the voltage at the source of Q_5 is taken as the output, find the voltage gain using the value of I_o/V_s obtained in (c). Also find the output resistance of this series–shunt voltage amplifier.

11.59 By setting $V_s = 0$ and breaking the feedback loop, show that the loop gain of the amplifier circuit in Fig. P11.58 is

$$A\beta = g_{m1,2}(r_{o2} \parallel r_{o4}) \frac{R_F \parallel r_{o5}}{(R_F \parallel r_{o5}) + 1/g_{m5}}$$

where $g_{m1,2}$ is the g_m of each of Q_1 and Q_2.

Feedback Transresistance Amplifiers (Shunt–Shunt)

11.60 For the transresistance amplifier analyzed in Example 11.9, use the formulas derived there to evaluate A_f, R_{in}, and R_{out} when μ is one-tenth the value used in the example. That is, evaluate for $\mu = 10^3$ V/V, $R_{id} = \infty$, $r_o = 100\,\Omega$, $R_F = 10$ kΩ, and $R_s = R_L = 1$ kΩ. Compare to the corresponding values obtained in Example 11.9.

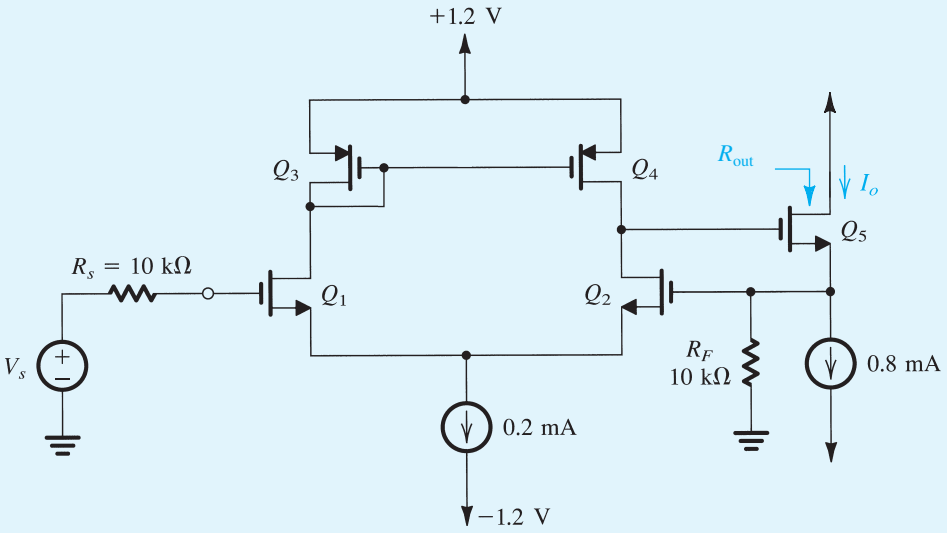


Figure P11.58

11.61 Use the formulas derived in Example 11.9 to solve the problem in Exercise 11.19. Show that the results are identical to those given in the answer to Exercise 11.19.

11.62 By setting $I_s = 0$, replacing the MOSFET with its hybrid-π model, and breaking the feedback loop, determine the loop gain of the feedback amplifier in Fig. E11.19. Hence find the open-loop gain. Evaluate $A\beta$, β, A, and A_f for the numerical values given in Exercise 11.8. Why do the results differ somewhat from those given in the answer to Exercise 11.19?

11.63 The CE BJT amplifier in Fig. P11.63 employs shunt–shunt feedback: Feedback resistor R_F senses the output voltage V_o and provides a feedback current to the base node.

(a) If V_s has a zero dc component, find the dc collector current of the BJT. Assume the transistor $\beta = 100$.
(b) Find the small-signal equivalent circuit of the amplifier with the signal source represented by its Norton equivalent (as we usually do when the feedback connection at the input is shunt).
(c) Find the A circuit and determine the value of A, R_i, and R_o.
(d) Find β and hence $A\beta$ and $1 + A\beta$.
(e) Find A_f, R_{if}, and R_{of} and hence R_{in} and R_{out}.
(f) What voltage gain V_o/V_s is realized? How does this value compare to the ideal value obtained if the loop gain is very large and thus the signal voltage at the base becomes almost zero (like what happens in an inverting op-amp circuit). Note that this single-transistor poor-man's op amp is not that bad!

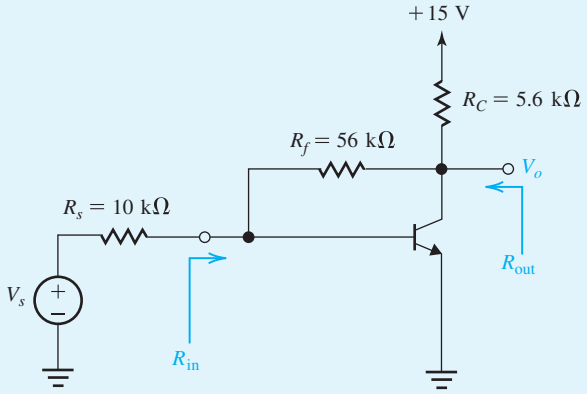


Figure P11.63

SIM = Multisim/PSpice; * = difficult problem; ** = more difficult; *** = very challenging; D = design problem

D 11.64 The circuit in Fig. P11.64 utilizes a voltage amplifier with gain μ in a shunt–shunt feedback topology with the feedback network composed of resistor R_F. In order to be able to use the feedback equations, you should first convert the signal source to its Norton representation. You will then see that all the formulas derived in Example 11.9 apply here as well.

(a) If the loop gain is very large, what approximate closed-loop voltage gain V_o/V_s is realized? If $R_s = 2\ \text{k}\Omega$, give the value of R_F that will result in $V_o/V_s \simeq -10$ V/V.
(b) If the amplifier μ has a dc gain of 10^3 V/V, an input resistance $R_{id} = 100\ \text{k}\Omega$, and an output resistance $r_o = 2\ \text{k}\Omega$, find the actual V_o/V_s realized. Also find R_{in} and R_{out} (indicated on the circuit diagram). You may use formulas derived in Example 11.9.
(c) If the amplifier μ has an upper 3-dB frequency of 1 kHz and a uniform −20-dB/decade gain rolloff, what is the 3-dB frequency of the gain $|V_o/V_s|$?

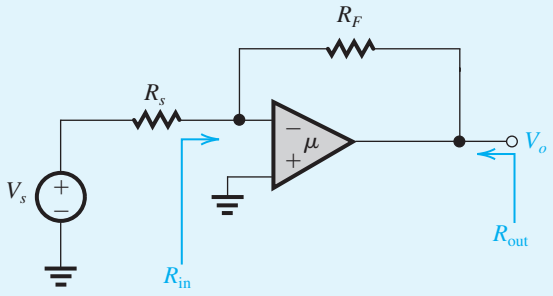


Figure P11.64

11.65 The feedback transresistance amplifier in Fig. P11.65 utilizes two identical MOSFETs biased by ideal current sources $I = 0.4$ mA. The MOSFETs are sized to operate at $V_{OV} = 0.2$ V and have $V_t = 0.5$ V and $V_A = 16$ V. The feedback resistance $R_F = 10\ \text{k}\Omega$.

(a) If I_s has a zero dc component, find the dc voltage at the input, at the drain of Q_1, and at the output.
(b) Find g_m and r_o of Q_1 and Q_2.
(c) Provide the A circuit and derive an expression for A in terms of g_{m1}, r_{o1}, g_{m2}, r_{o2}, and R_F.
(d) What is β? Give an expression for the loop gain $A\beta$ and the amount of feedback $(1 + A\beta)$.
(e) Derive an expression for A_f.
(f) Derive expressions for R_i, R_{in}, R_o, and R_{out}.
(g) Evaluate A, β, $A\beta$, A_f, R_i, R_o, R_{in}, and R_{out} for the component values given.

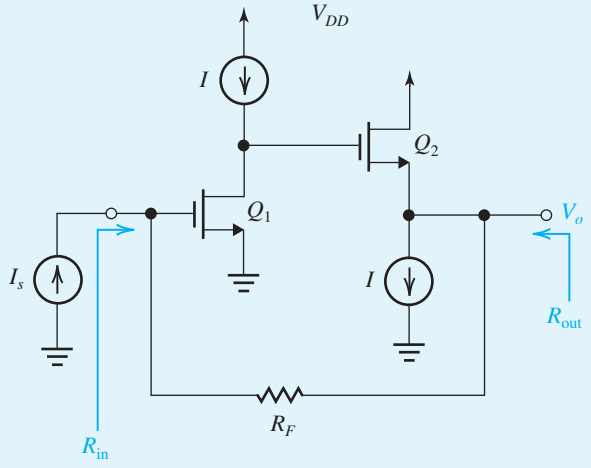


Figure P11.65

11.66 By setting $I_s = 0$ and breaking the feedback loop, find the loop gain of the feedback amplifier in Fig. P11.65. If you have already solved Problem 11.65, compare results. Which result do you think is more accurate, and why? For the numerical values given in Problem 11.65, by how much (in percent) do the two values of loop gain differ?

11.67 Analyze the circuit in Fig. E11.19 from first principles (i.e., do not use the feedback approach) and hence show that

$$A_f \equiv \frac{V_o}{I_s} = -\frac{(R_s \parallel R_F)\left(g_m - \dfrac{1}{R_F}\right)(r_o \parallel R_F)}{1 + (R_s \parallel R_F)\left(g_m - \dfrac{1}{R_F}\right)(r_o \parallel R_F)/R_F}$$

Comparing this expression to the one given in Exercise 11.19, part (b), you will note that the only difference is that g_m has been replaced by $(g_m - 1/R_F)$. Note that $-1/R_F$ represents the forward transmission in the feedback network, which the feedback-analysis method neglects. What is the condition then for the feedback-analysis method to be reasonably accurate for this circuit?

D 11.68 For the feedback amplifier in Fig. P11.68, select a value for R_F that results in a closed-loop gain $A_f \equiv V_o/I_s \simeq -10$ kΩ. Then, analyze the circuit to determine the actual value of A_f realized. As well, determine R_{in} and R_{out}. Transistors Q_1 and Q_2 are operated so that $g_{m1} = g_{m2} = 4$ mA/V and r_{o1} and r_{o2} can be neglected. Also, $R_{D1} = R_{D2} = 10$ kΩ.

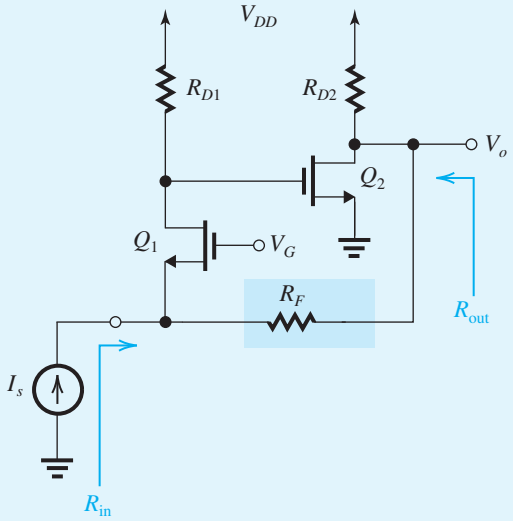


Figure P11.68

11.69 For the feedback transresistance amplifier in Fig. P11.69, let $V_{CC} = -V_{EE} = 5$ V, $R_C = R_E = R_F = 10$ kΩ. The transistors have $V_{BE} = 0.7$ V and $\beta = 100$.

(a) If I_s has a zero dc component, show that Q_1 and Q_2 are operating at dc collector currents of approximately 0.35 mA and 0.58 mA, respectively. What is the dc voltage at the output?

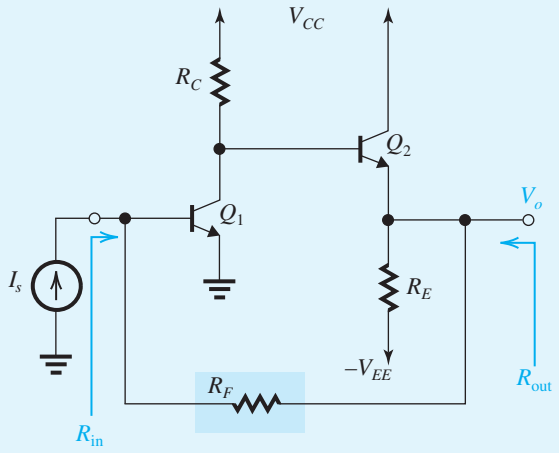


Figure P11.69

(b) Find the A circuit and the value of A, R_i, and R_o. Neglect r_{o1} and r_{o2}.


(c) Find the value of β, the loop gain, and the amount of feedback.

(d) Find $A_f \equiv V_o/I_s$, the input resistance R_{in}, and the output resistance R_{out}.


D **11.70 (a) Show that for the circuit in Fig. P11.70(a), if the loop gain is large, the voltage gain V_o/V_s is given approximately by

$$\frac{V_o}{V_s} \simeq -\frac{R_f}{R_s}$$

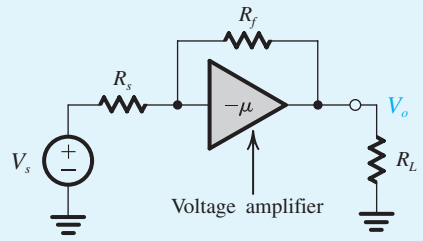(b) Using three cascaded stages of the type shown in Fig. P11.70(b) to implement the amplifier μ, design a feedback amplifier with a voltage gain of approximately –100 V/V. The amplifier is to operate between a source resistance $R_s = 10$ kΩ and a load resistance $R_L = 1$ kΩ. Calculate the actual value of V_o/V_s realized, the input resistance (excluding R_s), and the output resistance (excluding R_L). Assume that the BJTs have h_{fe} of 100. [*Note:* In practice, the three amplifier stages are not made identical, for stability reasons.]



(a)

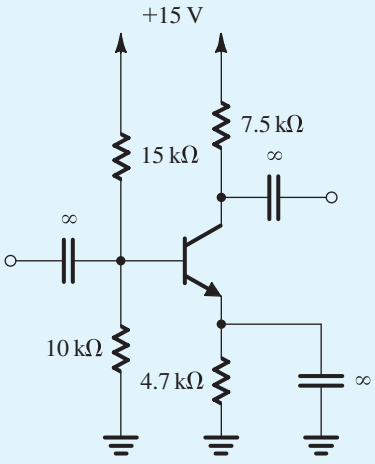

(b)

Figure P11.70

D 11.71 Negative feedback is to be used to modify the characteristics of a particular amplifier for various purposes. Identify the feedback topology to be used if:

(a) input resistance is to be lowered and output resistance raised.
(b) both input and output resistances are to be raised.
(c) both input and output resistances are to be lowered.

11.72 The feedback amplifier of Fig. P11.72 consists of a common-gate amplifier formed by Q_1 and R_D, and a feedback circuit formed by the capacitive divider (C_1, C_2) and the common-source transistor Q_f. Note that the bias circuit for Q_f is not shown. It is required to derive expressions for $A_f \equiv V_o/I_s$, R_{in}, and R_{out}. Assume that C_1 and C_2 are sufficiently small that their loading effect on the basic amplifier can be neglected. Also neglect r_o. Find the values of A_f, R_{in}, and R_{out} for the case in which $g_{m1} = 5$ mA/V, $R_D = 10$ kΩ, $C_1 = 0.9$ pF, $C_2 = 0.1$ pF, and $g_{mf} = 2$ mA/V.

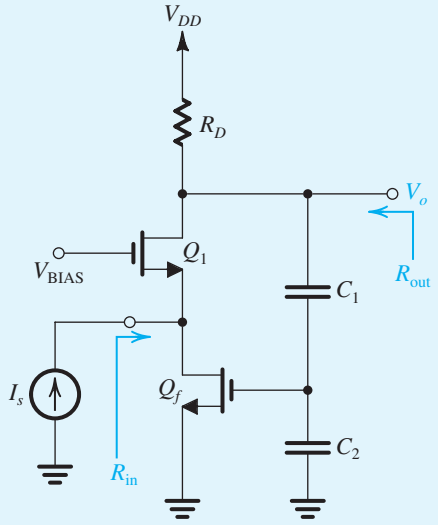


Figure P11.72

D *11.73 Figure P11.73 shows a shunt–shunt feedback amplifier. The MOSFETs have $V_{tn} = 0.6$ V, $V_A = 20$ V, and $\mu_n C_{ox} = 200\ \mu\text{A/V}^2$. The power supply $V_{DD} = 3.3$ V, and $R_L = 2$ kΩ. The coupling capacitor C_C can be assumed to be very large.

(a) Perform a dc design to meet the following specifications: $I_{D1} = 100\ \mu$A, $I_{D2} = 1$ mA, $I_{R2,R1} = 10\ \mu$A, $V_{OV1} = V_{OV2} = 0.2$ V. Neglect the Early effect. Specify the values required for I_1, R_1, R_2, $(W/L)_1$, and $(W/L)_2$.
(b) Find an expression for β and hence an expression for the ideal value of V_o/V_s.
(c) Find the value of R_s that results in V_o/V_s being ideally −6 V/V.

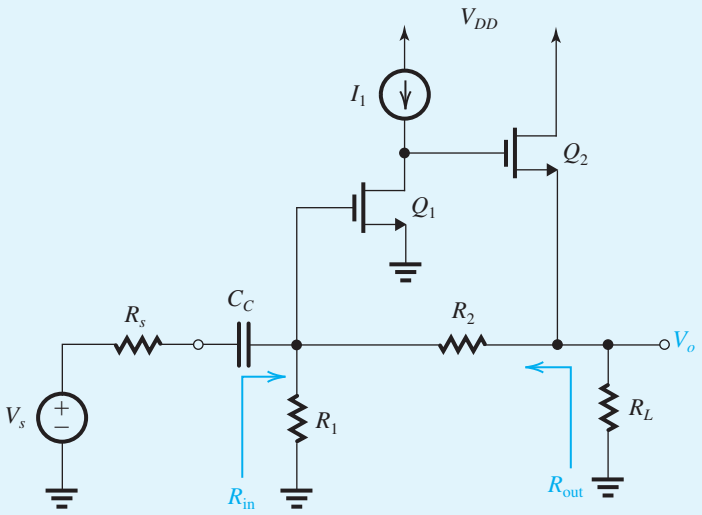


Figure P11.73

(d) Find the A circuit and use it to determine the values of A, R_i, and R_o.
(e) Find the value obtained for V_o/V_s.
(f) Find R_{in} and R_{out}.

Feedback Current Amplifiers (Shunt–Series)

11.74 For the feedback current amplifier in Fig. P11.47:

(a) Provide the A circuit and derive expressions for R_i and A. Neglect r_o of both transistors.
(b) Provide the β circuit and an expression for β.
(c) Find an expression for $A\beta$.
(d) For $g_{m1} = g_{m2} = 5$ mA/V, $R_D = 20$ kΩ, $R_M = 10$ kΩ, and $R_F = 90$ kΩ, find the values of A, β, $A\beta$, A_f, R_i, and R_{if}.
(e) If $r_{o2} = 20$ kΩ and $R_L = 1$ kΩ, find the output resistance as seen by R_L.

D 11.75 Design the feedback current amplifier of Fig. 11.27(a) to meet the following specifications:

(i) $A_f \equiv I_o/I_s = -100$ A/A
(ii) amount of feedback $\simeq 40$ dB
(iii) $R_{in} \simeq 1$ kΩ

Specify the values of R_1, R_2, and μ. Assume that the amplifier μ has infinite input resistance and that $R_s = \infty$. For the MOSFET, $g_m = 5$ mA/V and $r_o = 20$ kΩ. What R_{out} is obtained?

11.76 Consider the feedback current amplifier in Fig. 11.27(a) (which was analyzed in Example 11.10). Let $R_s = R_{id} = \infty$. By setting $I_s = 0$ and breaking the feedback loop at the gate of Q, find an expression for the loop gain $A\beta$. Evaluate $A\beta$ for the component values given in Example 11.10 and hence determine A and A_f. Why do the results differ somewhat from those found in Example 11.10?

11.77 The feedback current amplifier in Fig. P11.77 utilizes two identical NMOS transistors sized so that at $I_D = 0.2$ mA they operate at $V_{OV} = 0.2$ V. Both devices have $V_t = 0.5$ V and $V_A = 10$ V.

(a) If I_s has zero dc component, show that both Q_1 and Q_2 are operating at $I_D = 0.2$ mA. What is the dc voltage at the input?
(b) Find g_m and r_o for each of Q_1 and Q_2.
(c) Find the A circuit and the value of R_i, A, and R_o.
(d) Find the value of β.
(e) Find $A\beta$ and A_f.
(f) Find R_{in} and R_{out}.

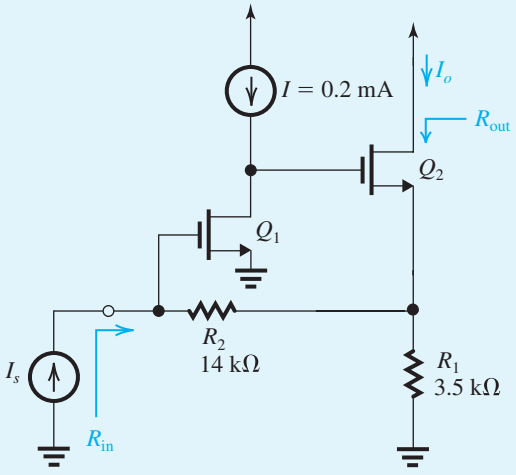


Figure P11.77

***11.78** The feedback current amplifier in Fig. P11.78(a) can be thought of as a "super" CG transistor. Note that rather than connecting the gate of Q_2 to signal ground, an amplifier is placed between source and gate.

(a) If μ is very large, what is the signal voltage at the input terminal? What is the input resistance? What is the current gain I_o/I_s?
(b) For finite μ but assuming that the input resistance of the amplifier μ is very large, find the A circuit and derive expressions for A, R_i, and R_o.
(c) What is the value of β?
(d) Find $A\beta$ and A_f. If μ is large, what is the value of A_f?
(e) Find R_{in} and R_{out} assuming the loop gain is large.
(f) The "super" CG transistor can be utilized in the cascode configuration shown in Fig. P11.78(b), where V_G is a dc bias voltage. Replacing Q_1 by its small-signal model, use the analogy of the resulting circuit to that in Fig. P11.78(a) to find I_o and R_{out}.

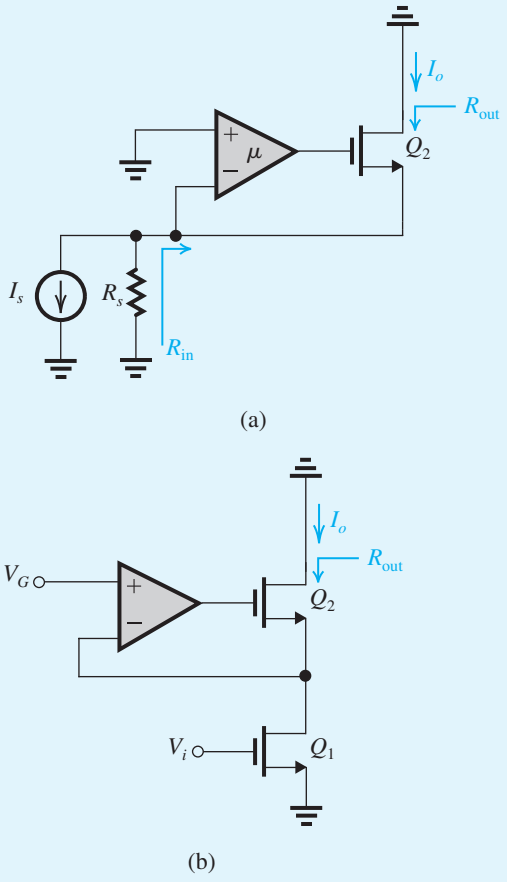


Figure P11.78

***11.79** Figure P11.79 shows an interesting and very useful application of feedback to improve the performance of the current mirror formed by Q_1 and Q_2. Rather than connecting the drain of Q_1 to the gate, as is the case in simple current mirrors, an amplifier of gain $+\mu$ is connected between the drain and the gate. Note that the feedback loop does not include transistor Q_2. The feedback loop ensures that the value of the gate-to-source voltage of Q_1 is such that I_{o1} equals I_s. This regulated V_{gs} is also applied to Q_2. Thus, if W/L of Q_2 is n times W/L of Q_1, $I_{o2} = nI_{o1} = nI_s$. This current tracking, however, is *not* regulated by the feedback loop.

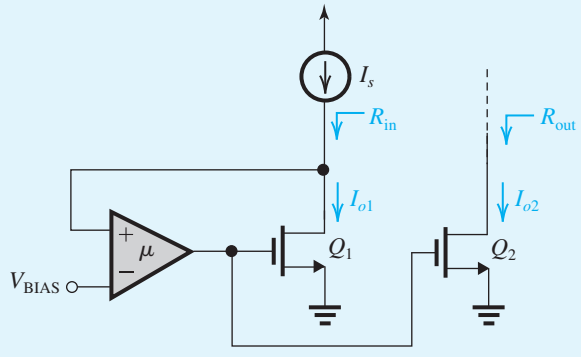


Figure P11.79

SIM = Multisim/PSpice; * = difficult problem; ** = more difficult; *** = very challenging; D = design problem

(a) Show that the feedback is negative.
(b) If μ is very large and the input resistance of the amplifier μ is infinite, what dc voltage appears at the drain of Q_1? If Q_1 is to operate at an overdrive voltage of 0.2 V, what is the minimum value that V_{BIAS} must have?
(c) Replacing Q_1 by its small-signal model, find an expression for the small-signal input resistance R_{in} assuming finite gain but infinite input resistance for the amplifier μ. Note that here it is much easier to do the analysis directly than to use the feedback-analysis approach. For large μ, what does R_{in} become?
(d) What is the output resistance R_{out}?

***11.80** The circuit in Fig. P11.80 is an implementation of a particular circuit building block known as **second-generation current convoyer** (CCII). It has three terminals besides ground: x, y, and z. The heart of the circuit is the feedback amplifier consisting of the differential amplifier μ and the complementary source follower (Q_N, Q_P). (Note that this feedback circuit is one we have encountered a number of times in this chapter, albeit with only one source-follower transistor.) In the following, assume that the differential amplifier has a very large gain μ and infinite differential input resistance. Also, let the two current mirrors have unity current-transfer ratios.

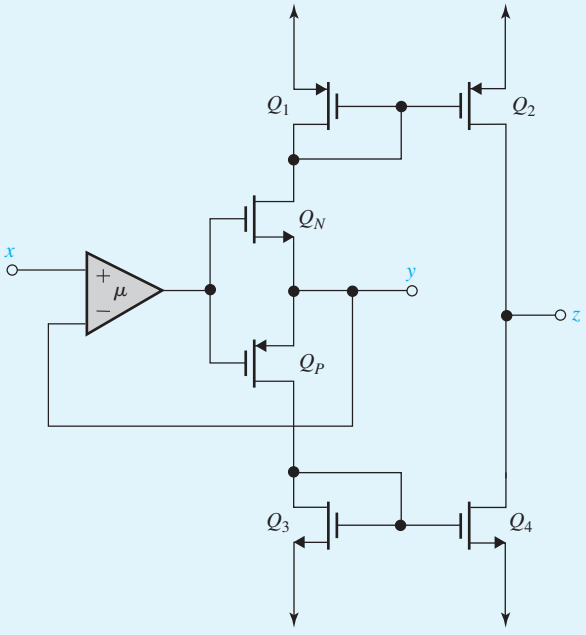


Figure P11.80

(a) If a resistance R is connected between y and ground, a voltage signal V_x is connected between x and ground, and z is short-circuited to ground. Find the current I_z through the short circuit. Show how this current is developed and its path for V_x positive and for V_x negative.
(b) If x is connected to ground, a current source I_y is connected to input terminal y, and z is connected to ground, what voltage appears at y and what is the input resistance seen by I_y? What is the current I_z that flows through the output short circuit? Also, explain the current flow through the circuit for I_y positive and for I_y negative.
(c) What is the output resistance at z?

SIM ***11.81** For the amplifier circuit in Fig. P11.81, assuming that V_s has a zero dc component, find the dc voltages at all nodes and the dc emitter currents of Q_1 and Q_2. Let the BJTs have $\beta = 100$. Use feedback analysis to find V_o/V_s and R_{in}. Let $V_{BE} = 0.7$ V.

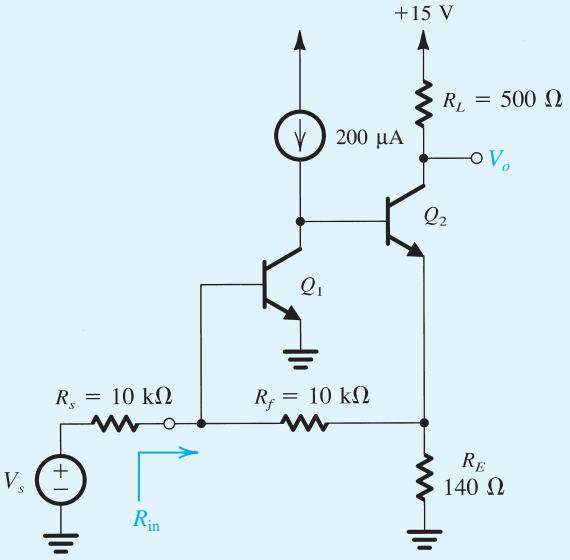


Figure P11.81

****11.82** Figure P11.82 shows a feedback amplifier utilizing the shunt–series topology. All transistors have $\beta = 100$ and $V_{BE} = 0.7$ V. Neglect r_o except in (f).

(a) Perform a dc analysis to find the dc emitter currents in Q_1 and Q_2 and hence determine their small-signal parameters.

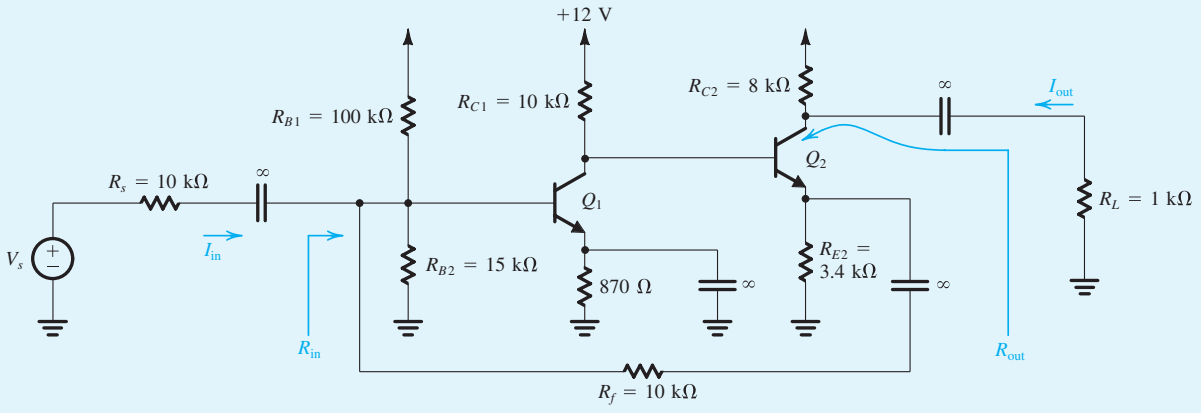


Figure P11.82

(b) Replacing the BJTs with their hybrid-π models, give the equivalent circuit of the feedback amplifier.

(c) Give the A circuit and determine A, R_i, and R_o. Note that R_o is the resistance determined by breaking the emitter loop of Q_2 and measuring the resistance between the terminals thus created.

(d) Find the β circuit and determine the value of β.

(e) Find $A\beta$, $1+A\beta$, A_f, R_{if}, and R_{of}. Note that R_{of} represents the resistance that in effect appears in the emitter of Q_2 as a result of the feedback.

(f) Determine R_{in}, I_{out}/I_{in}, and R_{out}. To determine R_{out}, use $V_{A2} = 75$ V and recall that the maximum possible output resistance looking into the collector of a BJT is approximately βr_o, where β is the BJT's β (see Problem 11.55).

Section 11.7: The Stability Problem

11.83 An op amp designed to have a low-frequency gain of 10^5 and a high-frequency response dominated by a single pole at 100 rad/s acquires, through a manufacturing error, a pair of additional poles at 20,000 rad/s. At what frequency does the total phase shift reach 180°? At this frequency, for what value of β, assumed to be frequency independent, does the loop gain reach a value of unity? What is the corresponding value of closed-loop gain at low frequencies?

***11.84** For the situation described in Problem 11.83, sketch Nyquist plots for $\beta = 1.0$ and 10^{-3}. (Plot for $\omega = 0$ rad/s, 100 rad/s, 10^3 rad/s, 10^4 rad/s, 2×10^4 rad/s, and ∞ rad/s.)

11.85 An op amp having a low-frequency gain of 10^4 and a single-pole rolloff at 10^3 rad/s is connected in a negative-feedback loop via a feedback network having a transmission k and a two-pole rolloff at 10^3 rad/s. Find the value of k above which the closed-loop amplifier becomes unstable.

11.86 Consider a feedback amplifier for which the open-loop gain $A(s)$ is given by

$$A(s) = \frac{10{,}000}{(1+s/10^4)(1+s/10^5)^2}$$

If the feedback factor β is independent of frequency, find the frequency at which the phase shift is 180°, and find the critical value of β at which oscillation will commence.

Section 11.8: Effect of Feedback on the Amplifier Poles

11.87 A dc amplifier having a single-pole response with pole frequency 10 Hz and unity-gain frequency of 1 MHz is operated in a loop whose frequency-independent feedback factor is 0.1. Find the low-frequency gain, the 3-dB frequency, and the unity-gain frequency of the closed-loop amplifier. By what factor does the pole shift?

11.88 An amplifier has dc open-loop gain of 80 dB and a single pole with 100-Hz frequency. It is utilized to design a feedback amplifier with a 3-dB frequency of 10 kHz. What β is needed? What is the dc closed-loop gain realized? Give an expression for $A_f(s)$.

SIM = Multisim/PSpice; * = difficult problem; ** = more difficult; *** = very challenging; D = design problem

*11.89 An amplifier having a low-frequency gain of 10^4 and poles at 10^4 Hz and 10^5 Hz is operated in a closed negative-feedback loop with a frequency-independent β.

(a) For what value of β do the closed-loop poles become coincident? At what frequency?
(b) What is the low-frequency, closed-loop gain corresponding to the situation in (a)? What is the value of the closed-loop gain at the frequency of the coincident poles?
(c) What is the value of Q corresponding to the situation in (a)?
(d) If β is increased by a factor of 10, what are the new pole locations? What is the corresponding pole Q?

D 11.90 A dc amplifier has an open-loop gain of 1000 and two poles, a dominant one at 1 kHz and a high-frequency one whose location can be controlled. It is required to connect this amplifier in a negative-feedback loop that provides a dc closed-loop gain of 10 and a maximally flat response. Find the required value of β and the frequency at which the second pole should be placed. What is the 3-dB frequency of the closed-loop amplifier?

11.91 Reconsider Example 11.11 with the circuit in Fig. 11.34, modified to incorporate a so-called tapered network, in which the components immediately adjacent to the amplifier input are raised in impedance to $C/10$ and $10R$. Find expressions for the resulting pole frequency ω_0 and Q factor. For what value of K do the poles coincide? For what value of K does the response become maximally flat? For what value of K does the circuit oscillate?

D 11.92 A feedback amplifier having a dc closed-loop gain of 10 and a maximally flat second-order response with a 3-dB frequency of 1 kHz is required. The open-loop amplifier utilizes a cascade of two identical amplifier stages, each having a single-pole frequency response. Find the values required for β, the 3-dB frequency, and the dc gain of each of the two amplifier stages. Give an expression for $A_f(s)$.

11.93 Three identical inverting amplifier stages, each characterized by a low-frequency gain K and a single-pole response with $f_{3dB} = 100$ kHz, are connected in a feedback loop with $\beta = 1$. What is the minimum value of K at which the circuit oscillates? What would the frequency of oscillation be?

Section 11.9: Stability Study Using Bode Plots

11.94 Reconsider Exercise 11.26 for the case of the op amp wired as a unity-gain buffer. At what frequency is $|A\beta| = 1$? What is the corresponding phase margin?

11.95 Reconsider Exercise 11.26 for the case of a manufacturing error introducing a second pole at 10^3 Hz. What is now the frequency for which $|A\beta| = 1$? What is the corresponding phase margin? For what values of β is the phase margin 45° or more?

11.96 For what phase margin does the gain peaking have a value of 5%? Of 10%? Of 0.1 dB? Of 1 dB? Of 3 dB? [*Hint:* Use the result in Eq. (11.82).]

11.97 An amplifier has a dc gain of 10^4 and poles at 10^5 Hz, 3.16×10^5 Hz, and 10^6 Hz. Find the value of β, and the corresponding closed-loop gain, for which a phase margin of 45° is obtained.

11.98 A two-pole amplifier for which $A_0 = 10^3$ and having poles at 1 MHz and 10 MHz is to be connected as a differentiator. On the basis of the rate-of-closure rule, what is the smallest differentiator time constant for which operation is stable? What are the corresponding gain and phase margins?

11.99 For the amplifier described by Fig. 11.37 and with frequency-independent feedback, what is the minimum closed-loop voltage gain that can be obtained for phase margins of 90° and 45°?

Section 11.10: Frequency Compensation

D 11.100 A multipole amplifier having a first pole at 1 MHz and a dc open-loop gain of 80 dB is to be compensated for closed-loop gains as low as unity by the introduction of a new dominant pole. At what frequency must the new pole be placed?

D 11.101 For the amplifier described in Problem 11.100, rather than introducing a new dominant pole we can use additional capacitance at the circuit node at which the pole is formed to reduce the frequency of the first pole. If the frequency of the second pole is 20 MHz and if it remains unchanged while additional capacitance is introduced as

mentioned, find the frequency to which the first pole must be lowered so that the resulting amplifier is stable for closed-loop gains as low as unity. By what factor is the capacitance at the controlling node increased?

11.102 For the amplifier whose $A(s)$ is depicted in Fig. 11.38, to what value must the first pole frequency be lowered to obtain stable performance for (a) $\beta = 0.001$ and (b) $\beta = 0.1$?

11.103 Contemplate the effects of pole splitting by considering Eqs. (11.89), (11.93), and (11.94) under the conditions that $R_1 \simeq R_2 = R$, $C_2 \simeq C_1/10 = C$, $C_f \gg C$, and $g_m = 100/R$, by calculating ω_{P1}, ω_{P2}, and ω'_{P1}, ω'_{P2}. Comment on the results.

D 11.104 An op amp with open-loop voltage gain of 10^5 and poles at 10^6 Hz, 10^7 Hz, and 10^8 Hz is to be compensated by the addition of a fourth dominant pole to operate stably with unity feedback ($\beta = 1$). What is the frequency of the required dominant pole? The compensation network is to consist of an *RC* low-pass network placed in the negative-feedback path of the op amp. The dc bias conditions are such that a 1-MΩ resistor can be tolerated in series with each of the negative and positive input terminals. What capacitor is required between the negative input and ground to implement the required fourth pole?

D *11.105 An op amp with an open-loop voltage gain of 80 dB and poles at 10^5 Hz, 10^6 Hz, and 2×10^6 Hz is to be compensated to be stable for unity β. Assume that the op amp incorporates an amplifier equivalent to that in Fig. 11.40, with $C_1 = 150$ pF, $C_2 = 5$ pF, and $g_m = 40$ mA/V, and that f_{P1} is caused by the input circuit and f_{P2} by the output circuit of this amplifier. Find the required value of the compensating Miller capacitance and the new frequency of the output pole.

SIM **11.106 The op amp in the circuit of Fig. P11.106 has an open-loop gain of 10^5 and a single-pole rolloff with $\omega_{3\text{dB}} = 10$ rad/s.

(a) Sketch a Bode plot for the loop gain.
(b) Find the frequency at which $|A\beta| = 1$, and find the corresponding phase margin.
(c) Find the closed-loop transfer function, including its zero and poles. Sketch a pole-zero plot. Sketch the magnitude of the transfer function versus frequency, and label the important parameters on your sketch.

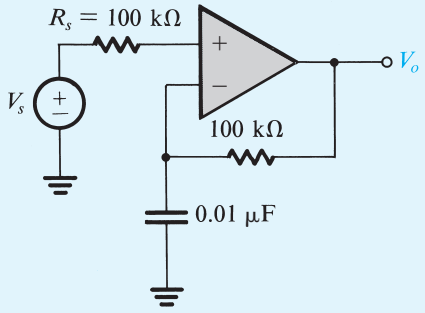


Figure P11.106

SIM = Multisim/PSpice; * = difficult problem; ** = more difficult; *** = very challenging; D = design problem